



COLLEGE OF ENGINEERING & TECHNOLOGY

Department : Electrical & Control Engineering

Lecturer : Staff

Course : Electric Circuits I

Course Code : EE 231

Marks : 40

Date : 14/1/2015

Time : 2 hour

Final Exam

Answer all the following questions

1. For the circuit shown in figure 1, find the power dissipated in the $2\ \Omega$ resistor.

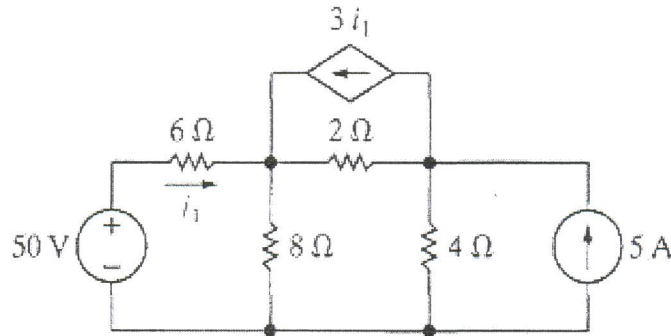


Figure 1

(8 marks)(B.2)

2. Find the Thevenin equivalent circuit between terminals a & b for the circuit shown in Figure 2.

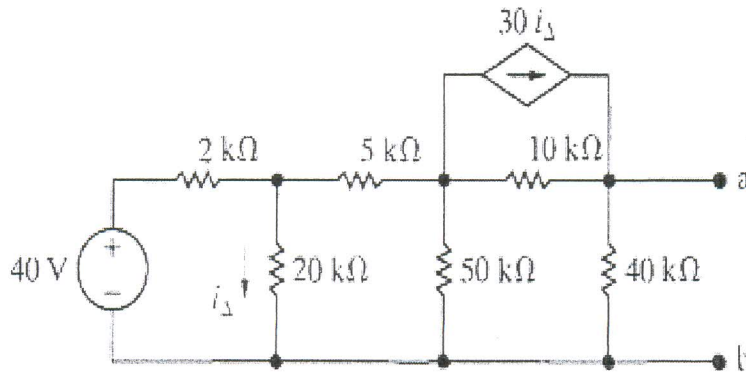


Figure 2

(8 marks)(A.13)

Members of course Examination Committee:	Signature:	Date:
Lecturers: Dept. Staff	<i>S. Elsayfy</i>	6/1/2015
Course Coordinator : Prof. Samah Elsafty		6/1/2015
Head of Department : Prof. Hamdy Ashour	<i>Hamdy</i>	6/1/2015

3. For the circuit shown in Figure 3, find v_0 using the principle of superposition.

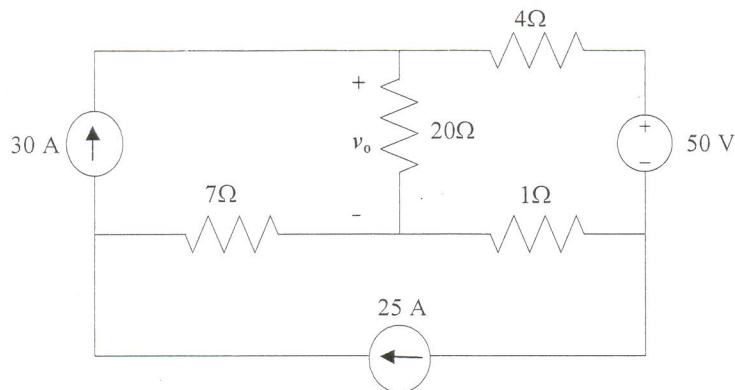


Figure 3

(8 marks)(A.25)

4. A sinusoidal voltage is given by the expression $v = 300 \cos(100\pi t + 30^\circ)$

- What is the period of the voltage in second?
- What is the frequency in Hertz?
- What is the magnitude of v at $t = 2.778 \text{ ms}$?
- What is the RMS of v ?

(4 marks)(A.25)

5. For the circuit shown in Figure 4, find the average value and the effective value.

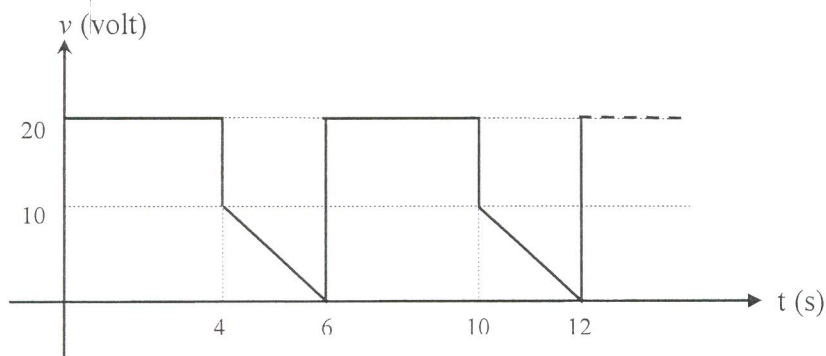


Figure 4

(4 marks)(A.25)

6. For the circuit shown in Figure 5,

$$v(t) = 100 \sin 377t$$

- Find I , V_R , V_1 .
- Find the average (real) power.
- Draw the phasor diagram for V , I , V_R , and V_1 .

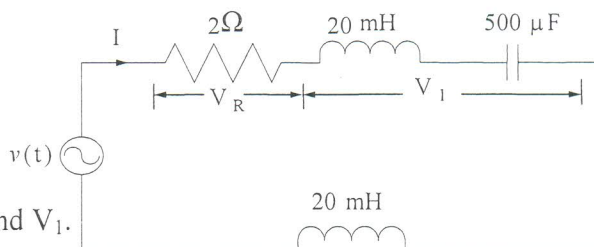


Figure 5 (8 marks)(B.2)

Members of course Examination Committee:	Signature:	Date:
Lecturers: Dept. Staff	<i>Safy</i>	6/1/2015
Course Coordinator : Prof. Samah Elsafty	<i>Hamdy</i>	6/1/2015
Head of Department : Prof. Hamdy Ashour		

GOOD LUCK