



COLLEGE OF ENGINEERING & TECHNOLOGY

Department : Electrical & Control Engineering

Lecturer : Staff

Course : Electrical Circuits II

Marks: 40

Course Code : EE 232

Time: 2 hours

Date : 1/6/2015

Starting time: 14:00

Final Exam

Answer the following questions

1. For the circuit shown in Fig. 1, find the current I_x .

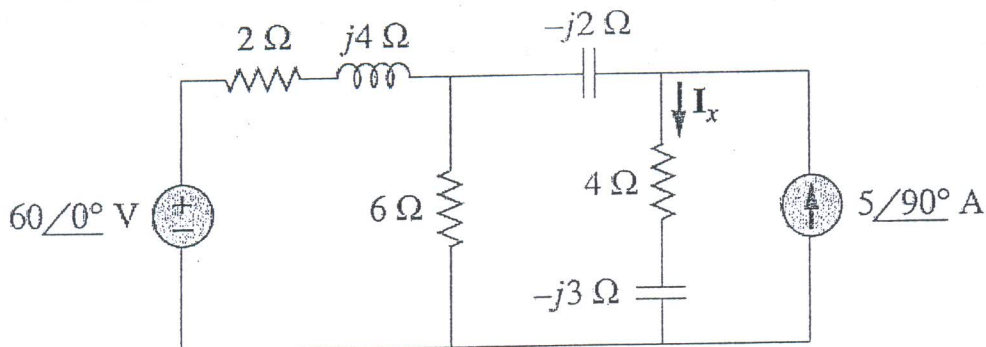


Figure 1

(8 marks) [A.30,B.2]

2. For the circuit shown in Fig. 2, Determine I_s , if the voltage source supplies 2.5 kW and 0.4 kVAR (leading).

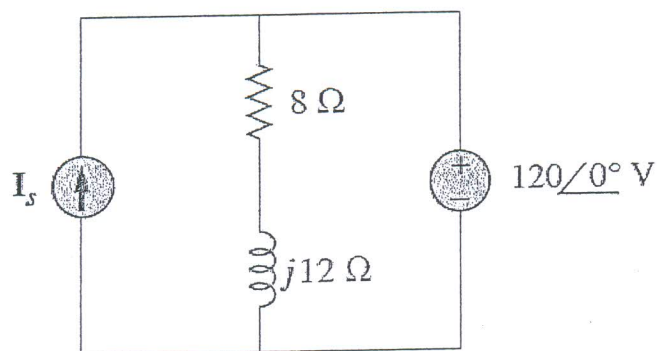


Figure 2

(8 marks) [A.13]

Members of course Examination Committee:	Signature:	Date:
Lecturer: Staff	<i>Safky</i>	6/5/2015
Course Coordinator : Prof. Samah El Safty	<i>Hamdy</i>	6/5/2015
Head of Department: Prof. Hamdy Ashour		

3. A balanced star connected load with a phase impedance of $10-j16 \Omega$ is connected to a balanced three phase generator with a line voltage of 220 V. Determine the line current and the complex power absorbed by the load.

(8 Marks)[A.5]

4. For the unbalanced circuit shown in Fig. 3, find the phase current I_{AB} and the line current I_{aA} .

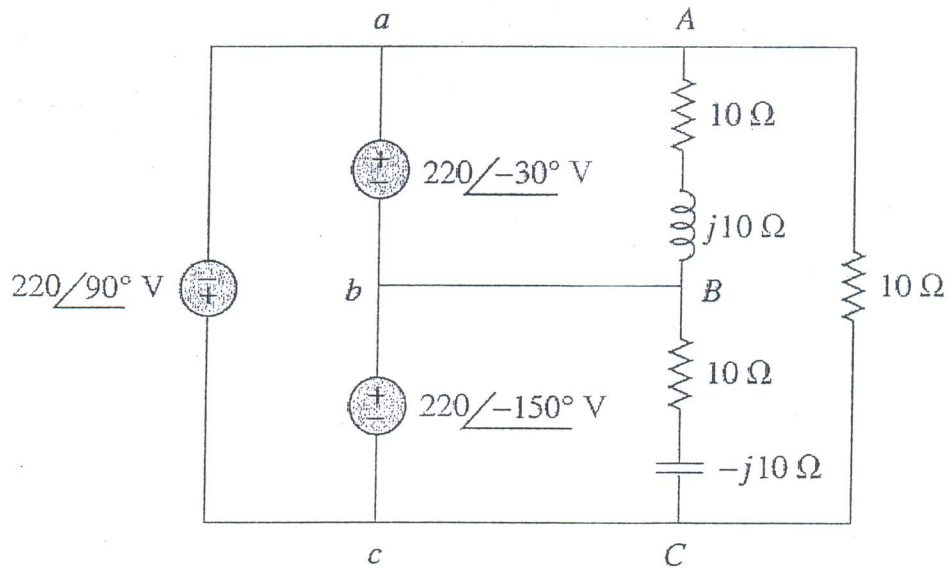


Figure 3

(8 marks) [A.5]

5. For the circuit shown in Fig. 4, the switch has been open for a long time. At $t=0$ the switch is closed. Find:
- $v(t)$ for $t > 0$
 - $i(t)$ for $t > 0^+$

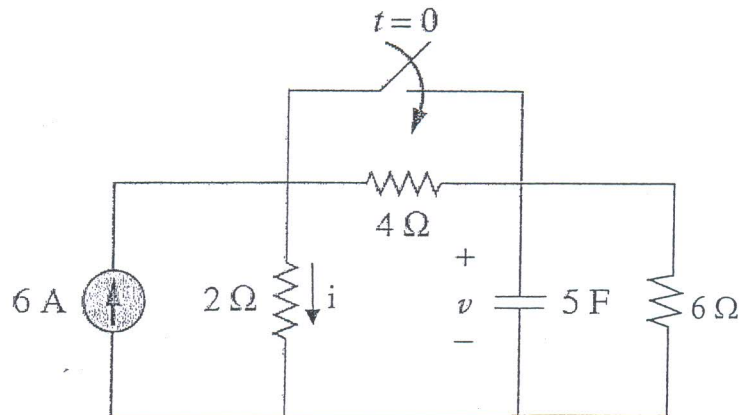


Figure 4

(8 marks) [A.30,B.2]

Good Luck

Members of course Examination Committee:	Signature:	Date:
Lecturer: Staff		
Course Coordinator : Prof. Samah El safty	<i>safty</i>	6/5/2015
Head of Department: Prof. Hamdy Ashour	<i>Hamdy</i>	6/5/2015