



COLLEGE OF ENGINEERING & TECHNOLOGY

Department : Electrical & Control Engineering

Lecturer : Dr. Hussein El Desouki

Course : Electric Engineering (1)

Course Code : EE 236

Date : 17 / 1 / 2016

Marks : 40

Time : 2 hour

Final Exam

Answer the following questions:-

Question 1:

Find the power dissipated in the 5Ω shown in figure 1, using node voltage method OR mesh current method.

8 Marks
(A1, A5, B13)

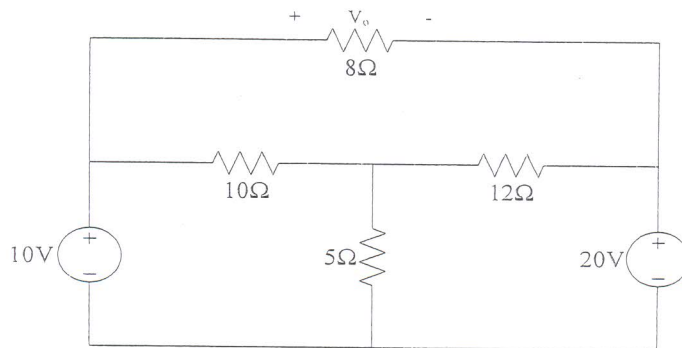


Figure 1

Question 2:

I. Define the following terms:

- Magnetic flux (Φ).
- Magnetic permeability (μ).
- Magnetic field intensity (H).

8 Marks
(A1, A5, B7)

Members of course Examination Committee:	Signature:	Date:
Lecturer:	H. Desouki	3/1/2016
Course Coordinator :	Safy	3/1/2016
Head of Department:	H. Desouki	3/1/2016

II. Find the current I required shown in figure 2 to establish a flux $\Phi = 4 \times 10^{-4}$ Wb in the magnetic circuit:

Area (throughout) = $2 \times 10^{-4} \text{ m}^2$.

$N = 100$ Turns.

$l_{ab} = l_{cd} = 0.05 \text{ m}$.

$l_{ad} = l_{bc} = 0.02 \text{ m}$.


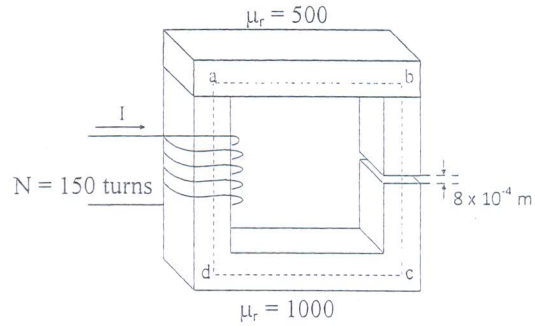


Figure 2

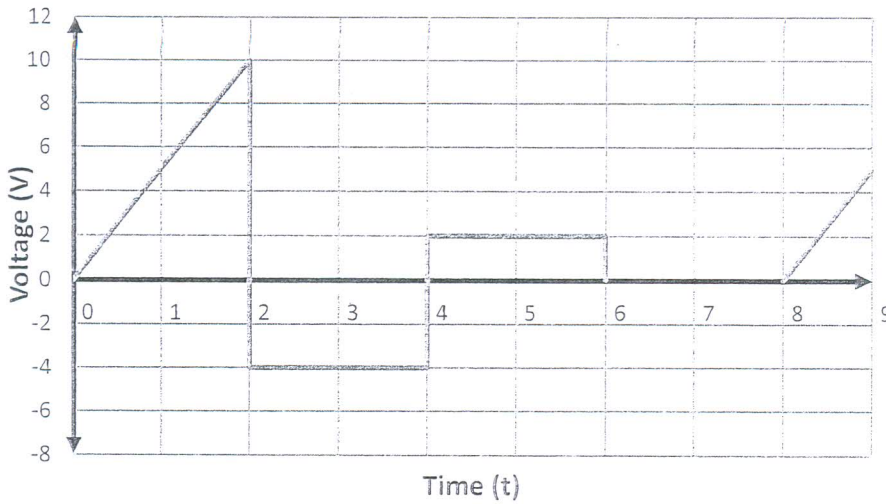Question 3:

Find the average and the RMS for the waveform shown in figure 3:



8 Marks
(A1, A5, C1, C6)

Figure 3

Members of course Examination Committee:	Signature:	Date:
Lecturer:	<i>H. Doran</i>	3/1/2016
Course Coordinator :	<i>S. J. J.</i>	3/1/2016
Head of Department:	<i>Hamdy</i>	3/1/2016

