



# COLLEGE OF ENGINEERING & TECHNOLOGY

Department : Electrical & Computer Control Engineering

Lecturer : Prof. Ahmed F. Amer

Course : Electrical Engineering II

Course Code : EE 326

Marks : 40

Date : 9 / 1 / 2016

Time : 2 hours

## Answer Four Questions Only:

### Question One: (10 marks)

- Explain briefly using a neat sketch the general configuration of a control system showing the different control components of the loop and the function of each component.
- Find the overall transfer function  $C(s)/R(s)$  for the given closed-loop system shown in Fig.1 below.

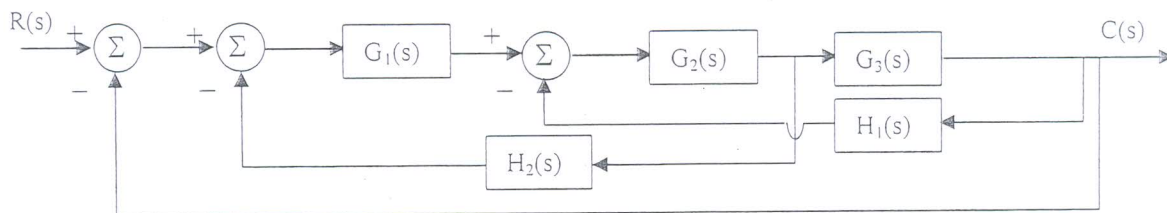


Fig.1

### Question Two: (10marks)

- An R-C circuit has a resistance of  $500 \text{ k}\Omega$  and a capacitor of  $100 \mu\text{F}$  is shown in the circuit given below, determine:
  - The circuit transfer function  $V_o(s)/V_i(s)$ .
  - Circuit time constant.
  - Draw the output voltage for a step input voltage of 100V.

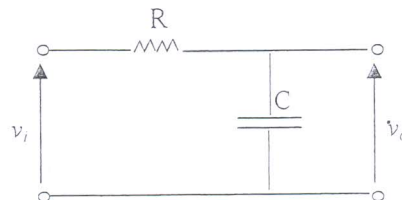


Fig.2 R-C electric circuit

Members of course Examination Committee	Signature	Date
Lecturer: Prof. Ahmed Fouad M. Amer	<i>Ahmed F. Amer</i>	6/1/2016
Course Coordinator : Dr. Ahmed Kadry	<i>Ahmed Kadry</i>	6/1/2016
Head of Department: Prof. Hamdy Ashour	<i>Hamdy Ashour</i>	6/1/2016

(b) The mass-spring-damper mechanical system shown in Fig.3 has a mass  $m$ , kg, a spring of stiffness  $k_s$ , N/m and a damper of damping coefficient  $b$ , N/m/sec. If a unit-impulse force is applied to the system as shown in figure below:

- Obtain the system differential equation.
- Determine the system transfer function.
- If  $m=1$  N/m/sec<sup>2</sup>,  $b=4$  N/m/sec, and  $k_s=13$  N/m, obtain the natural frequency and the damping factor of the system.
- If  $b=0$ , find the system response for an impulse function.

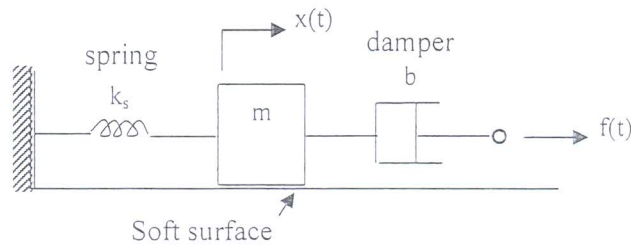


Fig. 3 A spring-mass-dashpot mechanical system

Question Three:

- Explain briefly the idea of D.C. (d'Arsonval) moving coil meter and show how it can be used to measure different ranges of voltages.
- An ammeter is used to measure d.c. currents. It has an internal resistance (meter resistance,  $R_M$ ) of  $105 \Omega$  and the maximum coil current is  $10$  mA. Calculate the required shunt resistors to measure different ranges of currents of  $25$ mA and  $200$ mA.

Question Four:

- Draw neat sketches for the different types of d.c. generators.
- A dc shunt motor has an armature resistance of  $0.01 \Omega$  runs at  $1000$  rpm. The supply voltage is  $250$  V and the shunt field resistance is  $250 \Omega$ . The input power equals  $6.5$  kW. The supply voltage is reduced to  $230$  V and the field resistance is reduced to  $125 \Omega$ . Find the new speed to keep the motor torque constant.
- A  $25$  kVA single-phase transformer has  $500$  turns on the primary and  $50$  turns on the secondary winding. The primary winding is connected to a  $3000$  V,  $50$  Hz supply. Find the full-load primary and secondary currents, and the secondary emf induced voltage. Neglect leakage drops and no load current (i.e., consider an ideal transformer).

Members of course Examination Committee	Signature	Date
Lecturer: Prof. Ahmed Fouad M. Amer	<i>Ahmed Fouad M. Amer</i>	
Course Coordinator : Dr Ahmed Kadry	<i>Ahmed Kadry</i>	6/11/2016
Head of Department: Prof. Hamdy Ashour	<i>Hamdy Ashour</i>	6/11/2016

