

COLLEGE OF ENGINEERING & TECHNOLOGY



Department : Electrical & Computer Control Engineering
 Lecturer : Dr. M. Abdel-Rahim
 Course : Network Analysis
 Course Code : EE 332
 Date : 12 / 1 / 2016

Marks : 40
 Time : 2 hours

Final Exam

Answer the following questions:-

1- Let $i_g(t) = 5 e^{-4t} \cos(3t + 60^\circ)$ A in the circuit shown in fig.(1), and using the concept of the complex frequency.

- (i) Find the phasor value V_{in} .
- (ii) Find $v_{in}(t)$.

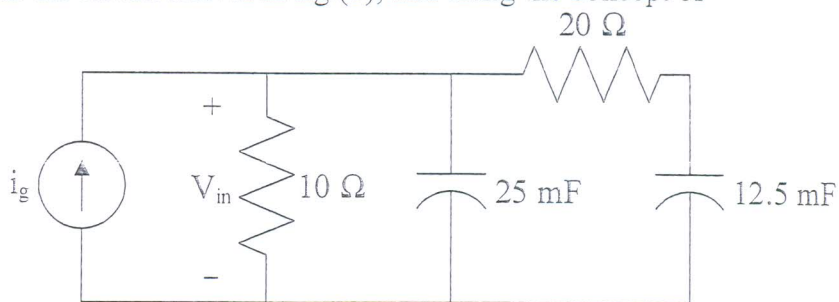


fig.(1)

b) For the circuit shown in fig.(2), let $H(s) = \frac{V_x(s)}{I_g(s)}$

- (i) Find $|H(\sigma)|$ as a ration of polynomials of σ .
- (ii) Determine all the critical frequencies of $H(\sigma)$.
- (iii) Sketch $|H(\sigma)|$ versus σ .

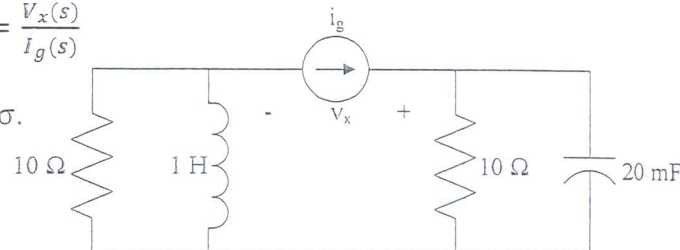


fig.(2)

(10 marks) (AI)

2- Draw the Bode amplitude and phase plots for the following transfer function

$$H(s) = \frac{5 \times 10^5 (s + 10)}{s(s + 25)(s + 100)^2} \quad (6 \text{ marks}) \text{ (AI)}$$

Members of course Examination Committee:	Signature:	Date:
Lecturer: <i>Dr. M. Abdel-Rahim</i>	<i>M. Abdel-Rahim</i>	<i>4/1/2016</i>
Course Coordinator: <i>Samah El Solhy</i>	<i>Samah</i>	<i>4/1/2016</i>
Head of Department: <i>Prof. Hany Ashour</i>	<i>Hany</i>	<i>4/1/2016</i>

3- The switch in the circuit shown in fig.(3) has been in position a for a long time.

At $t = 0$, the switch is moved to position b.

- (i) Construct the s-domain equivalent circuit for $t > 0$.
- (ii) Find $V_o(s), I_o(s)$.
- (iii) Find $v_o(t), i_o(t)$ for $t \geq 0$.

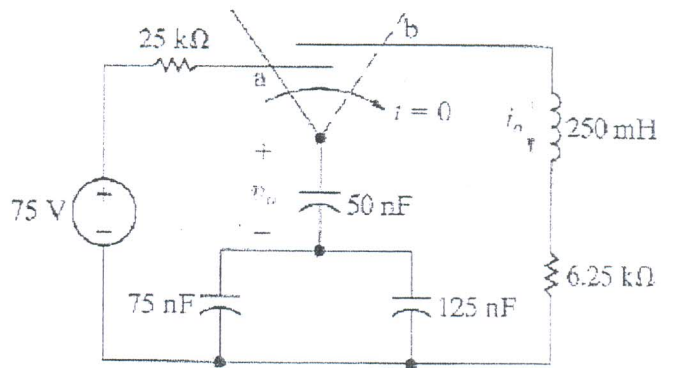


fig.(3) (8 marks) (B2)

4- Let $V_s = 100 \angle 0^\circ$ V rms and $\omega = 100$ rad/s in the circuit shown in fig.(4). Find the average power supplied to the 3-Ω resistor.

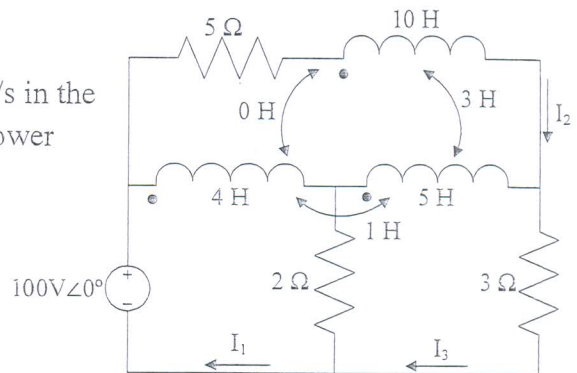


fig.(4)

(8 marks) (A25)

5 – The y-parameters of the network shown in fig.(5) is given as

$$y_{11} = 2 \text{ mS} ; y_{12} = -2 \mu\text{S}$$

$$y_{21} = 100 \text{ mS} ; y_{22} = -50 \mu\text{S}$$

- (a) Find the value of Z_L for maximum average power transfer to Z_L .
- (b) Find the maximum average power delivered to Z_L .

$$\text{If } v_g = 80 \sqrt{2} \cos 4000t \text{ mV, } Z_g = 2500 + j0 \Omega.$$

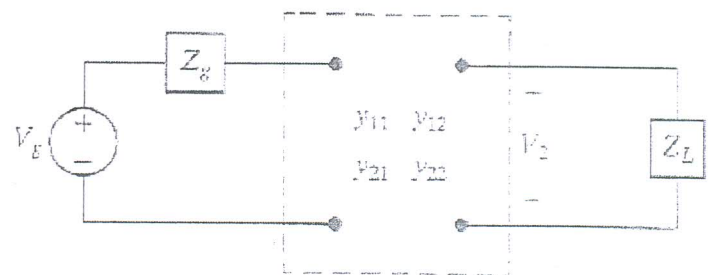


fig.(5)

(8 marks) (A25)

GOOD LUCK

Members of course Examination Committee:	Signature:	Date:
Lecturer: <i>Dr. M. Abdel-Rahim</i>	<i>M. Abdel-Rah</i>	<i>4/1/2016</i>
Course Coordinator: <i>Sarah El Sayy</i>	<i>Sah</i>	<i>4/1/2016</i>
Head of Department: <i>Mohamed Ashour</i>	<i>Moh</i>	<i>4/1/2016</i>