



# COLLEGE OF ENGINEERING & TECHNOLOGY

Department: Electrical & Computer Control Engineering

Lecturer : Prof. Dr. Hamdy Ashour

Marks: 40

Course : Power Electronics (II)

Time: 2 hours

Course Code: EE 423

Date : 09/ 01/ 2016

## Final Exam

### Answer ALL questions

**Q1-** Design power electronic circuits that can be used to: (8Marks) (A4)

- (a) Control the light intensity of incandescent lamp of 220V/50Hz fed from 220V/50Hz supply
- (b) Charging a battery of 18V from 12V output voltage of the photovoltaic cell (PV)
- (c) Generate a 4-ph AC supply of 100V/400Hz from 200V battery
- (d) Continuously feeding a computer (PC) with 220V/50Hz in case of main supply failure

**Q2-** Use simple sketches to discuss concept and typical application of:- (8Marks) (A8, A24)

- (a) 4-Quadrant DC chopper
- (b) Sinusoidal Pulse Width Modulation (SPWM)
- (c) Gate drive circuit
- (d) AC static switch

**Q3** (6 Marks) (A8, A24)

(a) For the circuit shown in figure1 draw wave forms of  $v_s$  ,  $v_1$  ,  $v_2$  and  $v_o$  giving that ,  $v_s = 24V$ ,

$N_p / N_s = 24 / 200$  and gating signals are  $Q_1 = \overline{Q_2}$  of 10kHz

(b) For the circuit shown in figure2 draw waveforms of gate signals,  $v_s$  ,  $i_s$  and  $v_o$  giving that,

$v_s = 300\sin(100\pi)t$  V ,  $R_L = 5\Omega$  and  $T_1$  gating signals are repeated each half cycle with firing

delay angle  $\alpha = 30$  degree.

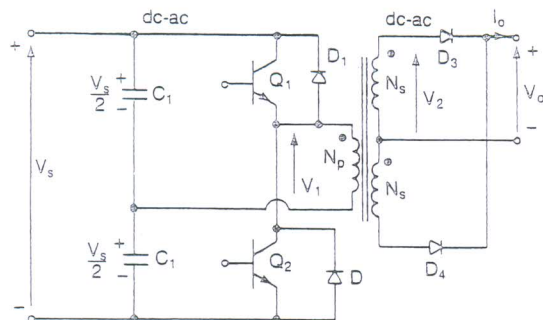


Figure1

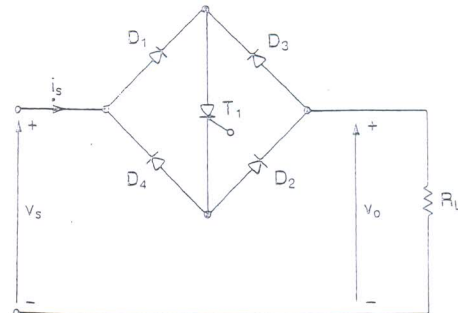


Figure2

Members of course Examination Committee:	Signature:	Date:
Lecturer: <i>Prof. Hamdy Ashour</i>	<i>Hamdy</i>	<i>3/1/2016</i>
Course Coordinator : <i>Dr Ahemd Kadery</i>	<i>Hamdy</i>	<i>3/1/2016</i>
Head of Department: <i>Prof. Hamdy Ashour</i>		

Q4- For the Cycloconverter circuit, shown figure3, if input voltage  $v_s = 120V/60Hz$

- (a) Draw, input voltage ( $v_s$ ), Thyristors gate signals, and output voltage ( $v_o$ ) waveforms for delay angle  $\alpha_p = 90$  degree and to give output frequency of  $30 Hz$ .  
 (b) Calculate the corresponding value of the ( $V_o$ ) RMS

(6 Marks) (A24, B2)

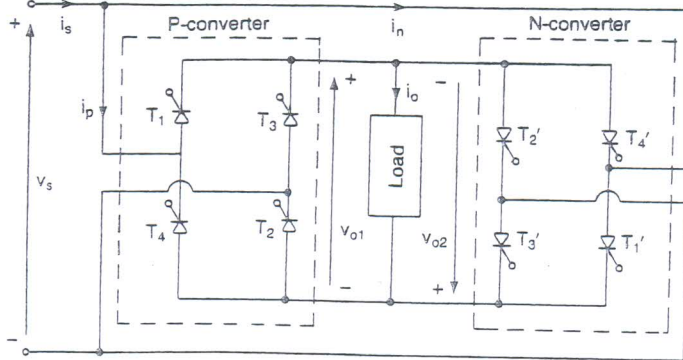


Figure 3

Q5- For the regulator shown in figure4, if the supply voltage  $V_s = 48V$ , the required average load voltage  $V_a = 24V$  at  $R=100\Omega$ ,  $\Delta V_C = 100mV$ ,  $\Delta I_L = 0.9A$ , switching frequency is  $f=10kHz$ ,

- (a) Calculate the required duty cycle  $k$  and values of the filter  $L$  and  $C$ .  
 (b) State two different typical applications of that circuit

(6 Marks) (A24, B2)

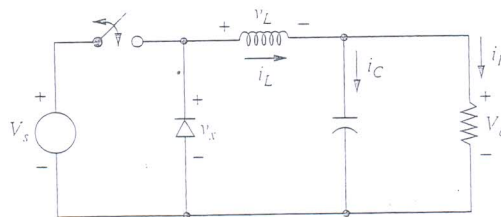


Figure 4

Q6- An H-bridge 1-ph inverter has a load of  $5\Omega$  resistive and  $20\Omega$  inductive while the battery voltage is  $48V$ .

- (a) Draw gate signals and waveforms of transistors currents and output voltage to get  $V_0=48V/25Hz$  then calculate total harmonic distortion and third harmonic factor.  
 (b) Suggest two different methods to reduce the output voltage to be  $24V$

(6 Marks) (A24, B2)

**GOOD LUCK**

Members of course Examination Committee:	Signature:	Date:
Lecturer: Prof. Hamdy Ashour	<i>Hamdy</i>	3/1/2016
Course Coordinator : Dr Ahemd Kadery	<i>Ahmed</i>	
Head of Department: Prof. Hamdy Ashour	<i>Hamdy</i>	3/1/2016