

VLSI DIGITAL DESIGN Projects

- 1- 4 bit flash ADC:
- 2- 4-stage binary asynchronous counter:
- 3- Arithmetic Logic Unit
- 4- 3 bit ADC
- 5- Oscillators: Ring and VCO
- 6- 3 bit charge scaling DAC
- 7- Simple Voltage regulator
- 8- Programmable Analog to Digital Converter
- 9- 3 bit comparator design