



### Sheet #5

[1] For the transistor shown in fig.1,  $\mu_n C_{ox}(W/L) = 0.5 \text{ mA/V}^2$  and  $r_o = 100 \text{ k}\Omega$ . Find  $v_o/v_i$ ,  $R_i$  and  $R_o$ . What does the gain become for  $R_S = 0$ ? And for  $R_S = 3.76 \text{ k}\Omega$ ?

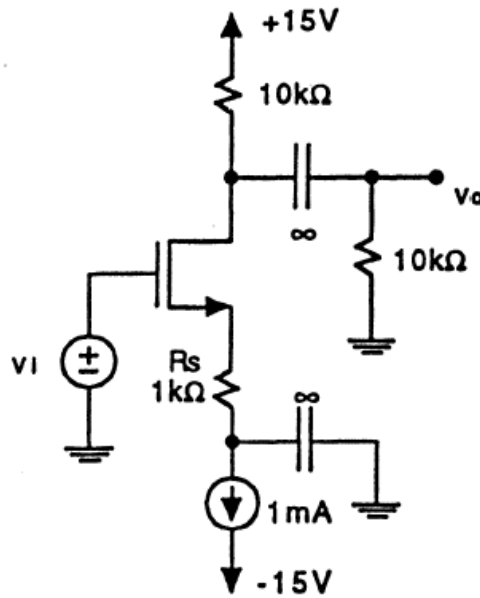


Figure 1

[2] For the transistor shown in fig.2,  $\mu_n C_{ox}(W/L) = 2 \text{ mA/V}^2$ ,  $V_t = 1 \text{ V}$ , and  $V_A = 50 \text{ V}$ . For  $I = 1 \text{ mA}$ , what are  $v_o/v_i$ ,  $R_i$ ,  $R_o$  for  $R_L = R_G$ ?  $r_o$ ?

Note: Channel Length Modulation Effect is neglected in dc analysis.

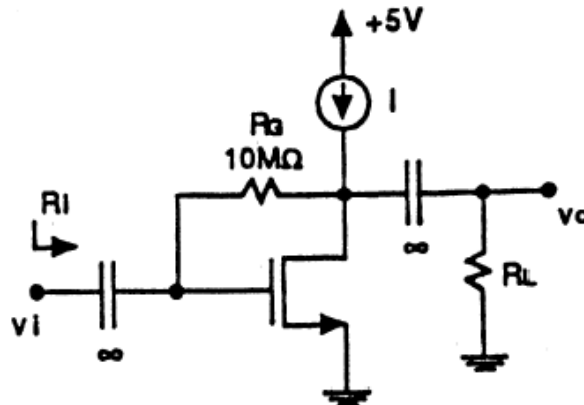


Figure 2

[3] For the CMOS amplifier shown in fig.3 and employs devices for all of which  $k=k'(W/L)=20\mu\text{A}/\text{V}^2$  and  $V_A=100\text{V}$ . What is the small-signal voltage gain,  $R_{in}$  and  $R_{out}$  which results for  $I_{REF}=25\mu\text{A}$ ?

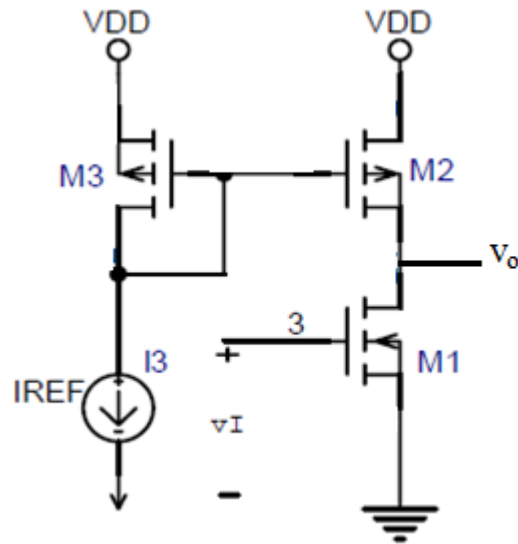


Figure 3

[4] For the common drain shown in fig.4,  $\mu_n C_{ox} = 0.1\text{mA}/\text{V}^2$ ,  $\frac{W}{L} = 1$  for  $V_t = 1\text{V}$  and  $\lambda = 0.01\text{V}^{-1}$ . Find the small-signal voltage gain,  $R_{in}$  and  $R_{out}$ .

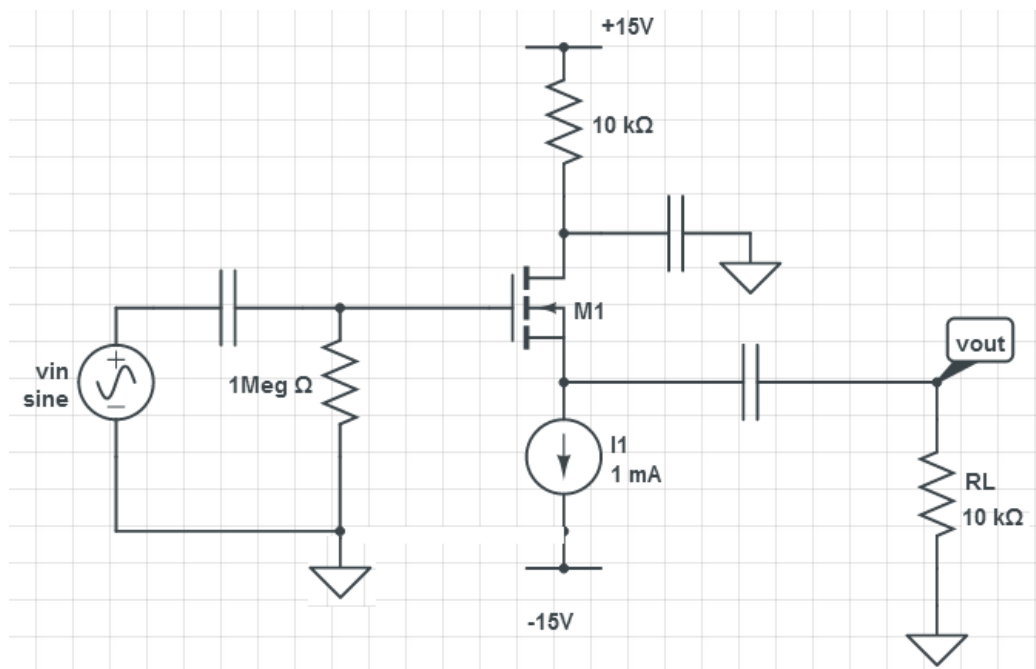


Figure 4

[5] For the common gate shown in fig.5,  $\mu_n C_{oc} = 0.1 \text{mA/V}^2$ ,  $\frac{W}{L} = 8$  for  $V_t = 1 \text{V}$  and  $\lambda = 0.01 \text{V}^{-1}$ .  
 Find the small-signal voltage gain,  $R_{in}$  and  $R_{out}$ .

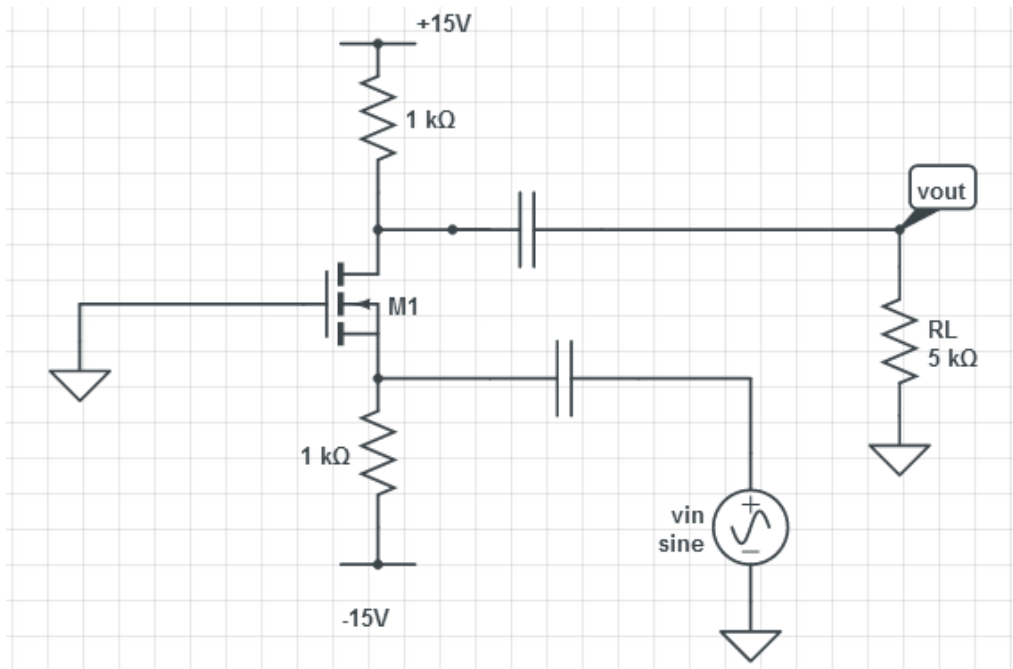


Figure 5