

EC332 Devices 2

Sheet 6 (ctd.)and 7

A decorative graphic consisting of several horizontal lines of varying lengths and colors (teal, light blue, white) extending from the right side of the page towards the center.

BJT

- Rules:

- $I_E = I_B + I_C$

For Active Region:

- $V_{BE} = 0.7$

- $I_E = (\beta + 1) I_B$

- $I_C = \beta I_B$

- $I_C = \alpha I_E$

- $\alpha = \frac{\beta}{\beta + 1}$

- $\beta = \frac{\alpha}{1 - \alpha}$

Sheet 6 - P3(a)

(Q) Assume Active region

$$V_{BE} = 0.7 \quad \beta = 10$$


Apply KVL:

$$-10 + 100k I_B + 0.7 = 0$$

$$I_B = 93 \mu A$$

$$I_C = \beta I_B = 0.93 \text{ mA}$$

$$I_E = (\beta + 1) I_B = 1.023 \text{ mA}$$

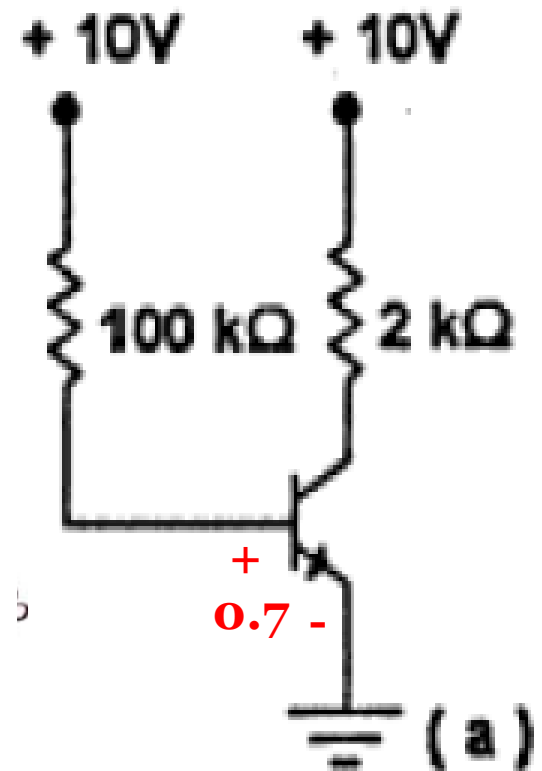

Sheet 6- P3(c)

(c) $\because V_E = 0 \ \Delta \ V_{BE} = 0.7$

$\therefore V_B = 0.7$

$$I_1 = \frac{10 - V_B}{100k} \quad I_2 = \frac{V_B - 0}{10k}$$

Apply KCL at base:


$$I_1 = I_B + I_2$$

$$I_B = I_1 - I_2 = 23 \mu A$$

$$I_C = \beta I_B = 0.23 \text{ mA}$$

$$I_E = (\beta + 1) I_B = 0.253 \text{ mA}$$

$$\frac{10 - V_C}{2k} = I_C \quad V_C = 9.54 \text{ V}$$

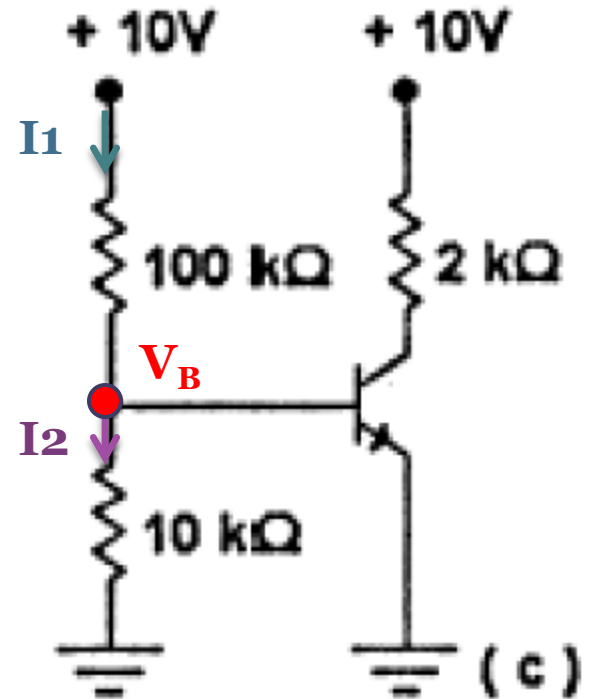

Sheet 6 - P3(b)

$$(b) \because V_{EB} = 0.7V \text{ \& } V_E = 10V$$


$$\therefore V_B = 9.3V$$

$$I_B = \frac{V_B}{100k} = 93 \mu A$$

$$I_C = \beta I_B = 0.93 \text{ mA}$$

$$I_E = (\beta + 1) I_B = 1.023 \text{ mA}$$

$$\frac{V_C - 0}{2k} = I_C \quad V_C = 1.86V$$

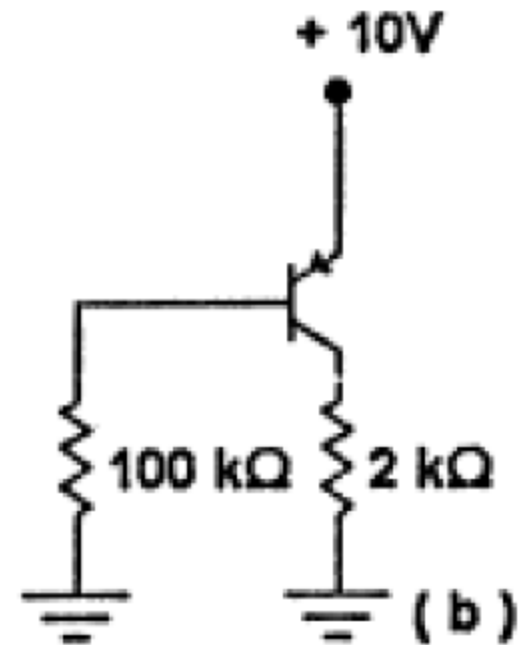

Sheet 6 - P3 (d)

(d) $V_{EB} = 0.7$ & $V_E = 0V$


$$I_1 = \frac{10 - V_B}{100k} \quad I_2 = \frac{V_B - (-10V)}{100k}$$

Apply KCL:

$$I_2 = I_1 + I_B \quad I_B = I_2 - I_1$$

$$I_B = -1.4 \times 10^{-5}$$

Not in Active Region.

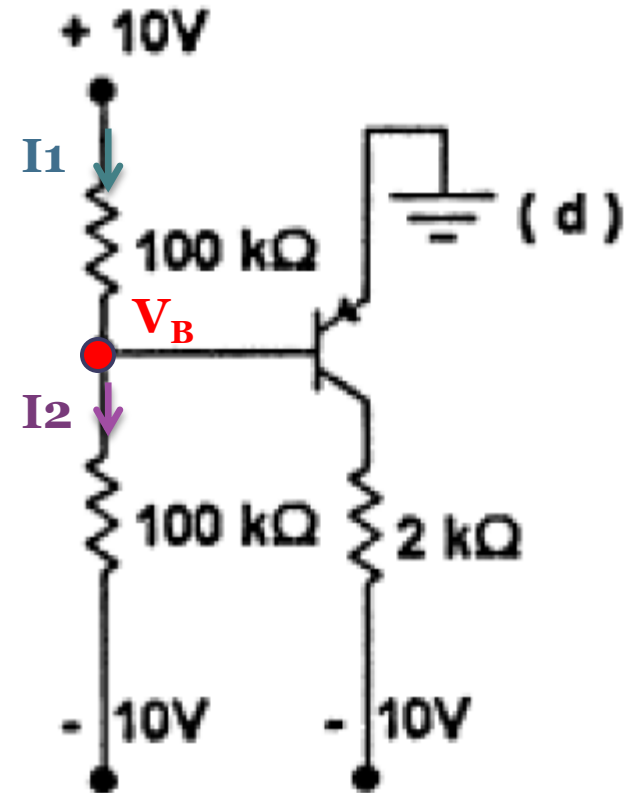

Sheet 6-P4(a)

(a) At node B:

$$I_1 = I_B + 20\mu \quad \text{--- (1)}$$

At node C:

$$\begin{aligned} I_2 &= I_1 + I_C \\ &= I_B + 20\mu + I_C \\ &= I_B + 20\mu + \beta I_B \\ I_2 &= (\beta + 1) I_B + 20\mu \quad \text{--- (2)} \end{aligned}$$


Apply KVL:

$$\begin{aligned} -10 + I_2(10k) + I_1(100k) + 0.7 &= 0 \\ -10 + (\beta + 1) I_B + 20\mu + (I_B + 20\mu)(100k) + 0.7 &= 0 \end{aligned}$$

$$I_B = \checkmark$$


$$I_C = \beta I_B = 0.582 \text{ mA}$$

$$10 - V_C - I_C R_C = 0 \quad V_C = 3.86 = V_{CE}$$

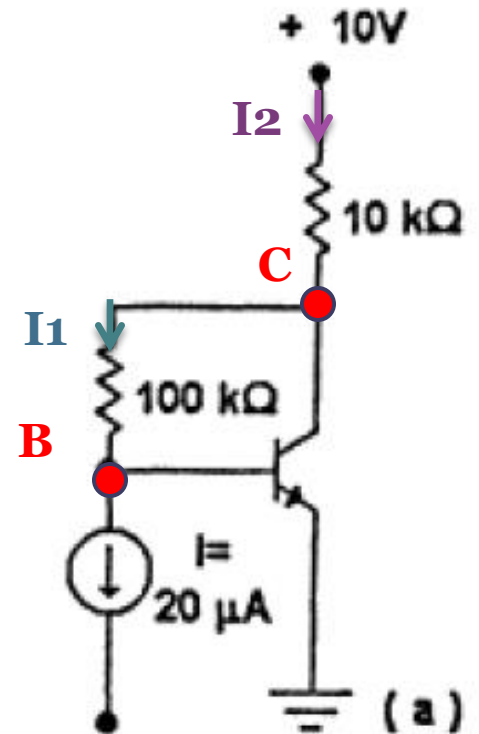


Sheet 6 -P4(b) and (c)

Similar to part (a) but..

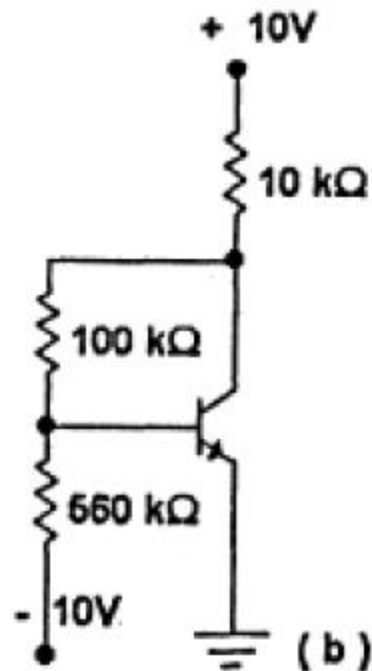

$$I = \frac{(V_B = 0.7) - (-10)}{550k}$$

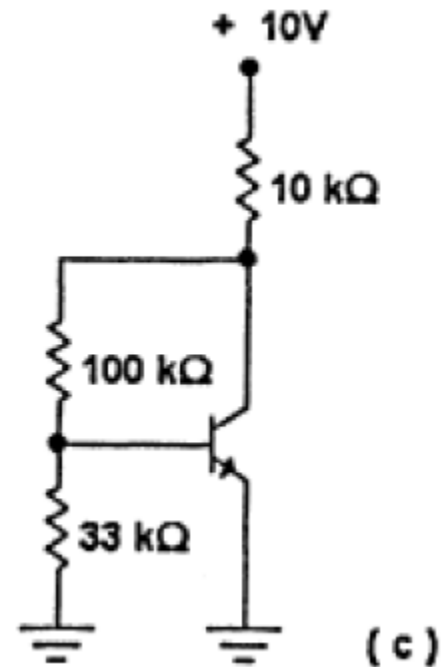

$$I = \frac{(V_B = 0.7)}{33k}$$

Sheet 6 - P4(d)

(d) Loop A:

$$-I_x(68k) + 0.7 + I_E(1k) = 0$$

$$I_x = \frac{0.7 + I_E(1k)}{68k} = 0.7 + \frac{(\beta+1)I_B(1k)}{68k} \quad \text{--- (1)}$$

At node B:

$$\begin{aligned} I_1 &= I_B + I_x = I_B + \frac{0.7 + (\beta+1)I_B(1k)}{68k} \\ &= I_B + (\beta+1)I_B \frac{1k}{68k} + \frac{0.7}{68k} \quad \text{--- (2)} \end{aligned}$$

At node C:

$$\begin{aligned} I_2 &= I_1 + I_C = I_B \left(1 + (\beta+1) \frac{1k}{68k} \right) + \frac{0.7}{68k} + I_C \\ &= I_B \left(1 + (\beta+1) \frac{1k}{68k} \right) + \frac{0.7}{68k} + \beta I_B \quad \text{--- (3)} \end{aligned}$$


Apply KVL

$$-10 - I_2(10k) + I_1(100k) + I_x(68k) = 0$$

Substitute with (1), (2) and (3):



Get I_B
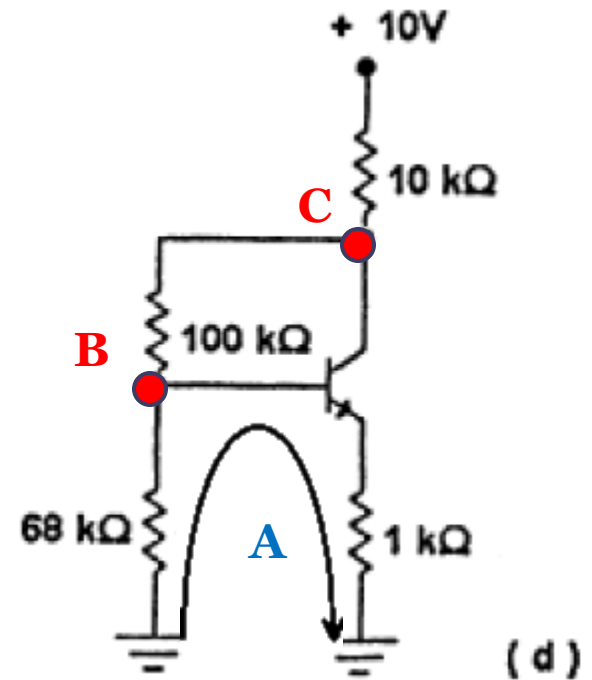
$$I_C = 0.5 \text{ mA} \quad V_{CE} = 3.69 \text{ V}$$



(d)

AC Analysis

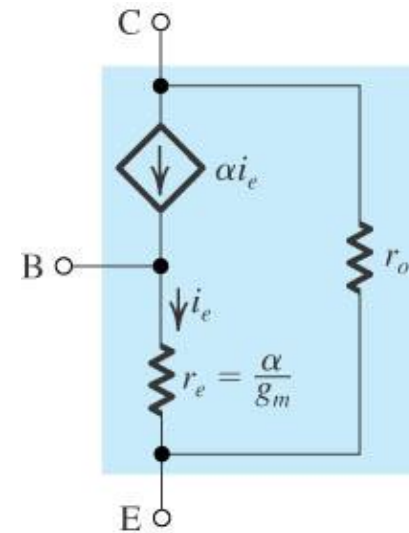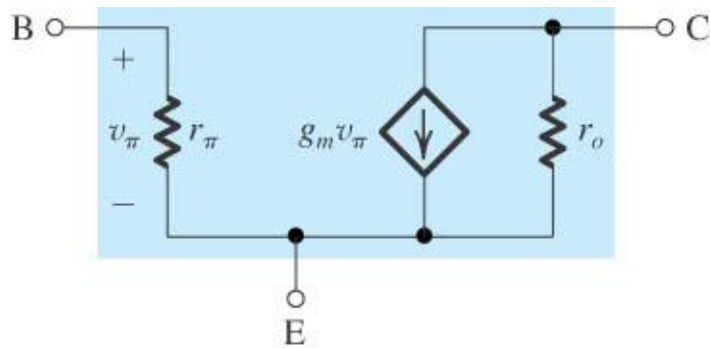

- AC Parameters

- $g_m = \frac{I_c}{V_t=25mV}$

- $r_o = \frac{V_A}{I_c}$

- $r_\pi = \frac{\beta}{g_m}$

- $r_e = \frac{\alpha}{g_m}$

Sheet 7 - P1

DC Analysis

Apply KVL:

$$I_B(100) + 0.7 + I_E(10k) - 10V = 0$$

Substitute with $I_E = (\beta + 1)I_B$

$$I_B(100) + 0.7 + (\beta + 1)I_B(10k) - 10 = 0$$

$$I_B = 9.11 \mu A$$



$$I_C = \beta I_B = 1.36 \text{ mA}$$

AC Parameters:



$$g_m = \frac{I_C}{V_t} = \frac{1.36 \text{ mA}}{25 \text{ mV}} = 0.054$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{150}{0.054} = 2.74 \text{ k}\Omega$$


$$r_o = \frac{g_m V_A}{I_C} = \frac{200}{1.36 \text{ mA}}$$

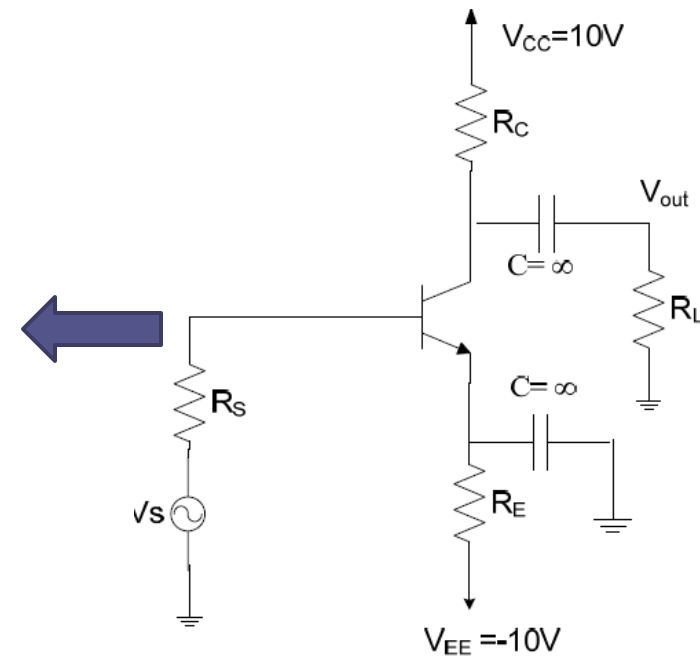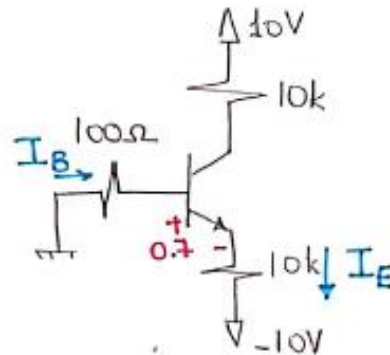

Sheet 7 - P1 (ctd.)

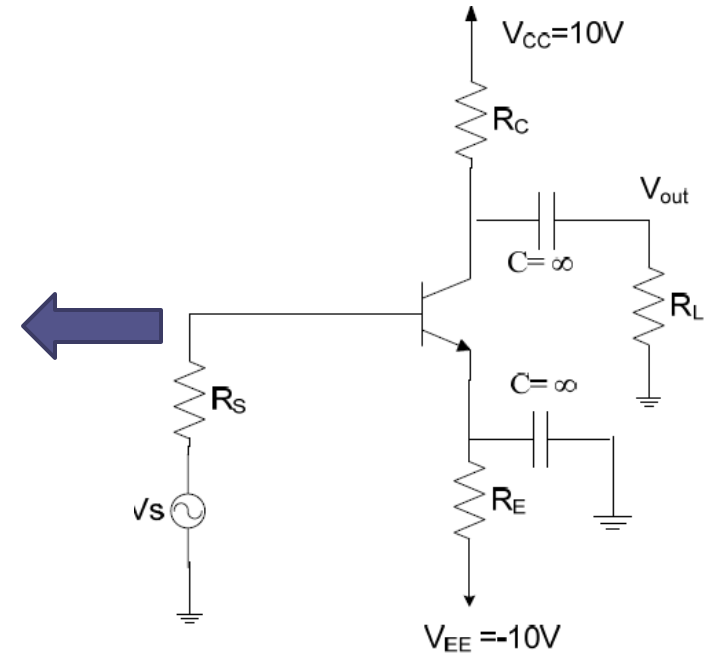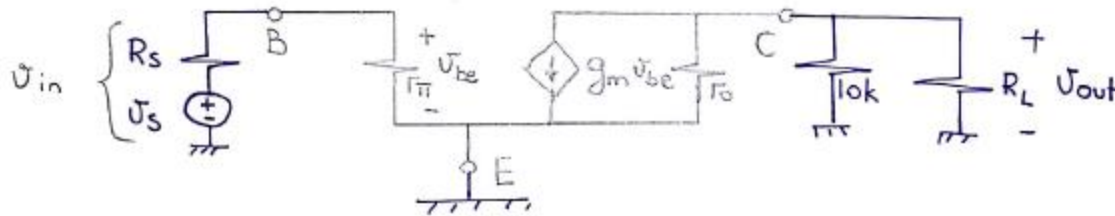

Sheet 7- P1 (ctd.)

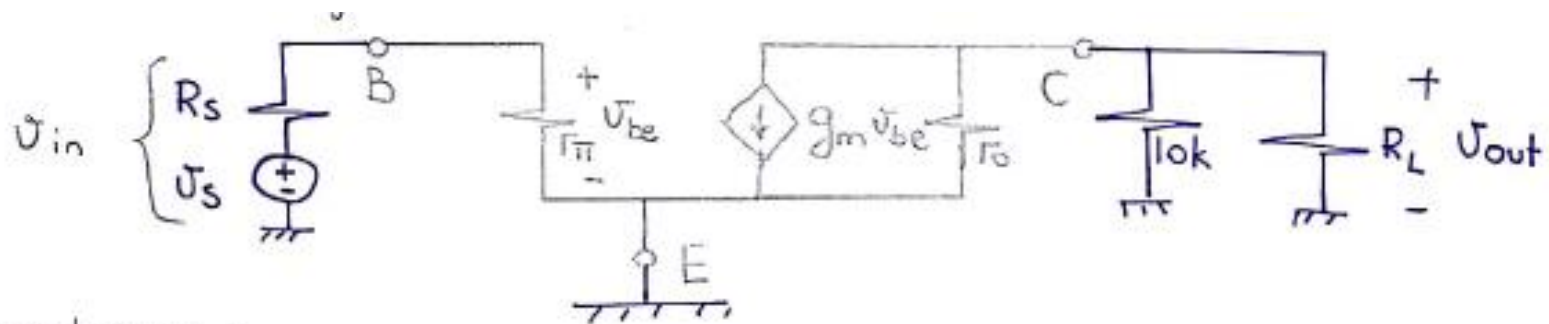

To get v_o/v_s :
Applying voltage divider:

$$v_{be} = \frac{v_s r_{\pi}}{R_s + r_{\pi}} \quad \text{--- (1)}$$

$$v_{out} = -g_m v_{be} (r_o \parallel 10k \parallel R_L) \quad \text{--- (2)}$$

Substitute (1) in (2):

$$v_{out} = -g_m \frac{v_s r_{\pi}}{R_s + r_{\pi}} (r_o \parallel 10k \parallel R_L)$$


$$\frac{v_{out}}{v_s} = -g_m \frac{r_{\pi}}{R_s + r_{\pi}} (r_o \parallel 10k \parallel R_L)$$

$$R_{in} = \frac{v_{in}}{i_{in}} = r_{\pi}$$

$$R_{out} = \frac{v_x}{i_x} \Big|_{v_{in}=0} = 10k \parallel r_o$$

Sheet7 - P2

- DC Analysis
Same as P1.
- AC Analysis

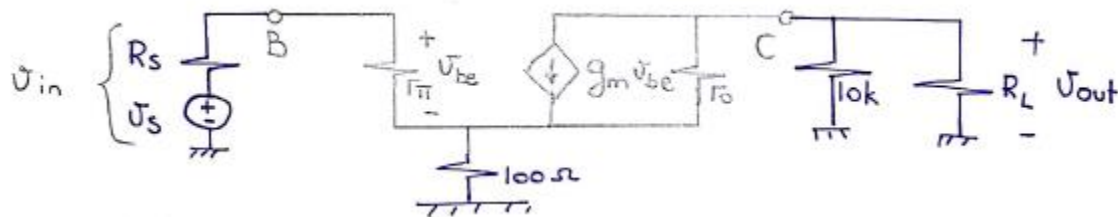

$$U_{be} = \frac{U_s \Gamma_\pi}{R_s + \Gamma_\pi + (\beta + 1)100} \quad \rightarrow \quad U_s = U_{be} \frac{(R_s + \Gamma_\pi + (\beta + 1)100)}{\Gamma_\pi}$$

$$U_o = -g_m U_{be} (r_o \parallel R_L \parallel 10k)$$

$$\frac{U_o}{U_s} = \frac{-g_m U_{be} (r_o \parallel R_L \parallel 10k)}{U_{be} \frac{(R_s + \Gamma_\pi + (\beta + 1)100)}{\Gamma_\pi}}$$

Sheet 7-P3

DC Analysis


$$I_E = 3\text{mA}$$

$$\alpha = \frac{\beta}{\beta + 1} = \frac{150}{151}$$



$$I_C = \alpha I_E =$$

$$g_m = \frac{I_C}{V_t}$$

$$r_{\pi} = \frac{\beta}{g_m}$$

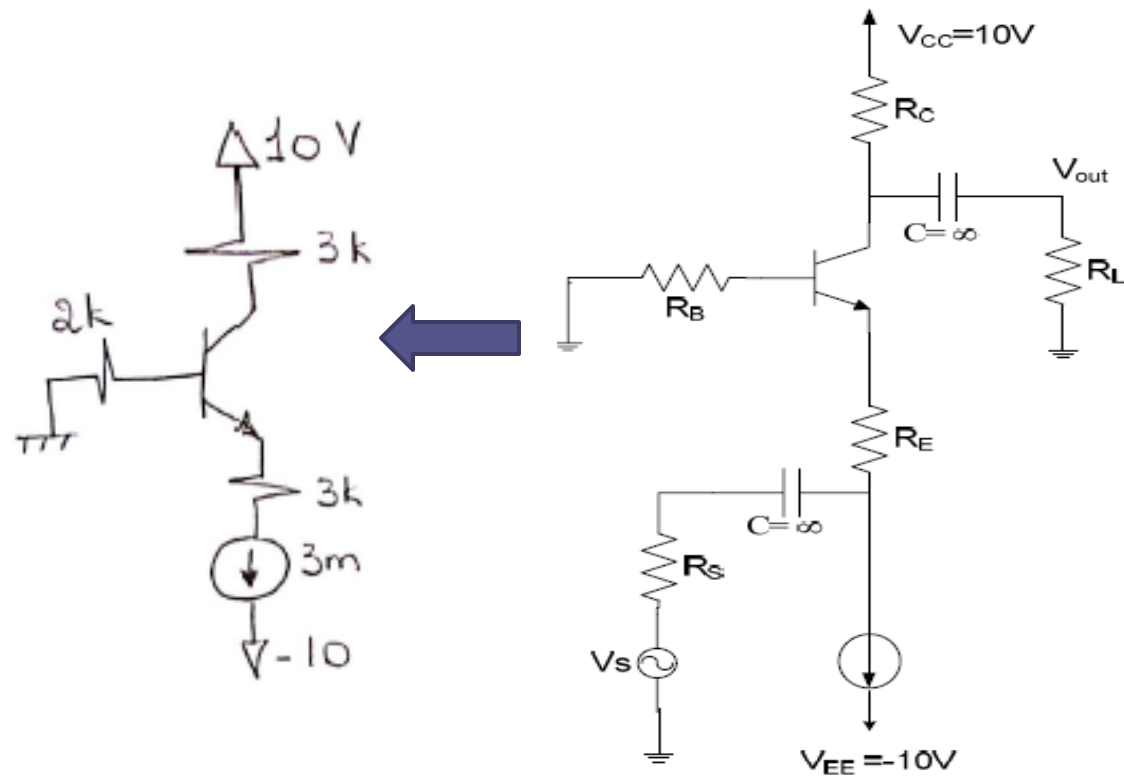

Sheet7-P3(ctd.)

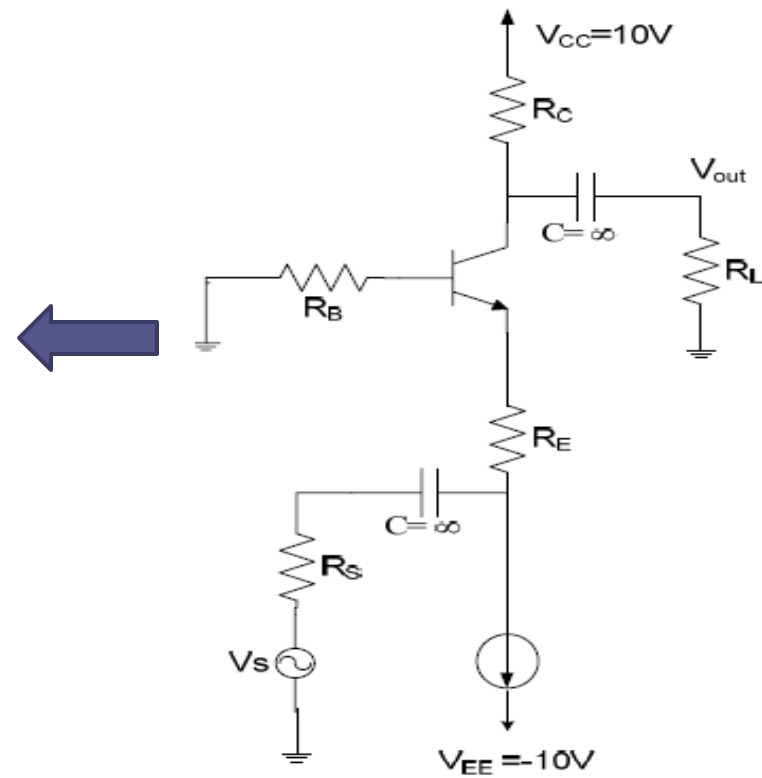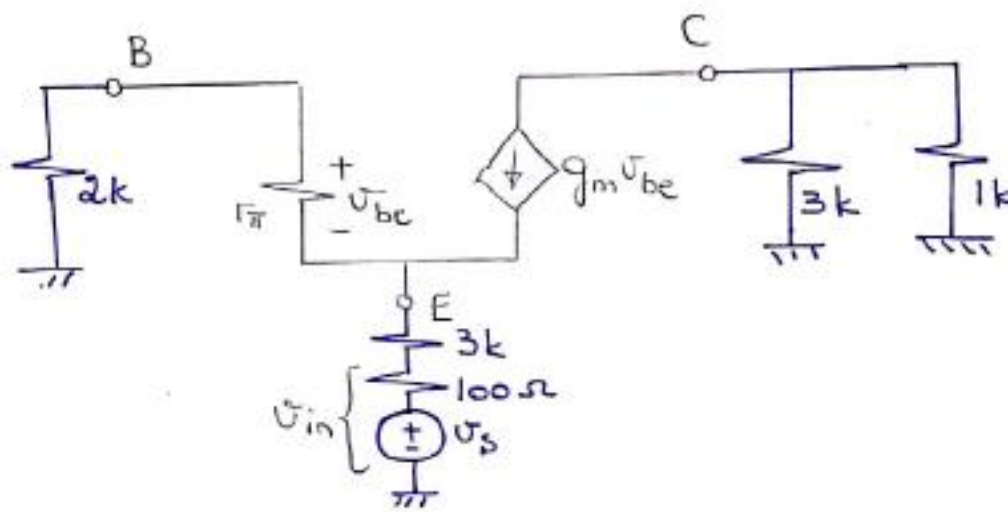

Sheet 7 - P3 (ctd.)

To get v_o/v_s :

Apply KVL:

$$i_b(2k) + i_b(r_{\pi}) + i_e(3k + 100) + v_s = 0$$

$$i_b(2k) + i_b(r_{\pi}) + (\beta + 1)i_b(3k + 100) + v_s = 0$$

$$v_s = -i_b(2k + r_{\pi} + (\beta + 1)(100 + 3k)) \quad \text{--- (1)}$$

$$v_o = -i_c(3k \parallel 1k)$$

$$v_o = -\beta i_b(3k \parallel 1k) \quad \text{--- (2)}$$


Divide (2) by (1):

$$\frac{v_o}{v_s} = \frac{-\beta i_b(3k \parallel 1k)}{-i_b(2k + r_{\pi} + (\beta + 1)(100 + 3k))}$$

To get R_{in} : $i_{in} = -i_e$

$$v_{in} = i_{in}(3k) - i_b(r_{\pi} + 2k) = i_{in}(3k) - (\beta + 1)i_e(r_{\pi} + 2k)$$

$$= i_{in}(3k) + i_{in}(\beta + 1)(r_{\pi} + 2k) \quad \therefore R_{in} = 3k + (\beta + 1)(r_{\pi} + 2k)$$

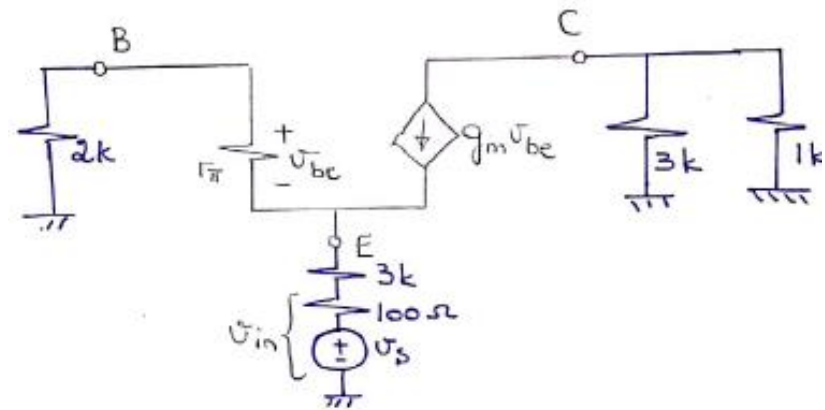

Sheet 7-P4

DC Analysis

$$I_E = 0.1 \text{ mA}$$
$$\alpha = \frac{\beta}{\beta + 1} = \frac{50}{51}$$



$$I_C = \alpha I_E =$$

AC Parameter



$$r_{\pi} = \frac{\beta}{g_m} =$$

$$g_m = \frac{I_C}{V_t} =$$

$$r_o = \frac{V_A}{I_C}$$

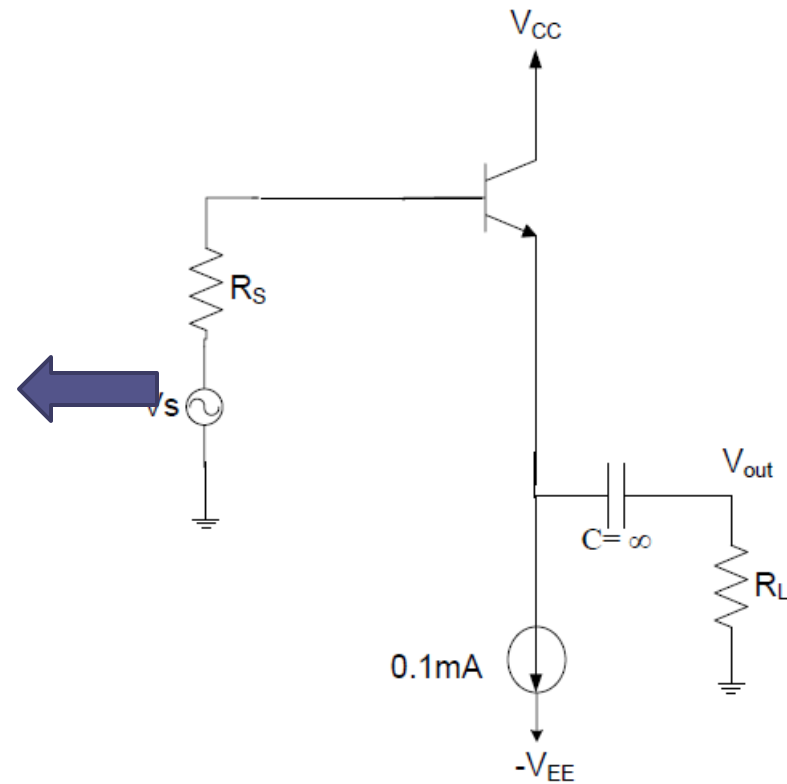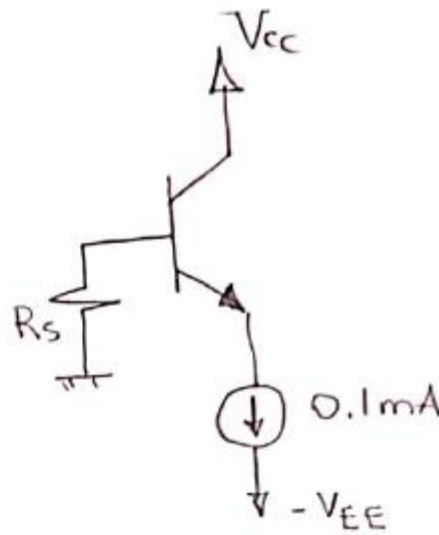

Sheet 7- P4 (ctd.)

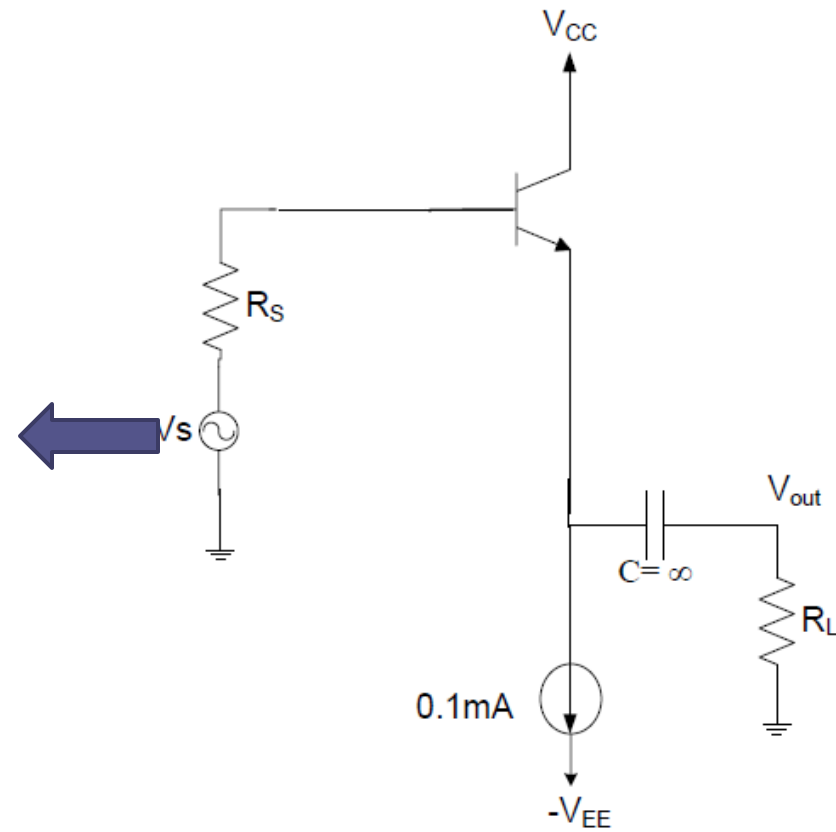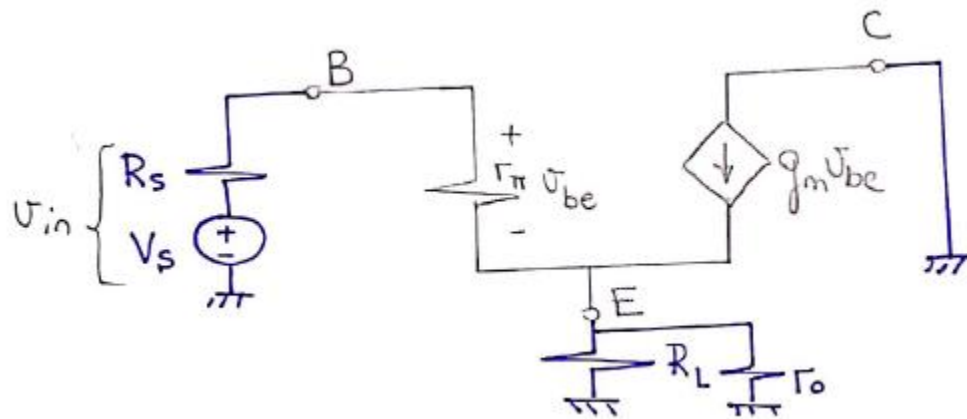

Sheet 7- P4 (ctd.)

To get $\frac{v_o}{v_s}$

$$-v_s + i_b R_s + i_b r_{\pi} + i_e (R_L \parallel r_o) = 0$$

Substitute with $i_e = (\beta + 1) i_b$

$$+v_s = i_b (R_s + r_{\pi} + (\beta + 1) (R_L \parallel r_o)) \quad \text{--- (1)}$$

$$v_o = i_e (R_L \parallel r_o)$$

$$v_o = (\beta + 1) i_b (R_L \parallel r_o) \quad \text{--- (2)}$$

Dividing (2) by (1):


$$\frac{v_o}{v_s} = \frac{(\beta + 1) i_b (R_L \parallel r_o)}{i_b (R_s + r_{\pi} + (\beta + 1) (R_L \parallel r_o))}$$

To get R_{in}

$$i_{in} = i_b$$

$$v_{in} = i_{in} r_{\pi} + i_e (R_L \parallel r_o) = i_{in} r_{\pi} + (\beta + 1) i_b (R_L \parallel r_o) = i_{in} (r_{\pi} + (\beta + 1) (R_L \parallel r_o))$$

$$R_{in} = r_{\pi} + (\beta + 1) (R_L \parallel r_o)$$

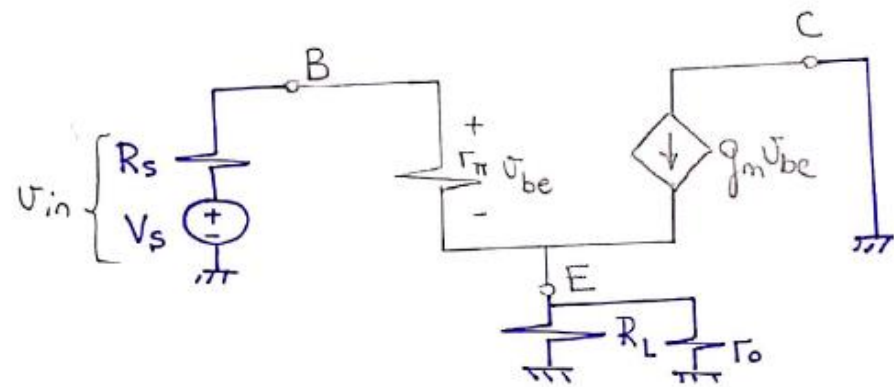

Sheet 7-P3 (T Model)

To get $\frac{v_o}{v_s}$

Apply KVL at loop (A):

$$-v_s - i_e(100 + 3k + r_e) - i_b(2k) = 0$$

$$v_s = -i_e(100 + 3k + r_e) - \frac{i_e}{\beta + 1}(2k) = -i_e \left(100 + 3k + r_e + \frac{2k}{\beta + 1} \right) \quad \text{--- (1)}$$

$$v_o = -\alpha i_e (3k \parallel 1k) \quad \text{--- (2)}$$

Divide (2) by (1):

$$\frac{v_o}{v_s} = \frac{-\alpha (3k \parallel 1k)}{100 + 3k + r_e + \frac{2k}{\beta + 1}}$$

To get R_{in}

$$R_{in} = \frac{v_{in}}{i_{in}} = 3k + r_e + \frac{2k}{\beta + 1}$$

To get R_{out}

$$R_{out} = 3k$$

