

# Device 2 Projects

## Projects

1. Design an amplifier with phase shift  $180^\circ$  between input and output and voltage gain  $A_v=10$  to feed  $R_{load}=10\text{ k}\Omega$ .
2. Design an amplifier with phase shift  $180^\circ$  between input and output and voltage gain  $A_v=13$  to feed  $R_{load}=5\text{ k}\Omega$ .
3. Design an amplifier with phase shift  $180^\circ$  between input and output and voltage gain  $A_v=8$  to feed  $R_{load}=7\text{ k}\Omega$ .
4. Design an amplifier with phase shift  $180^\circ$  between input and output and voltage gain  $A_v=14$  to feed  $R_{load}=20\text{ k}\Omega$ .
5. Design an amplifier with phase shift  $180^\circ$  between input and output and voltage gain  $A_v=6$  to feed  $R_{load}=10\text{ k}\Omega$ .
6. Design an amplifier with phase shift  $180^\circ$  between input and output and voltage gain  $A_v=12$  to feed  $R_{load}=8\text{ k}\Omega$ .
7. Design an amplifier with phase shift  $180^\circ$  between input and output and voltage gain  $A_v=16$  to feed  $R_{load}=15\text{ k}\Omega$ .
8. Design an amplifier with phase shift  $180^\circ$  between input and output and voltage gain  $A_v=7$  to feed  $R_{load}=11\text{ k}\Omega$ .
9. Design an amplifier with phase shift  $180^\circ$  between input and output and voltage gain  $A_v=11$  to feed  $R_{load}=5\text{ k}\Omega$ .
10. Design an amplifier with phase shift  $180^\circ$  between input and output and voltage gain  $A_v=7$  to feed  $R_{load}=10\text{ k}\Omega$ .
11. Design a unity voltage gain amplifier (Source follower) with  $g_m=21\text{ mA/v}$  to feed  $R_{load}=10\text{ k}\Omega$ .
12. Design a unity voltage gain amplifier (Source follower) with  $g_m=22\text{ mA/v}$  to feed  $R_{load}=15\text{ k}\Omega$ .
13. Design a unity voltage gain amplifier (Source follower) with  $g_m=23\text{ mA/v}$  to feed  $R_{load}=12\text{ k}\Omega$ .
14. Design a unity voltage gain amplifier (Source follower) with  $g_m=20\text{ mA/v}$  to feed  $R_{load}=13\text{ k}\Omega$ .
15. Design a unity voltage gain amplifier (Source follower) with  $g_m=22\text{ mA/v}$  to feed  $R_{load}=15\text{ k}\Omega$ .
16. Design a unity voltage gain amplifier (Source follower) with  $g_m=21\text{ mA/v}$  to feed  $R_{load}=10\text{ k}\Omega$ .

17. Design a unity voltage gain amplifier (Source follower) with  $g_m=25 \text{ mA/v}$  to feed  $R_{load}=8 \text{ k}\Omega$ .
18. Design a unity voltage gain amplifier (Source follower) with  $g_m=24 \text{ mA/v}$  and to feed  $R_{load}=12 \text{ k}\Omega$ .
19. Design a unity voltage gain amplifier (Source follower) with  $g_m=21 \text{ mA/v}$  and to feed  $R_{load}=15 \text{ k}\Omega$ .
20. Design a unity voltage gain amplifier (Source follower) with  $g_m=20 \text{ mA/v}$  and to feed  $R_{load}=15 \text{ k}\Omega$ .
21. Design a unity current gain amplifier with gain  $A_v=10$  and  $g_m=20 \text{ mA/v}$  to feed  $R_{load}=10 \text{ k}\Omega$ .
22. Design a unity current gain amplifier with gain  $A_v=12$  and  $g_m=20 \text{ mA/v}$  to feed  $R_{load}=8 \text{ k}\Omega$ .
23. Design a unity current gain amplifier with gain  $A_v=14$  and  $g_m=20 \text{ mA/v}$  to feed  $R_{load}=10 \text{ k}\Omega$ .
24. Design a unity current gain amplifier with gain  $A_v=15$  and  $g_m=20 \text{ mA/v}$  to feed  $R_{load}=7 \text{ k}\Omega$ .
25. Design a unity current gain amplifier with gain  $A_v=16$  and  $g_m=20 \text{ mA/v}$  to feed  $R_{load}=10 \text{ k}\Omega$ .
26. Design a unity current gain amplifier with gain  $A_v=8$  and  $g_m=20 \text{ mA/v}$  to feed  $R_{load}=15 \text{ k}\Omega$ .
27. Design a unity current gain amplifier with gain  $A_v=7$  and  $g_m=22 \text{ mA/v}$  to feed  $R_{load}=12 \text{ k}\Omega$ .
28. Design a unity current gain amplifier with gain  $A_v=11$  and  $g_m=20 \text{ mA/v}$  to feed  $R_{load}=15 \text{ k}\Omega$ .
29. Design a unity current gain amplifier with gain  $A_v=9$  and  $g_m=20 \text{ mA/v}$  to feed  $R_{load}=15 \text{ k}\Omega$ .
30. Design a unity current gain amplifier with gain  $A_v=5$  and  $g_m=20 \text{ mA/v}$  to feed  $R_{load}=14 \text{ k}\Omega$ .

**Students are required to accomplish the following:**

- A maximum of 2 students are allowed per project.
- Reports containing detailed design steps and ORCAD simulations are required.