



COLLEGE OF ENGINEERING & TECHNOLOGY

Department: Electronics and Communications

Lecturer : Dr.Saleh Eissa

Course : Analog Signal Processing

Course Code: EC434

Problem Set 1

P1. For the circuit shown in the fig.1 below, sketch the capacitor voltage $V_c(t)$ as well as the voltages and currents through both resistors with time if the switch is first set to position 1 and then turned to position 2 after $10 \mu\text{s}$.

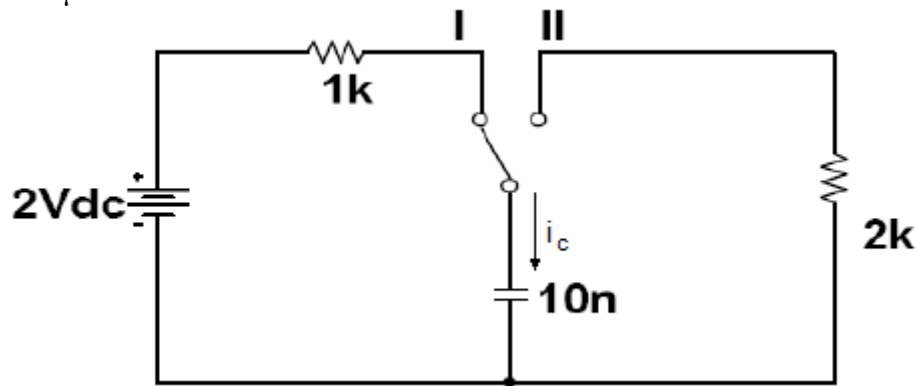


Fig.1

P2. For the RC circuit shown in the fig.2, if the switch is closed at $t = 0$, calculate:

- The initial slope $V_c(t)$
- The rise time
- Total charge time
- The time taken to reach 63.2% of the steady state value

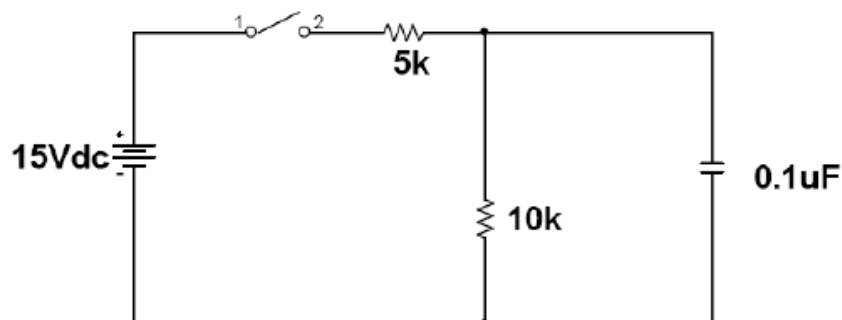


Fig.2

P3. The switch in the fig.3 is closed at $t = 0$ and then reopened after $1 \mu\text{s}$. Sketch $V_c(t)$ as well as the switch current i_{sw} during both intervals.

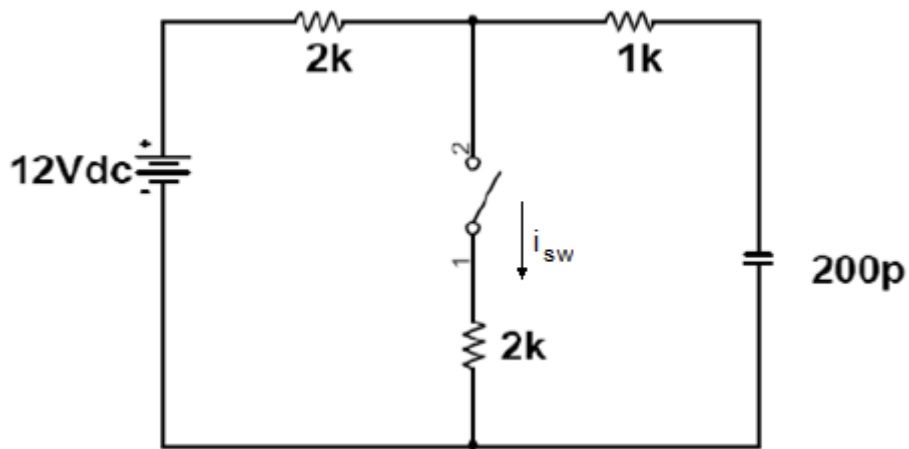


Fig.3

P4. Given that at $t=0$, switch 1 is closed and switch 2 is opened. At $V_{out}=10\text{V}$, switch 2 is closed. Calculate and sketch $V_{out}(t)$, $V_c(t)$ and $i_c(t)$ for the circuit in fig.4 .

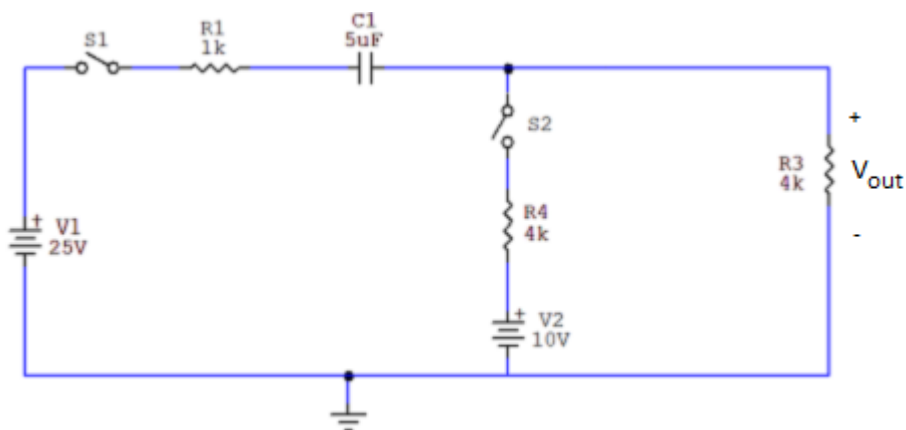


Fig.4

P5. Calculate and sketch the capacitor voltage in the circuit from $t=0$ to $t=20\text{ms}$ when a square wave of $f=125\text{Hz}$ and $E=20\text{V}$ is applied at the input of the circuit in fig.5 if $R=3.3\text{k}\Omega$ and $C=1\mu\text{F}$. Also, calculate the maximum and minimum levels at which the capacitor voltage will settle.

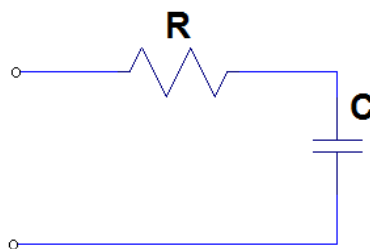


Fig.5

- P6. For the circuit in fig.5, a square wave is applied at the input with $E=10V$. Calculate the maximum and minimum settled capacitor voltage if $R=1K\Omega$ and $C=1\mu F$ for:
- $f=500Hz$
 - $f=5KHz$
 - $f=50Hz$
- Deduce the condition for which the circuit will operate as an integrator.

- P7. The circuit shown in fig.5 have the following pulse inputs applied:
- $E=10V, PW=1ms$
 - $E=10V, PW=2ms$
 - $E=20V, PW=1ms$
- If $R=10K\Omega$ and $C=20\mu F$, calculate the level of V_c at the end of each pulse. The initial charge on C is assumed to be zero. Show the $V_c \propto PA \times PW$. (PA = Pulse Amplitude, PW =Pulse Width)

- P8. For the circuit shown in fig.6, a pulse is applied at the input with $E=10V$, calculate and sketch $V_c(t)$ if $R=1K\Omega$ and $C=1\mu F$ for:
- $PW=1msec$
 - $PW=0.1msec$
 - $PW=10msec$
- Deduce the condition for which the circuit will operate as a differentiator.

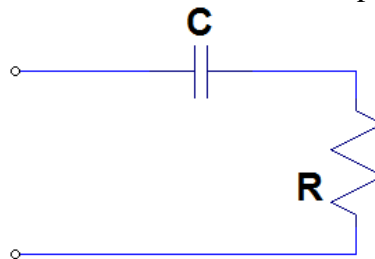


Fig.6