



# COLLEGE OF ENGINEERING & TECHNOLOGY

Department: Electronics and Communications

Lecturer : Dr.Saleh Eissa

Course : Analog Signal Processing

Course Code: EC434

## Problem Set 2

P1. For the Low Pass Filter (LPF) shown in figure 1, derive the transfer function and sketch its magnitude transfer function.

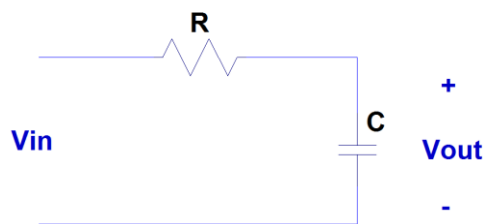


Fig.1

P2. For the High Pass Filter (HPF) shown in figure 2, derive the transfer function and sketch its magnitude transfer function.

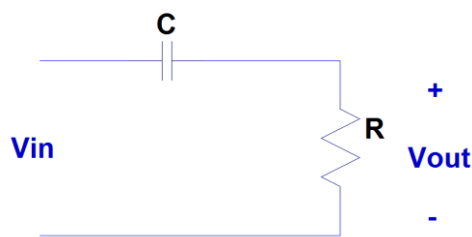


Fig.2

P3. For the LPF shown in figure 3, show that at  $\omega = \omega_n$  the magnitude response is 3dB below the value at DC for  $Q = 1/\sqrt{2}$ .

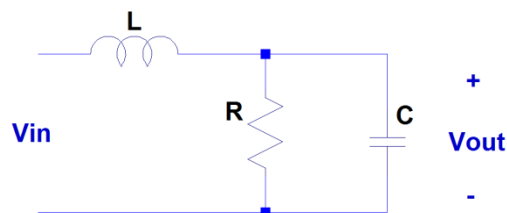


Fig.3

P4. For a maximally flat passive 2<sup>nd</sup> order LPF shown in figure 3, design for a cut-off frequency of 10k. Set R=10k.

P5. Design a 2<sup>nd</sup> order Low Pass Filter as shown in figure 3, for  $P_{1,2} = -150 \times 10^3 + j593.7 \times 10^3$ .

P6. Modify figure 1 to get a High Pass Filter. Derive the transfer function. Sketch its amplitude response for R=10K $\Omega$ , L=3.6mH and C=500pF.

P7. Give the transfer function for the 2<sup>nd</sup> order Band Pass Filter shown in figure 4 it the center frequency is  $10^5$  r/s and the 3dB-bandwidth is  $10^3$  r/s.

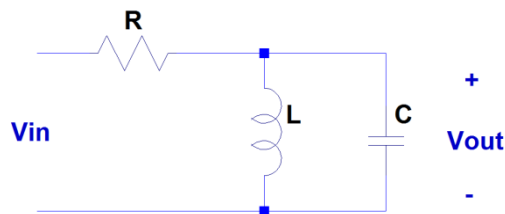


Fig.2