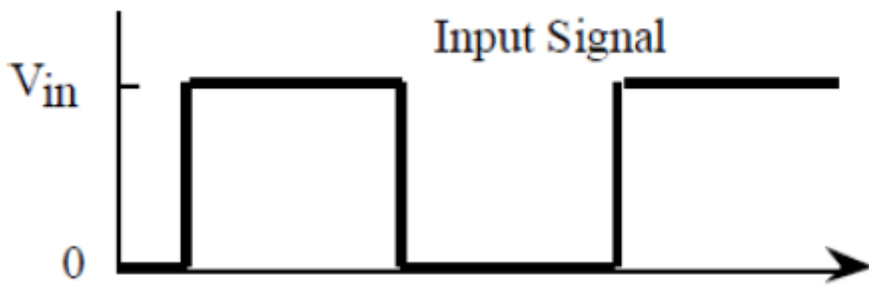


Problems:

[1]a)-----




b)-----



[2]a) -----



b) -----

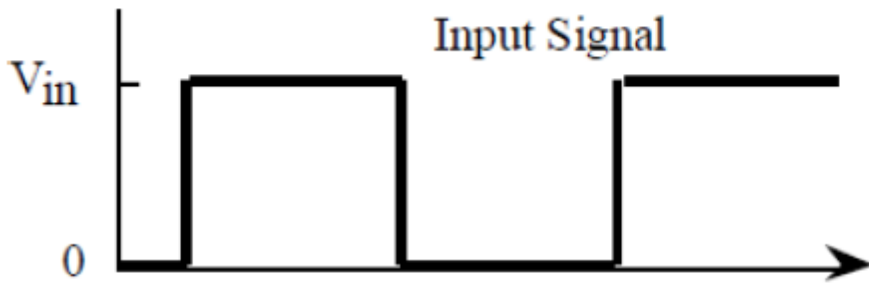

Measurements with sine waves

1)-----

2)-----

Next study the high-pass and low-pass filters

1)-----



3)-----

Measurements with Square Waves



For integrator:



Record frequency:

For differentiator:



Record frequency: