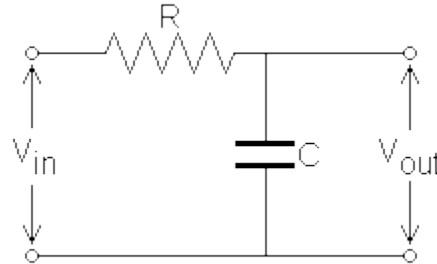


EC434: ASP Lab 1

Passive Filters: RC Integrator Circuit



Objective


- Studying the RC integrator circuit output.
- Observing the relation between the pulse width and τ .

Theory


- Time Constant: the time that it takes for the capacitor to reach 63% of the EMF (V_{in}) value during charging.

$$\tau = R.C$$

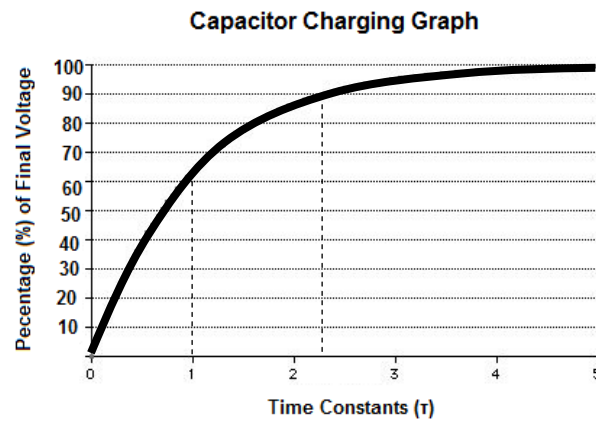- The RC circuit above acts as passive LPF at low frequencies and an integrator at high frequencies (i.e. Pulse width = $\frac{\tau}{10} = \frac{RC}{10}$)



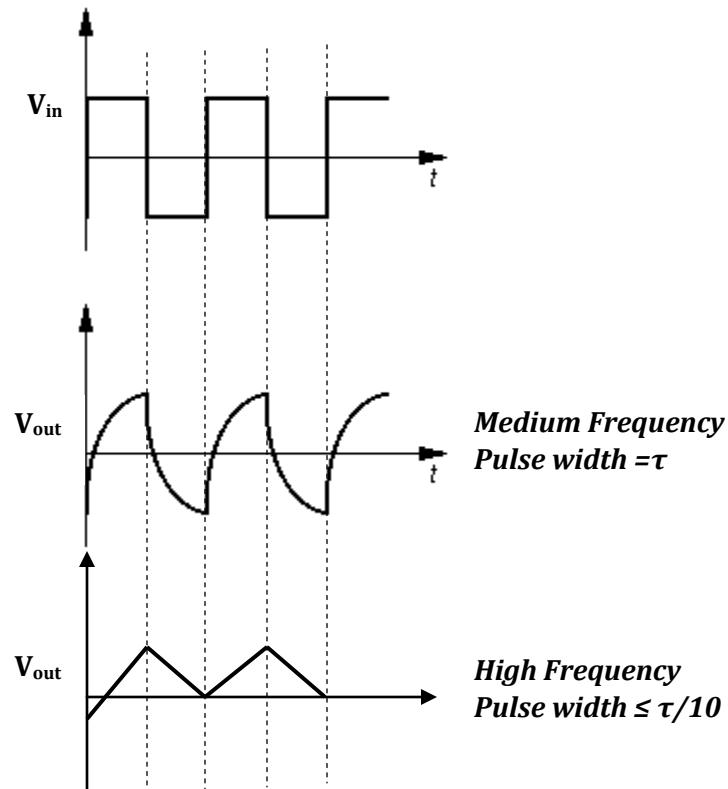- When the input is a square wave, the output of the integrator should be a triangular function.




Design Steps

1. Assuming the cycle time is 1ms, calculate the input wave frequency, then input a square wave of the same frequency to the circuit (duty cycle = 50%; pulse width = $T/2$).
2. Using the integrator condition below, design the RC circuit choosing suitable values for R and C.


$$\text{Pulse width} = \tau / 10 = RC / 10$$

3. Compare and Draw the relation between the output and input voltages.
4. Comment on your results.
5. Assignment: Prepare an ORCAD lab report for the RC integrator and differentiator circuits.

Using ORCAD

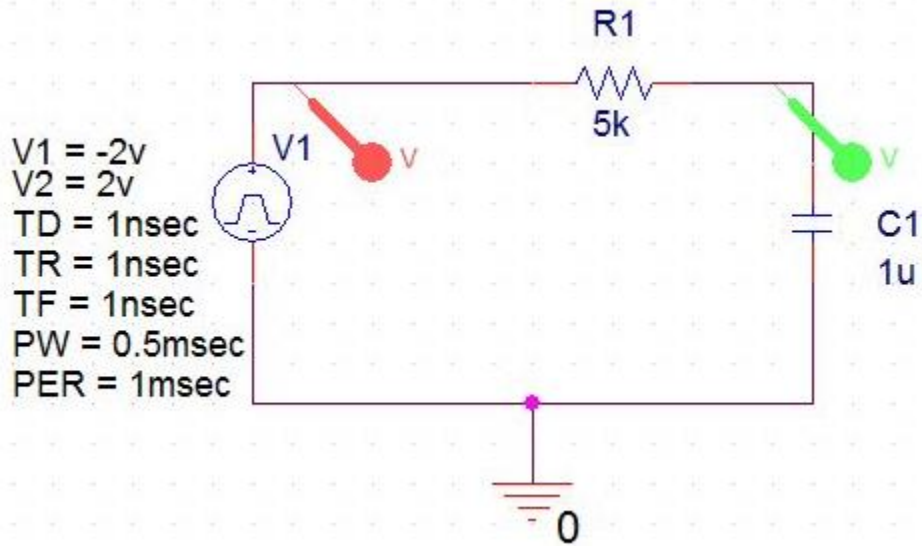

ORCAD results

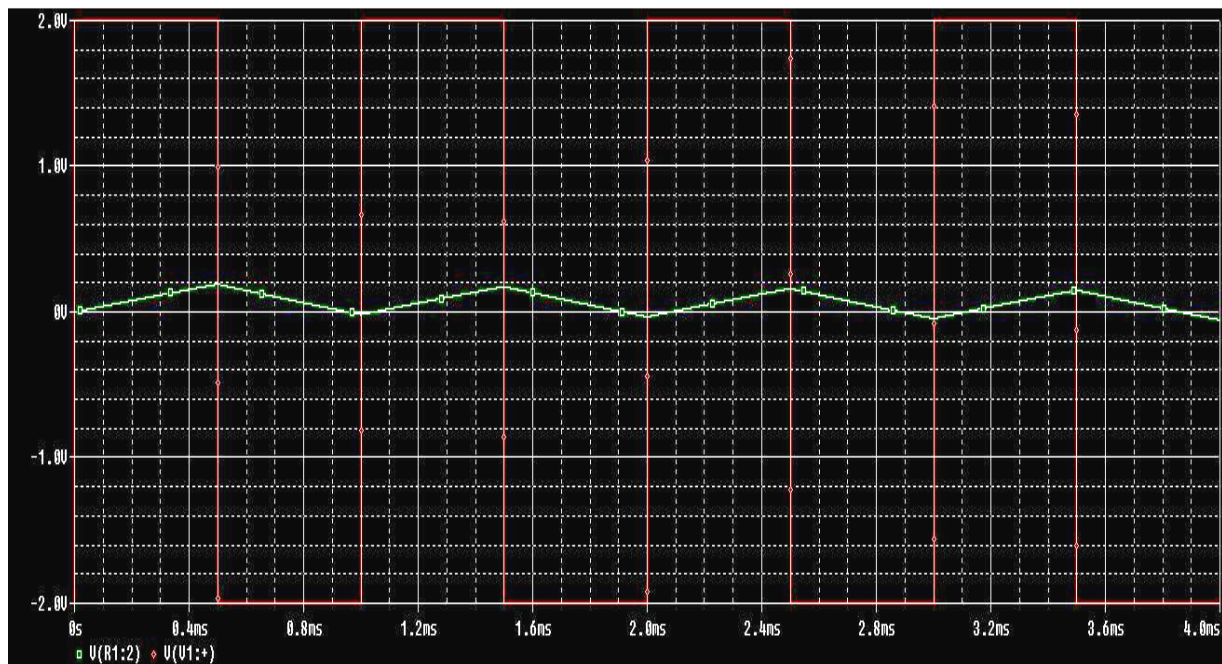

Next Lab: RC Differentiator Circuit