

COLLEGE OF ENGINEERING & TECHNOLOGY

Department: Electronics and Communications Engineering

Instructors: Dr. Amr Bayoumi, Dr. Saleh Eissa

Course Title: Modern Electronics Circuits

Course No.: EC560 Assignment 4

Date: March 16, 2016



Noise, LNA, Mixers

Note: For all transistors:

- Use the 1st Edition of the textbook
- Use -N-MOSFETs with the BSIM model in page 80-82
- Use $W = 100\mu\text{m}$, $L_{\text{gate}} = 0.5\mu\text{m}$, Source and drain dimensions are $W \times 2\mu\text{m}$
- Assume that in short channel, $I_{\text{ds}} = I_{\text{dso}}(1 + V_{\text{ds}}/V_{\text{A}})$, $V_{\text{A}} = 10\text{V}$, where I_{dso} is current at velocity saturation, assuming no short channel effects on V_{to} or L_{eff} .
- Use velocity saturation and channel length modulation for short channel at high V_{ds}
- Assume $V_{\text{gs}} = 3.3\text{V}$, $V_{\text{ds}} = 5\text{V}$ for all problems. You should start by finding, g_m , g_d , C_{gs} , C_{gd} . Ignore C_{sb} , but keep C_{sd} . Ignore RE

Question 1 :

Solve examples 1 and 2 p. 261-262, 1st Edition .

Question 2 :

Design a source degenerate inductance-based resistance which has a value of 50 Ohm at 1GHz.

Question 3 :

Draw the small signal ac model of the MOSFET, with noise source included. For the transistor in the header, use eqn. (5) p. 246, to find the values of the noise sources

Question 4 :

Design a power-optimized single-ended LNA to meet the following specifications (you are required to put current mirror biasing in your design):

- $\omega_{\text{resonance}} = 2 \text{ Grad/sec}$, $R_{\text{source}} = 50 \text{ Ohm}$.

Question 5 :

Design a square-law downconversion mixer with $f_{\text{RF}} = 1\text{GHz}$, $f_{\text{out}} = 100\text{MHz}$. Use a different channel length (L) for the MOSFET. Make sure your design is not sensitive to parasitics or output loads. (Hint. Consider cascode and source follower designs)

Question 6 :

Design a single-balanced mixer, like the one in Fig. 12.9, to meet the same requirements in Q5. Use $R_s = 50\text{Ohm}$. Match L_s to this R_s (although this is might not be the best option)

Question 7 :

Design a double-balanced active mixer, using Fig. 12.10, 12.11 (322-323) to meet requirements of Q5. R_s is 50 Ohm for each pair of the differential RF.