



Course: Electronics I

Course Code: EC238

Lecturer: Dr. Amr Bayoumi


Tutors: Eng. Sherry Heshmat

## Sheet (5)


### Question (1)

For the figure shown find

- 1)  $I_i$
- 2)  $V_L$
- 3)  $A_v$

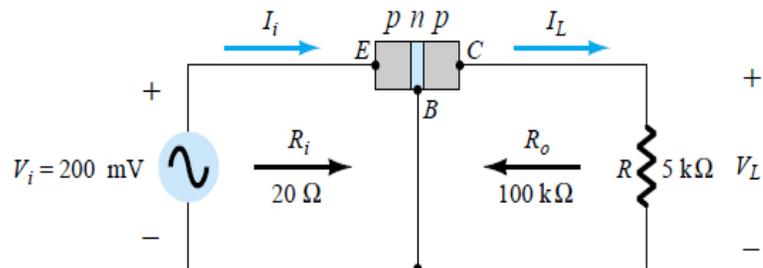

### Question (2)

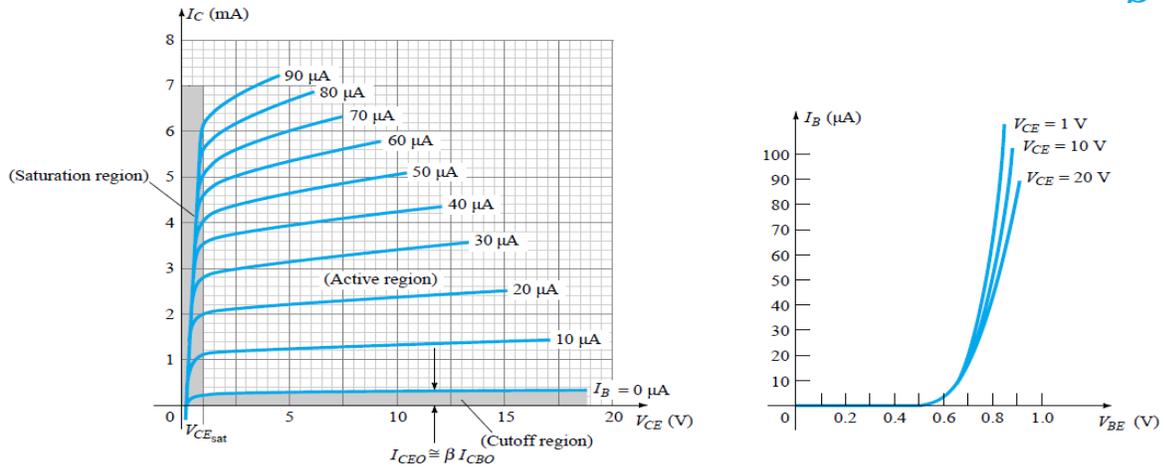

From the figure shown Determine:

- a)  $I_c$  at  $I_B = 30\mu A$  and  $V_{CE} = 10 V$
- b)  $I_c$  at  $V_{BE} = 0.7 v$  and  $V_{CE} = 15 V$
- c)  $\beta_{dc}$  at  $I_B = 10\mu A$  and  $V_{CE} = 10 V$