

# •Lecture 2

## Semiconductor Diodes



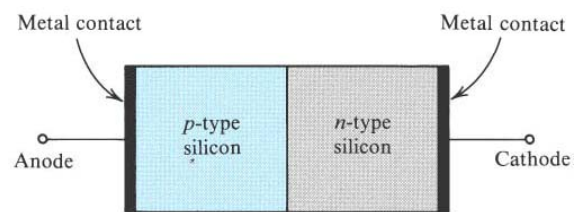


Figure 3.39 Simplified physical structure of the junction diode. (Actual geometries are given in Appendix A.)

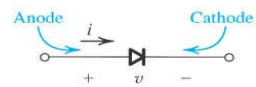


(a)

Circuit  
symbol

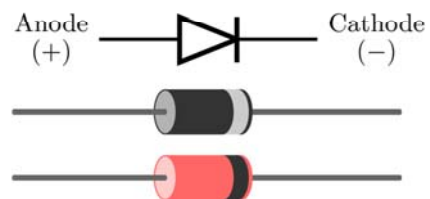

## Diodes

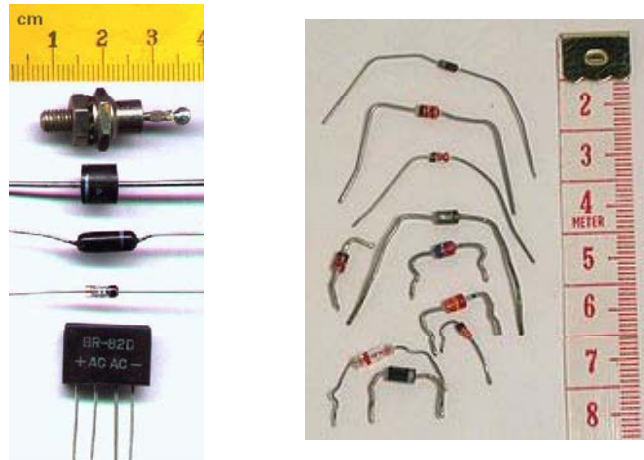

Several types of diodes. The scale is centimeters

## The $i-v$ characteristic of a silicon diode.

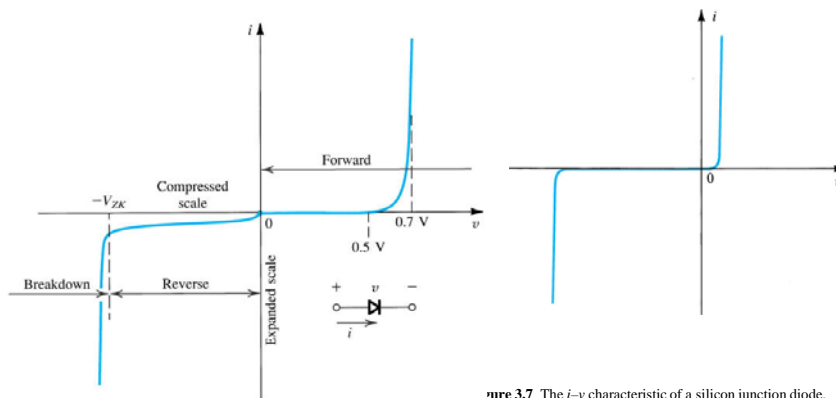


Figure 3.7 The  $i-v$  characteristic of a silicon junction diode.

Figure 3.8 The diode  $i-v$  relationship with some scales expanded and others compressed in order to reveal details.

## The $i-v$ characteristic of a silicon diode.

- **The Forward-Bias region:-**

- In the forward region the  $i-v$  relationship is closely approximated by.....

$$i = I_s (e^{kv/T_k} - 1)$$

- $I_s$  .....the reverse saturation current ( scale current)
  - $K$  = Boltzmann's constant =  $1.38 \times 10^{-23}$  joules / kelvin
  - $T_k$  = the absolute temperature in kelvins =  $273 + \text{temperature in } ^\circ\text{C}$

## The $i-v$ characteristic of a silicon diode.


- **The Reverse-Bias region:-**

- The exponential term becomes negligibly small compared to unity, and the diode current becomes.....

$$i \approx -I_s$$

- That is, the current in the reverse direction is constant and equal to  $I_s$  which tends to zero.
- **The Breakdown Region:-**
- The breakdown region is entered when the magnitude of the reverse voltage exceeds a threshold value that is specific to the particular diode, called the breakdown voltage.

## Ideal Diode

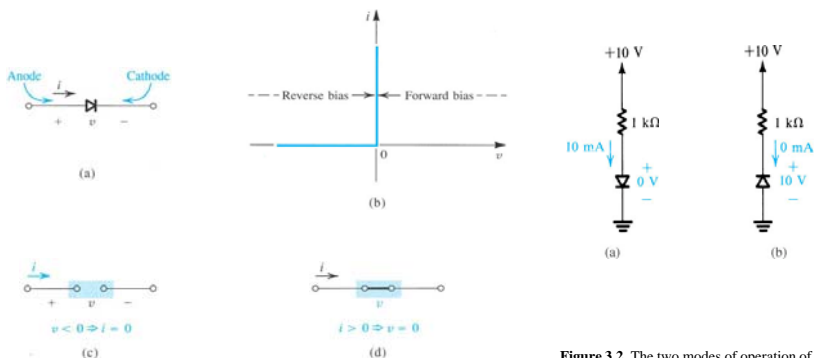


**Figure 3.1** The ideal diode: (a) diode circuit symbol; (b)  $i-v$  characteristic; (c) equivalent circuit in the reverse direction; (d) equivalent circuit in the forward direction.

**Figure 3.2** The two modes of operation of ideal diodes and the use of an external circuit to limit the forward current (a) and the reverse voltage (b).


## Modeling the diode forward characteristic

### The Piecewise-linear Model

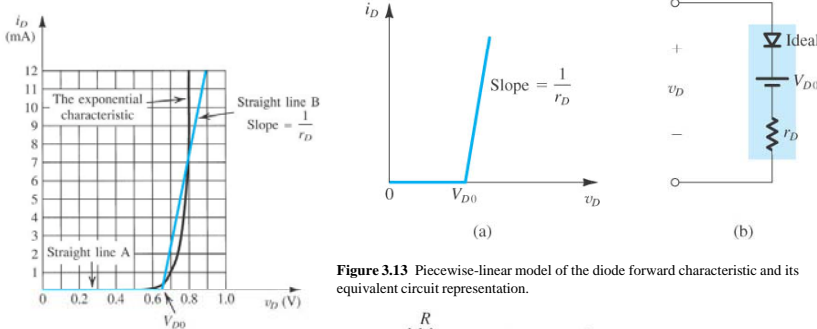

**Figure 3.12** Approximating the diode forward characteristic with two straight lines: the piecewise-linear model.

**Figure 3.13** Piecewise-linear model of the diode forward characteristic and its equivalent circuit representation.

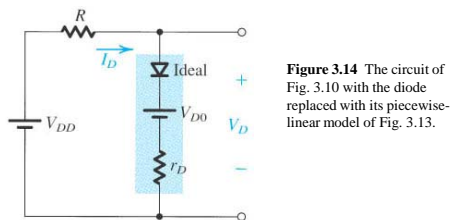


**Figure 3.14** The circuit of Fig. 3.10 with the diode replaced by its piecewise-linear model of Fig. 3.13.
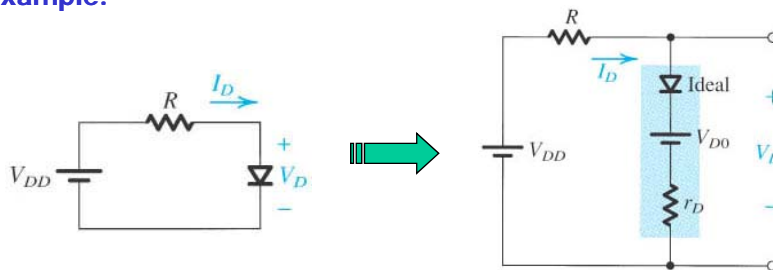
## Modeling the diode forward characteristic

### The Piecewise-linear Model

Example:



Given:  $V_{DD} = 5V$ ,  $V_{D0} = 0.65V$ ,  $r_D = 20\Omega$ ,  $R = 1K\Omega$


Thus 
$$I_D = \frac{5 - 0.65}{1 + 0.02} = 4.26mA$$

$$V_D = V_{D0} + I_D r_D$$


$$= 0.65 + 4.26 \times 0.02 = 0.735V$$

## Modeling the diode forward characteristic

### The Constant-voltage-drop Model

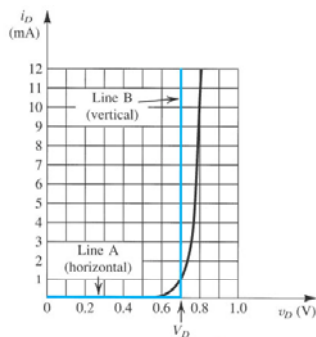

**Figure 3.15** Development of the constant-voltage-drop model of the diode forward characteristics. A vertical straight line (B) is used to approximate the fast-rising exponential. Observe that this simple model predicts  $V_D$  to within  $\pm 0.1V$  over the current range of 0.1 mA to 10 mA.

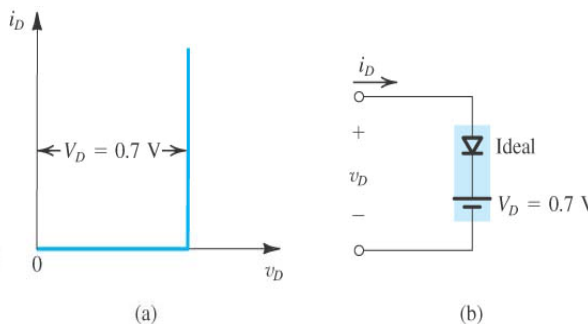

**Figure 3.16** The constant-voltage-drop model of the diode forward characteristics and its equivalent-circuit representation.

## Modeling the diode forward characteristic

### The Ideal Diode Model

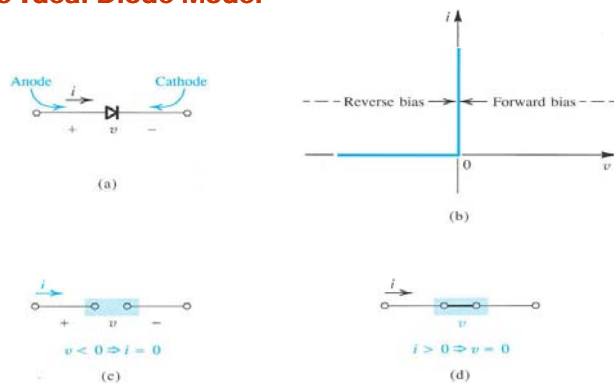


Figure 3.1 The ideal diode: (a) diode circuit symbol; (b)  $i-v$  characteristic; (c) equivalent circuit in the reverse direction; (d) equivalent circuit in the forward direction.

## Operation in The reverse Breakdown Region- Zener Diodes

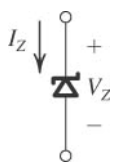


Figure 3.20 Circuit symbol for a zener diode.

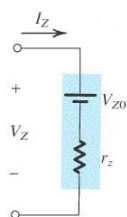


Figure 3.22 Model for the zener diode.


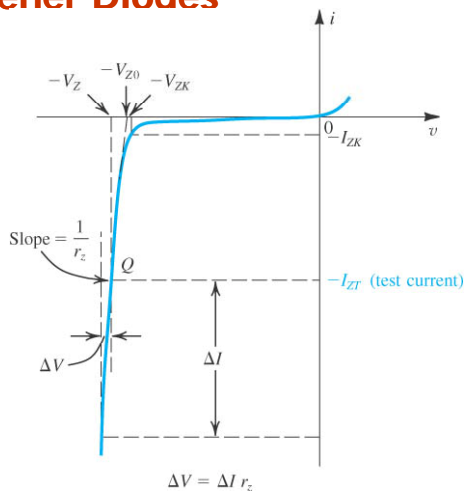


Figure 3.21 The diode  $i-v$  characteristic with the breakdown region shown in some detail.

## Operation in The reverse Breakdown Region- Zener Diodes



**Example: Find  $I$  ?**

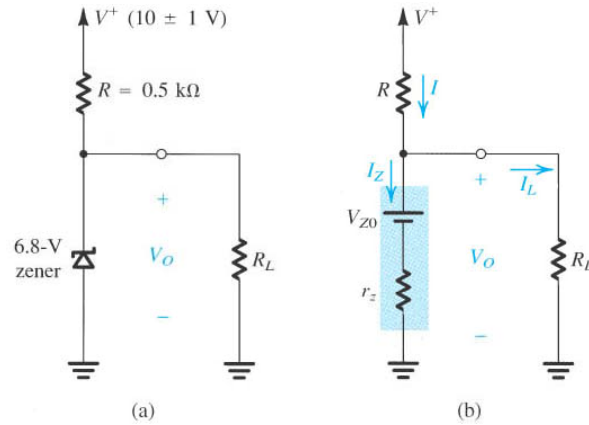

**Figure 3.23** (a) Circuit for Example 3.8. (b) The circuit with the zener diode replaced with its equivalent circuit model.

## Special Diode Types

### Light-Emitting Diodes (LEDs)

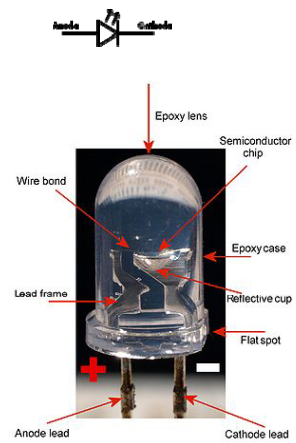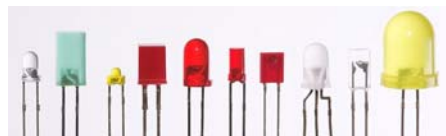

### Series Diode Configurations with DC Inputs

- For the series diode configurations that will be considered, the first thing to do is to determine the state of the diode “ON” or “OFF”
- In the “ON” state, the diode may be replaced with a constant voltage drop (0.3, or 0.7) or a short circuit based on the model of approximation.
- In the OFF state, diode is replaced with an open circuit.
- Example 2.8, and Example 2.9

### Parallel and Series Parallel Configurations

- The method applied before can be extended to the analysis of parallel and series-parallel configurations where more than one diode is contained in the circuit, simply match the sequential series steps applied to series diode configurations

– Example 2.12 and Example 2.15



# Diode Applications

## Diodes Applications: Rectifier Circuits

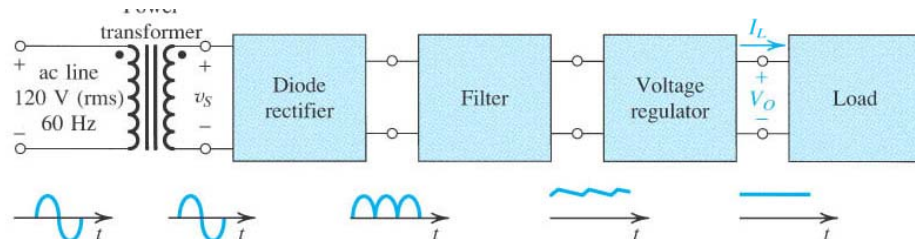


Figure 3.24 Block diagram of a dc power supply.

### The Half-Wave Rectifier

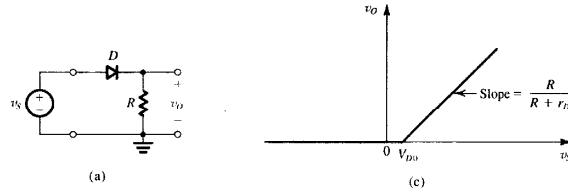


Figure 3.25 (a) Half-wave rectifier. (b) Equivalent circuit of the half-wave rectifier with the diode replaced with its battery-plus-resistance model.

$$v_o = 0, \quad v_s < V_{D0}$$

$$v_o = \frac{R}{R + r_D} v_s - V_{D0} \frac{R}{R + r_D}, \quad v_s \geq V_{D0}$$

$$v_o \approx v_s - V_{D0}$$

### The Half-Wave Rectifier

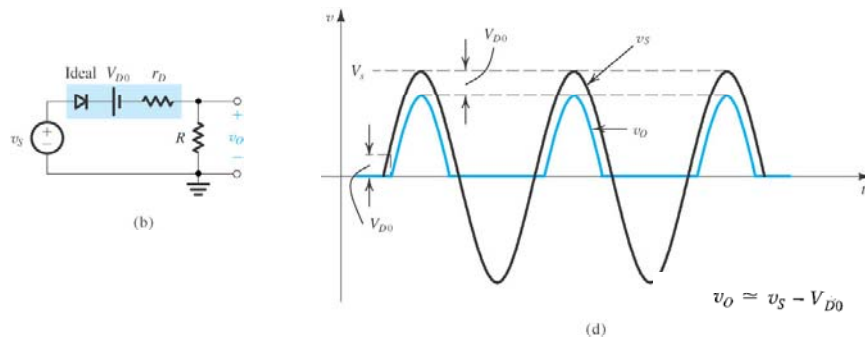


Figure 3.25. (c) Transfer characteristic of the rectifier circuit. (d) Input and output waveforms, assuming that  $r_D \ll R$ .

The Peak Inverse Voltage PIV =  $v_s$

### The Full Wave Rectifier

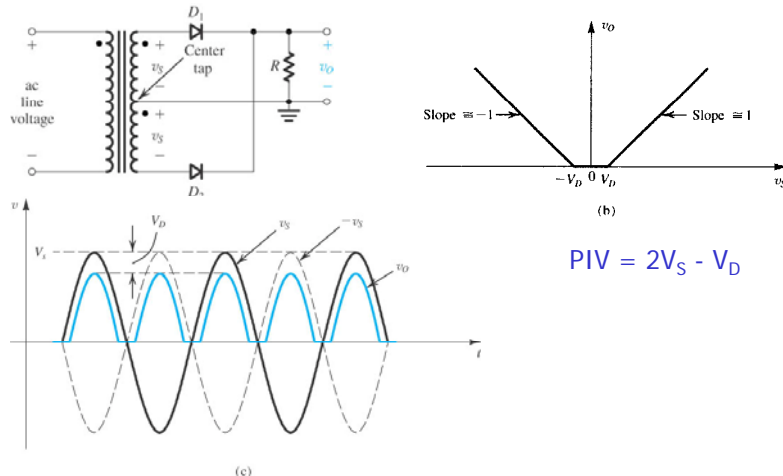


Figure 3.26 Full-wave rectifier utilizing a transformer with a center tapped secondary winding: (a) circuit; (b) transfer characteristics assuming a constant-voltage-drop model for the diodes; (c) input and output wave forms.

### The Bridge Rectifier


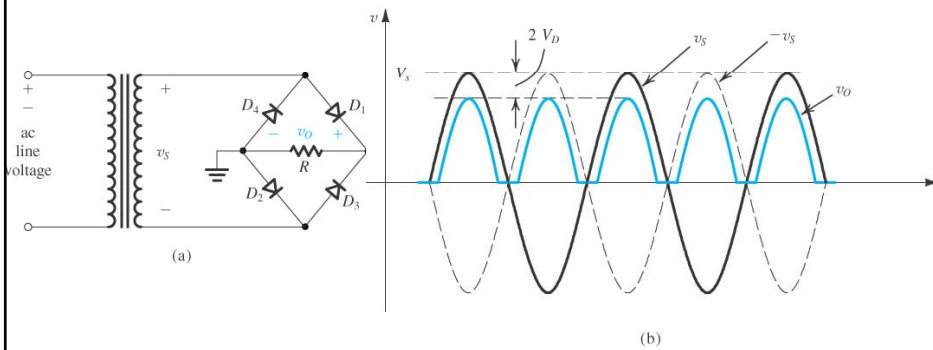


Figure 3.27 The bridge rectifier: (a) circuit; (b) input and output waveforms.


$$PIV = V_S - 2V_D + V_D = V_S - V_D$$

### The rectifier with a filter capacitor

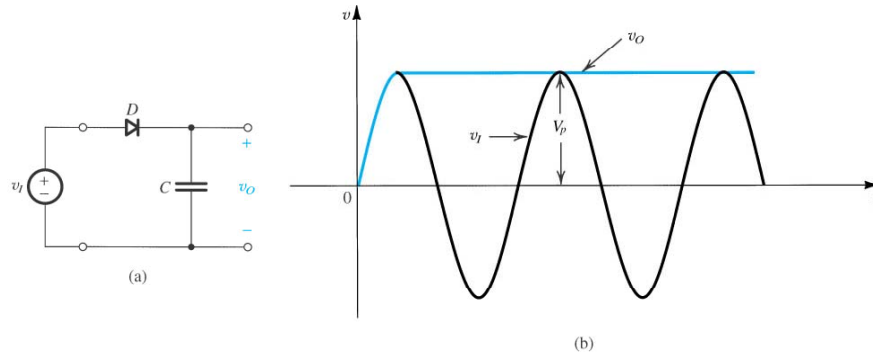

**Figure 3.28** (a) A simple circuit used to illustrate the effect of a filter capacitor. (b) Input and output waveforms assuming an ideal diode. Note that the circuit provides a dc voltage equal to the peak of the input sine wave. The circuit is therefore known as a peak rectifier or a peak detector.

### The rectifier with a filter capacitor

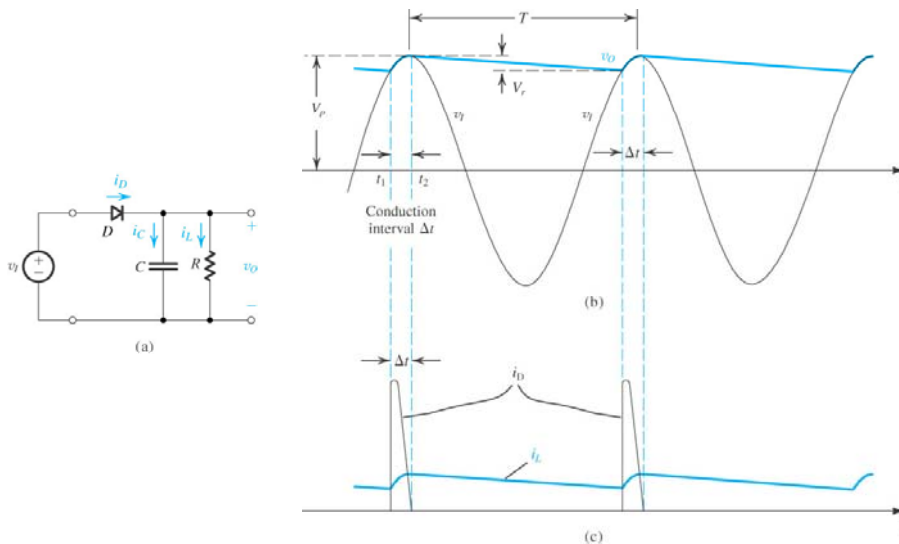

**Figure 3.29** Voltage and current waveforms in the peak rectifier circuit with  $CR \ll T$ . The diode is assumed ideal.

### The rectifier with a filter capacitor

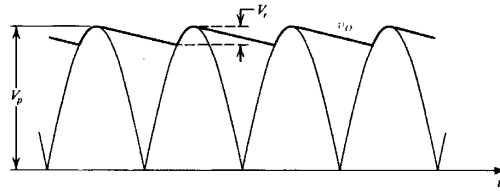


Figure 3.30 Waveforms in the full-wave peak rectifier.

### Precision Half-Wave Rectifier- The Super Diode

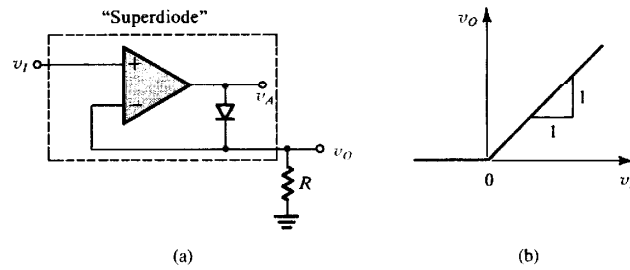


Figure 3.31 The "superdiode" precision half-wave rectifier and its almost-ideal transfer characteristic. Note that when  $v_I > 0$  and the diode conducts, the op amp supplies the load current, and the source is conveniently buffered, an added advantage. Not shown are the op-amp power supplies.

### Limiter Circuits

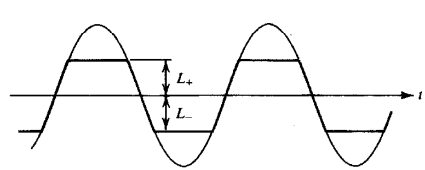


Figure 3.33 Applying a sine wave to a limiter can result in clipping off its two peaks.

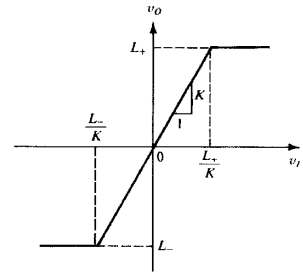


Figure 3.32 General transfer characteristic for a limiter circuit.

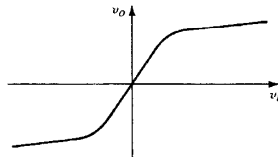


Figure 3.34 Soft limiting.

### Limiter Circuits

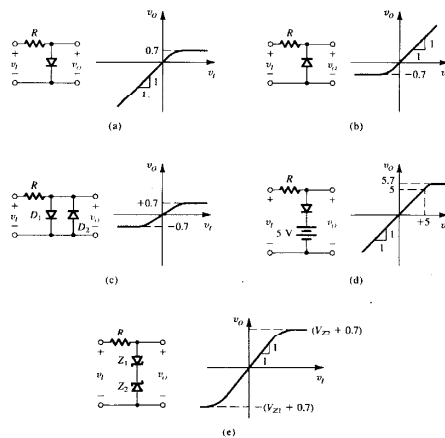


Figure 3.35 A variety of basic limiting circuits.

### The Clamped Capacitor or DC Restorer

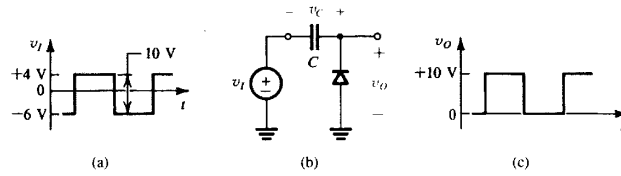


Figure 3.36 The clamped capacitor or dc restorer with a square-wave input and no load.

### The Clamped Capacitor or DC Restorer

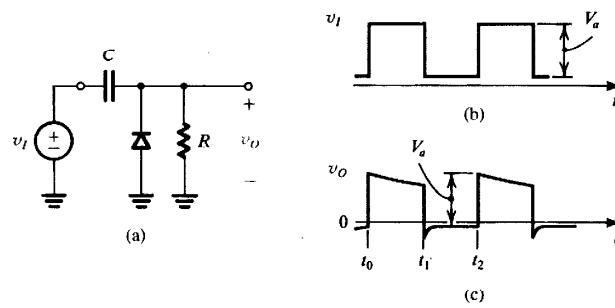


Figure 3.37 The clamped capacitor with a load resistance  $R$ .

### The Voltage Doublers


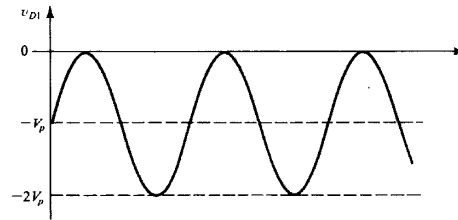


Figure 3.38 Voltage doubler: (a) circuit; (b) waveform of the voltage across  $D_1$ .

## Diode Applications

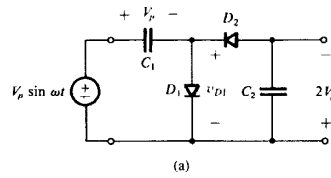

## AND/OR Gates

- AND and OR gates represent basic components of computers that are used in digital logic design.



OR-Gate

1	2	3
0	0	0
0	1	1
1	0	1
1	1	1



AND-Gate

1	2	3
0	0	0
0	1	0
1	0	0
1	1	1

If logic "1" is represented by +10 (+5) V and logic "0" is represented by 0 V, the OR and the AND gates can be represented by the following diode combinations;

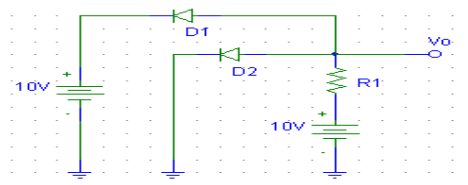
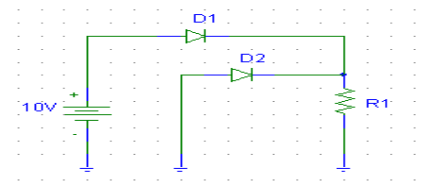
## AND/OR Gates

- For the OR gate;
  - D1  $\Rightarrow$  ON
  - D2  $\Rightarrow$  OFF
  - $V_o = 10V$  (logic 1)
- For the AND gate;
  - D1  $\Rightarrow$  OFF
  - D2  $\Rightarrow$  ON
  - $V_o = 0V$  (logic 0)



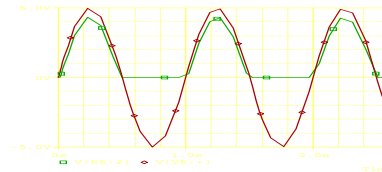
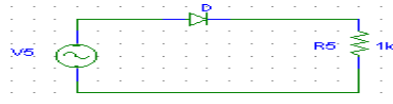
## Sinusoidal Inputs; Half-wave Rectification (Ideal diode Model)

- So far, we have considered time invariant signals only (DC).
- Now, diode circuit analysis will be extended to include circuits containing time varying signals (AC).
- The simplest diode application that uses AC signals is the HWR signal shown.
- To simplify the analysis, we'll assume that the diodes used are ideal.
- Note that, the DC content of the input waveform is zero, Why?
- During time interval  $t=0 \Rightarrow T/2$ , diode is ON.
- Since we are using an ideal diode model,  $v_o=v_i$ .
- *During the time interval  $t=T/2 \Rightarrow T$ , diode is OFF;  $v_o=0$ .*
- Now, what is the value of the DC level in the output waveform? ( $V_{dc}=0.318V_m$ )




M Hassan
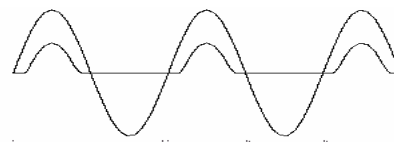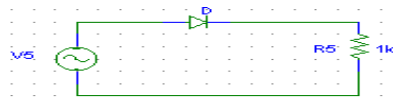
## HWR with Const Voltage Drop Diode Model





- In case of using the constant voltage drop diode model, during the conduction period diode will be replaced with a constant voltage source  $V_T$ .
- Thus, the peak of the output waveform will decrease from  $V_m$  by  $V_T$ .
- In addition, the conduction period of the diode will be slightly less than  $T/2$ .
- In this case, the DC content of the output waveform becomes;
- $V_{dc} \approx 0.318(V_m - V_T)$  (Note:  $0.318V_m = V_m/\pi$ )
- **Peak Inverse Voltage (PIV)**
- **Definition:** PIV is the value of the maximum reverse voltage that is expected to apply to the diode in during its operation.
- PIV: Peak Inverse Voltage in this case =  $V_m$ , Thus,  $PIV_{rating} > V_m$

### HWR Circuit With Smoothing Capacitor

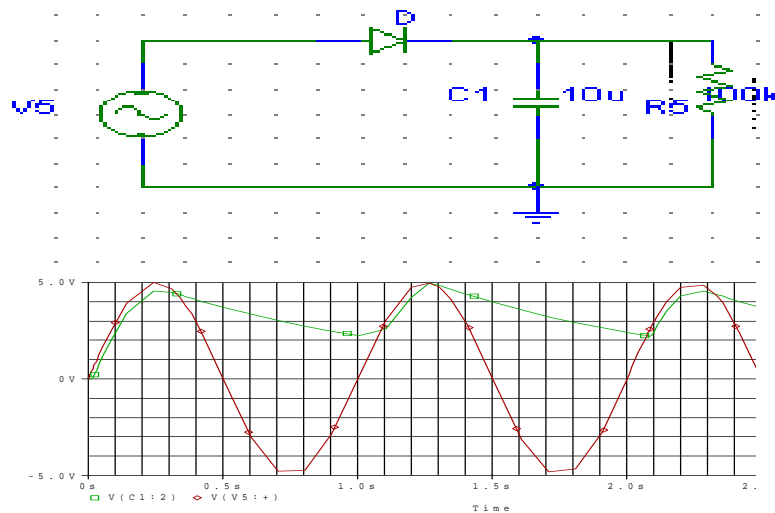


### Full-wave Rectifier

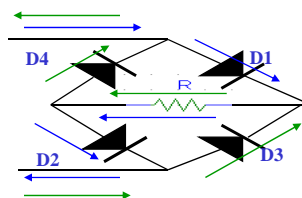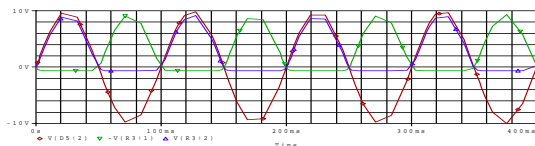

- As seen in the HWR circuit, the DC level obtained is small relative to the maximum value of the a/c signal.
- The reason for that low level DC is the removal of negative half-wave.
- DC level can be improved to 100% of that obtained in HWR, by using the **full-wave rectifier** configuration shown.
- For  $t=0 \rightarrow T/2$ , D1 and D2 ON while D3, and D4 OFF.
- For  $t=T/2 \rightarrow T$ , D3, D4 ON, while D1 and D2 OFF.
- As seen from the waveform generated, the DC level for that configuration is twice that of the HWR.
- $V_{dc(FWR)} = 2 \times V_{dc(HWR)} = 2 \times 0.318 V_m$ , ideal diode model.
- $= 2 \times 0.318 (V_m - 2V_T)$  simplified
- $PIV|_{rating} > V_m$

## Center Tapped Transformer FWR

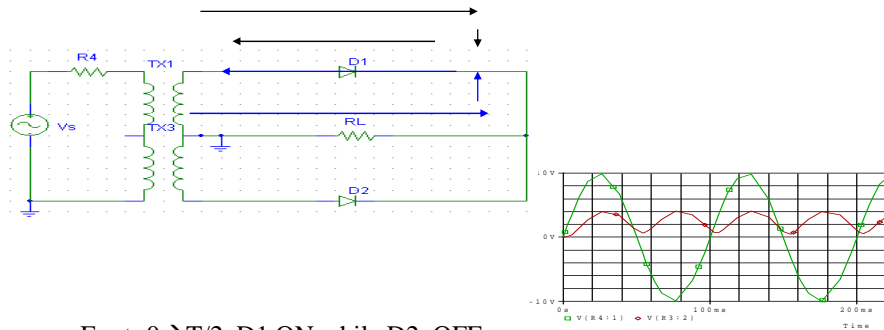

- For  $t=0 \rightarrow T/2$ ,  $D1$  ON while  $D2$ , OFF.
- For  $t=T/2 \rightarrow T$ ,  $D2$  ON, while  $D1$ , OFF
- $PIV|_{rating} > 2V_m$
- Example 2.19