

# Lecture 3

## Clipper Circuits

Clipper circuit is the circuit which clip off a portion of the input signal without distorting the remaining part of the signal


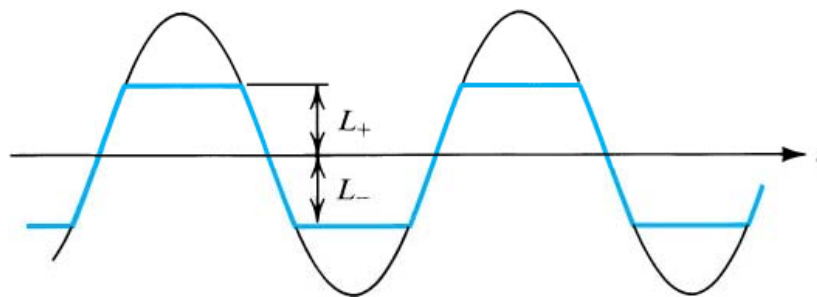


Figure 3.33 Applying a sine wave to a limiter can result in clipping off its two peaks.

# Clippers

- **Clipper** circuits is used to remove one part of the signal without distorting the remaining part.
- The orientation of the diode determines the part of the signal that is removed, while the value of the DC controls the level of clipping.
- It is usually consists of , a diode, a resistance and a DC source.
- Clippers have two major configurations;
  - Series Configuration, where the diode is connected in series with the the source.
  - Parallel Configuration; where the diode is connected in parallel with the output port.
    - *Single Side Clippers*      *Double Side Clippers*



## • Series Clippers

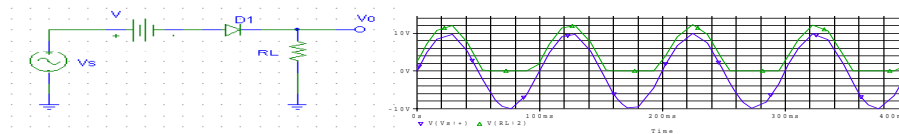

- The output voltage is given by KVL as;
- $v_o = v_s - V_D$  such that the voltage at the diode input has to be greater than  $V_T$  for the diode to conduct. Otherwise, the diode will be off and  $v_o$  will be zero.



## Parallel Clippers

### Upper Side Clippers:

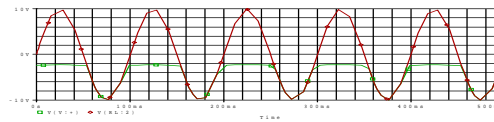
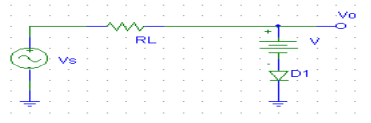


$$v_o = \begin{cases} v_i & \text{if } D \text{ is OFF} \\ v_D + V & \text{if } D \text{ is ON} \end{cases}$$

### Lower Side Clipper

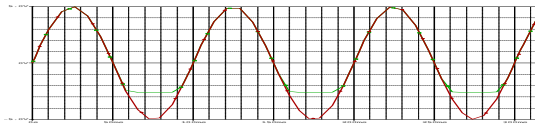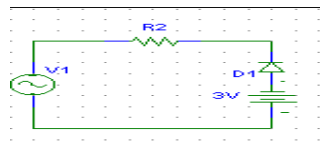


### Double Side Clipper

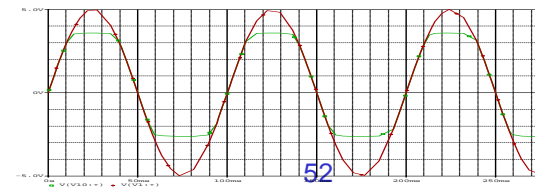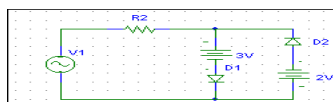
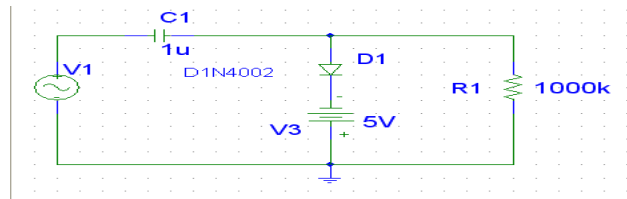
## Clampers

- A clamping circuit is the circuit that is used to clamp a signal to a certain DC level.
- It must contain a capacitor, a diode and a resistive element.
- The value of the *discharging* time constant of the capacitor,  $\tau_{dis}=RC \gg T/2$  has to be large enough to ensure that the capacitor doesn't discharge during the OFF period of the diode.
- The very small resistance of the diode  $R_D$  makes the *charging* time constant  $\tau_{ch}=R_D C$  so small that its can be considered that the diode charges in zero time.





## Clampers

- Rules:
  - The Direction of the diode's arrow determines whether the signal is clamped up or down.
  - The value of the DC source connected to the diode's anode determines the max or the min of the clamped signal respectively.

- Operation
  - For  $t=0 \rightarrow T/2$ , D is ON


Resistance R1 is short-circuited by the diode.

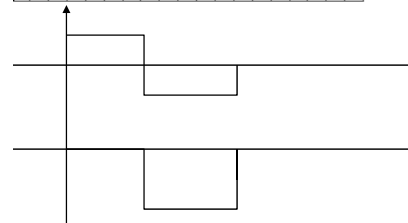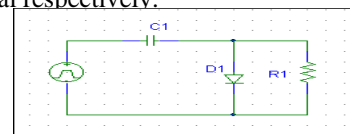- C charges to  $V_m$  in zero time (theoretically).
- For  $t=T/2 \rightarrow T$ , D is OFF.
- C discharges through R1
- The Value of the output voltage is  $-(V_s(V_m) + V_c(V_m))$



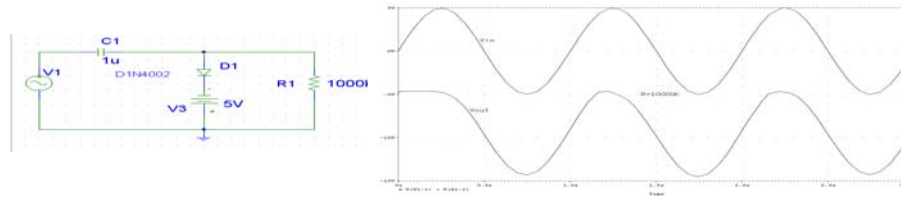
## Clampers

- Rules:
  - The Direction of the diode's arrow determines whether the signal is clamped up or down.
  - The value of the DC source connected to the diode's anode determines the max or the min of the clamped signal respectively.
- Operation


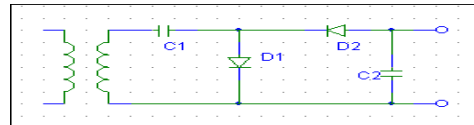
## VOLTAGE MULTIPLIER CIRCUITS

- Voltage multiplier circuits are used to maintain low transformer peak voltage and stepping up the voltage to 2, 3, or 5 times this value
- Voltage Doubler ( Half-Wave)




During +ive half cycle, D1 ON, D2 OFF, C1 charges to  $+V_m$

– During -ive half cycle, D1 OFF, D2 ON, C2 charges to  $+2V_m$  as following;

$$-V_{C2} + V_{C1} + V_m = 0$$


$$V_{C2} = V_{C1} + V_m = 2V_m$$

## Full-wave Voltage Multiplier

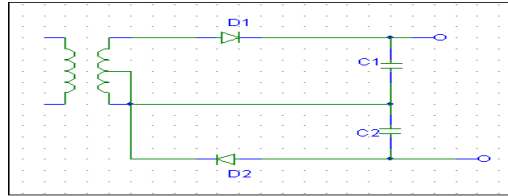

- During (+)ive half cycle, D1 ON, D2 OFF, C1 charges to  $+V_m$
- During (-)ive half cycle, D1 OFF, D2 ON, C2 charges to  $+V_m$ .
- So the total output voltage applied to the load is  $2V_m$ .

## Voltage Tripler and Quadrupler

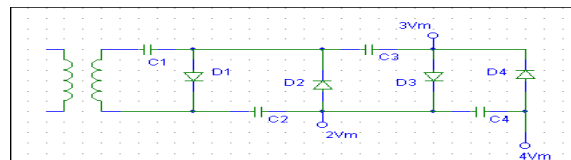

- During (+)ive half cycle , D1 ON, C1 charges to  $V_m$ .
- During (-)ive half cycle , D1 OFF, C2 charges to  $2V_m$  through C1 and the secondary winding of transformer.
- During the next (+)ive half-cycle, D3 conducts, and C2 charges C3 to  $2V_m$