

# Basic Circuit Theorems, Laws and Techniques

---

**Dr. : Mohamed Hassan Abd El-azeem**

# Lecture 2

## **Contents:**

---

### **1. Part 1 : Ohm's Law**

**Kirchhoff's Laws**

**Voltage Divider**

**Current Divider**

### **2. Part 2 : Source Transformation**


---

# 2.1 Ohm's Law

---


## □ Current and voltage sources in

action

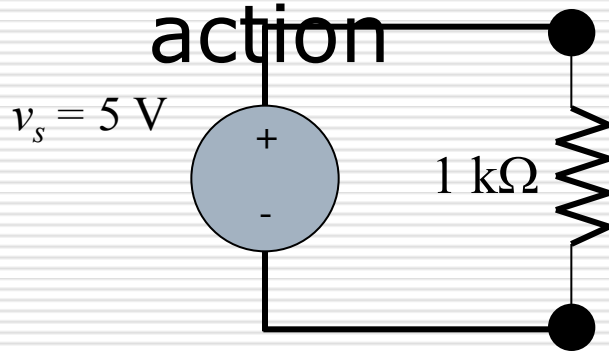

□ Compute current across R
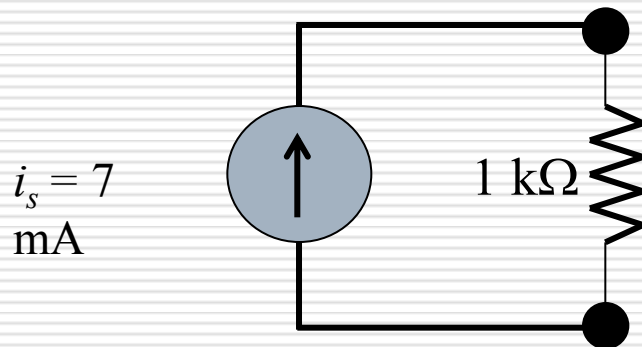
$$i = \frac{v}{R} = \frac{5V}{10^3 \Omega} = 5mA$$




□ Compute voltage across R

$$V = iR = 7mA \cdot 1k\Omega = 7V$$

# 2.2 Kirchhoff's Laws

---

## □ Nodes and loops

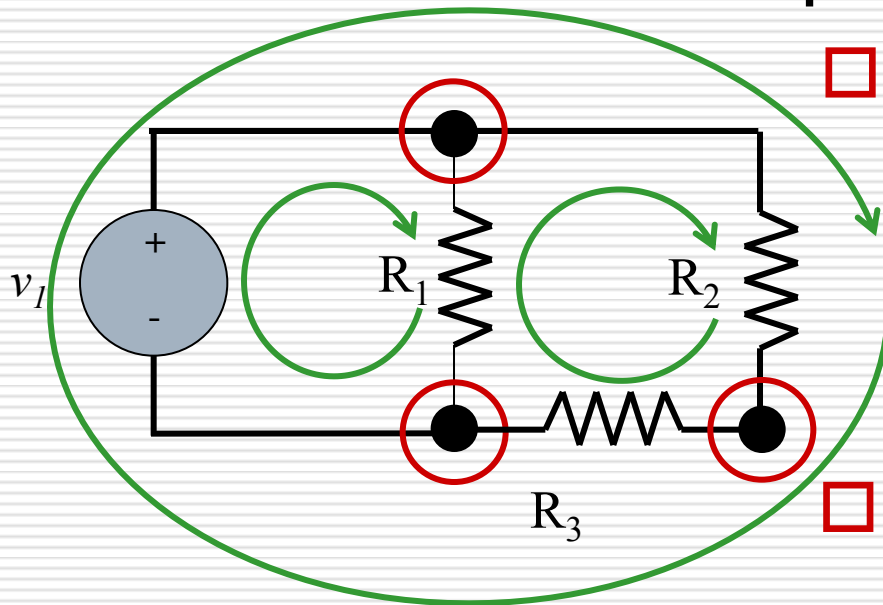


□ Nodes are points where 2 or more elements meet

□ Loops are closed paths around the circuit starting and ending at a node
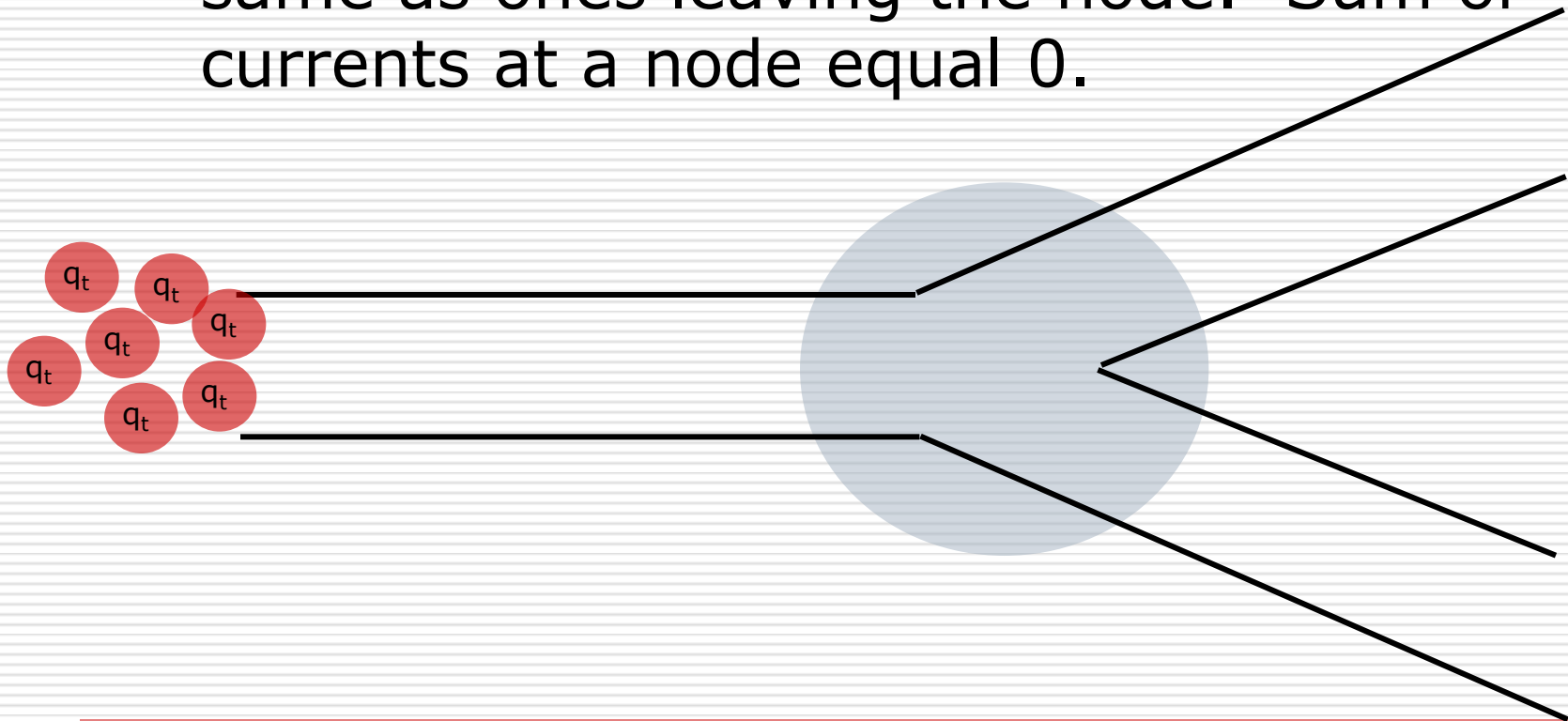
## 2.2.1 Kirchhoff's Current Law

---


- Charges entering a node are exactly the same as ones leaving the node. Sum of currents at a node equal 0.



## 2.2.1 Kirchhoff's Current Law

---


### □ Circuit Example

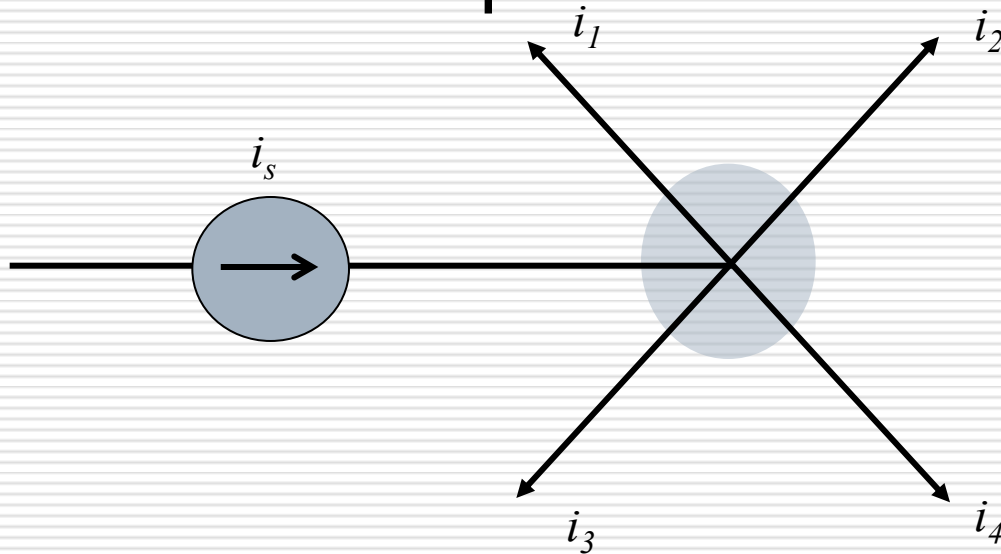

$$i_s = i_1 + i_2 + i_3 + i_4 \quad i_s - i_1 - i_2 - i_3 - i_4 = 0$$

## 2.2.2 Kirchhoff's Voltage Law

- Sum of voltages around a loop equal 0

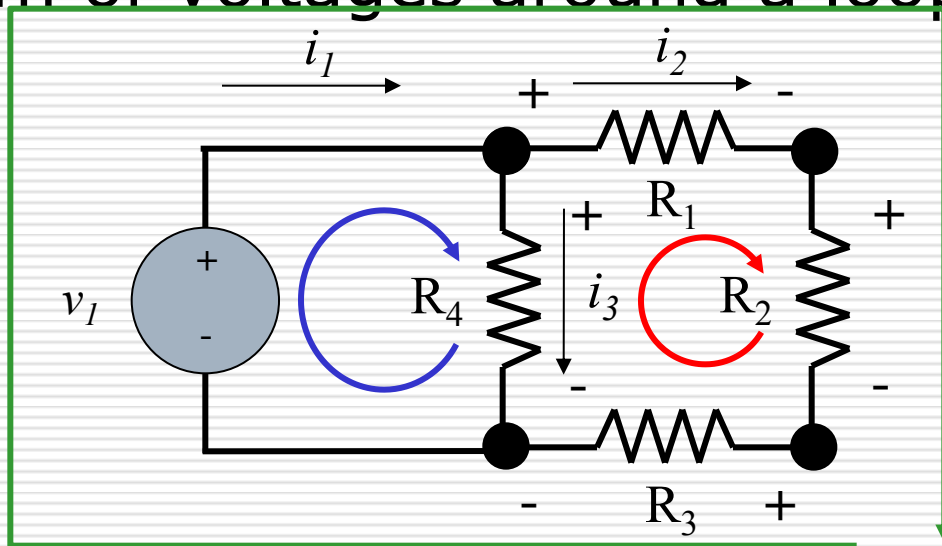

Loop 1:  $-v_1 + R_1 i_2 + R_2 i_2 + R_3 i_2 = 0$

Loop 2:  $-v_1 + R_4 i_3 = 0$

Loop 3:  $-R_4 i_3 + R_1 i_2 + R_2 i_2 + R_3 i_2 = 0$

## 2.3 Kirchhoff's Laws Exercise

- Compute  $i_1$ ,  $i_2$ , &  $i_3$ , & p expended for all resistors.  
Given  $R_1 = R_2 = R_3 = 10\text{k}\Omega$ ,  $R_4 = 15\text{k}\Omega$ , &  $v_1 = 15\text{V}$

Loop Equations

$$-v_1 + i_2(R_1 + R_2 + R_3) = 0$$

$$-v_1 + R_4 i_3 = 0$$


$$-R_4 i_3 + R_1 i_2 + R_2 i_2 + R_3 i_2 = 0$$

Node Equation(s)

$$i_1 - i_2 - i_3 = 0$$

$$-v_1 + R_4 i_3 = 0 \implies -15 + 15e3 i_3 = 0 \implies i_3 = 1\text{mA}$$
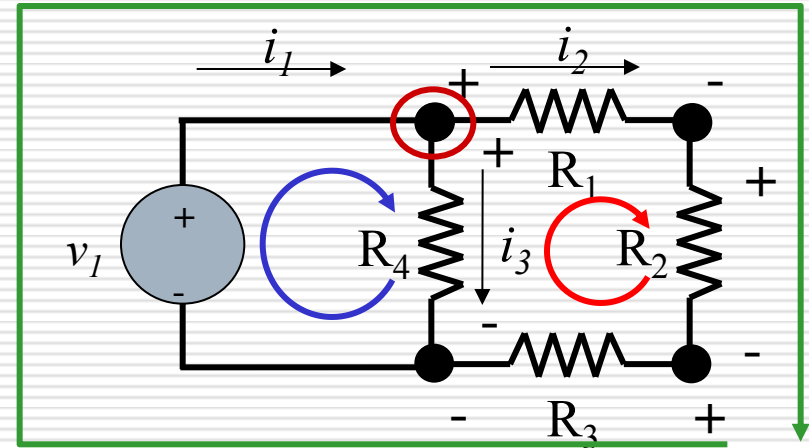
$$-v_1 + i_2(R_1 + R_2 + R_3) = 0 \implies -15 + i_2(30e3) = 0 \implies i_2 = 0.5\text{mA}$$





## 2.3 Kirchhoff's Laws Exercise

□ Given  $R_1 = R_2 = R_3 = 10\text{k}\Omega$ ,  $R_4 = 15\text{k}\Omega$ , &  $v_1 = 15\text{V}$   
 Loop Equations


$$-v_1 + i_2(R_1 + R_2 + R_3) = 0$$

$$-v_1 + R_4 i_3 = 0$$

$$-R_4 i_3 + R_1 i_2 + R_2 i_2 + R_3 i_2 = 0$$

Node Equation(s)

$$i_1 - i_2 - i_3 = 0$$

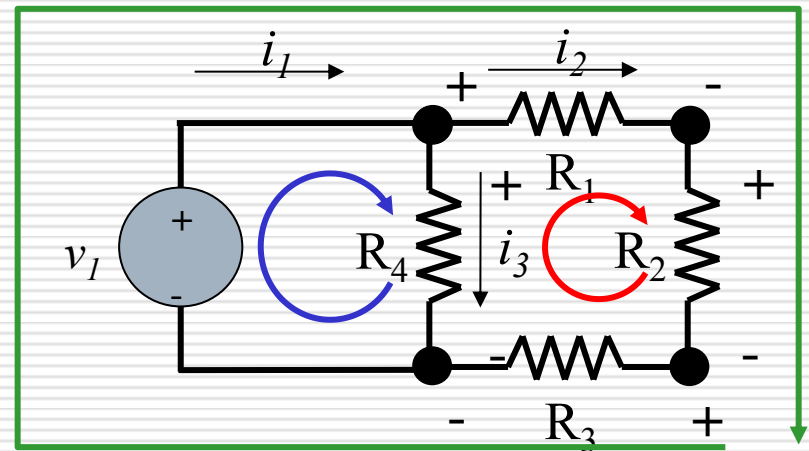

$$i_2 = 0.5\text{mA} \quad i_3 = 1\text{mA} \quad i_1 - i_2 - i_3 = 0 \quad \Rightarrow \quad i_1 = 1.5\text{mA}$$

$$p_{R1} = p_{R2} = p_{R3} = (i_2)^2 R = (0.5\text{mA} \times 0.5\text{mA}) 10\text{e}3 = 2.5\text{mW}$$

$$p_{R4} = (i_3)^2 R = (1\text{mA})^2 15\text{e}3 = 15\text{mW}$$


# 2.4 Voltage Divider

---

$$i_s = \frac{v_s}{R_1 + R_2}$$


$$v_1 = \frac{R_1}{R_1 + R_2} v_s$$

$$v_2 = \frac{R_2}{R_1 + R_2} v_s$$

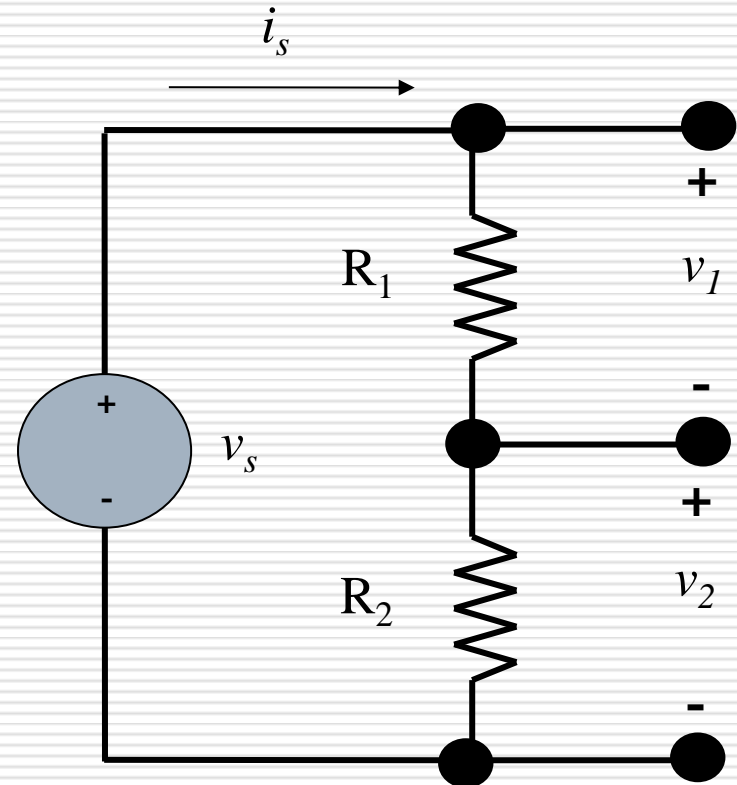

# Voltage Divider

- Find  $v_o$  in terms of  $v_s$

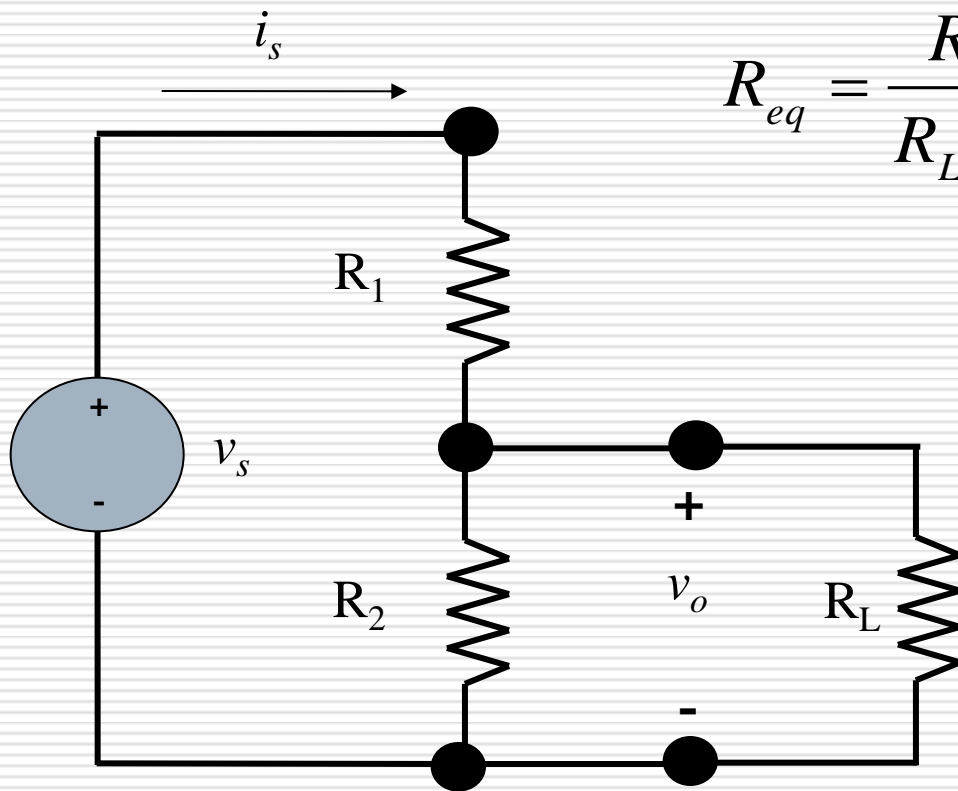

$$R_{eq} = \frac{R_L R_2}{R_L + R_2}$$

$$V_o = \frac{R_{eq}}{R_1 + R_{eq}} V_s$$

$$V_o = \frac{\frac{R_L R_2}{R_L + R_2}}{R_1 + \frac{R_L R_2}{R_L + R_2}} V_s$$

$$= \frac{R_L R_2}{R_1 (R_L + R_2) + R_L R_2} V_s$$

# 2.5 Current Divider


□ Find  $i_1$  and  $i_2$  in terms of  $i_s$

$$i_s = i_1 + i_2 \quad i_1 R_1 = i_2 R_2$$

$$i_2 = i_1 \frac{R_1}{R_2} \Rightarrow i_s = i_1 + i_1 \frac{R_1}{R_2} = i_1 \left( \frac{R_2 + R_1}{R_2} \right)$$


$$i_1 = i_s \left( \frac{R_2}{R_1 + R_2} \right)$$
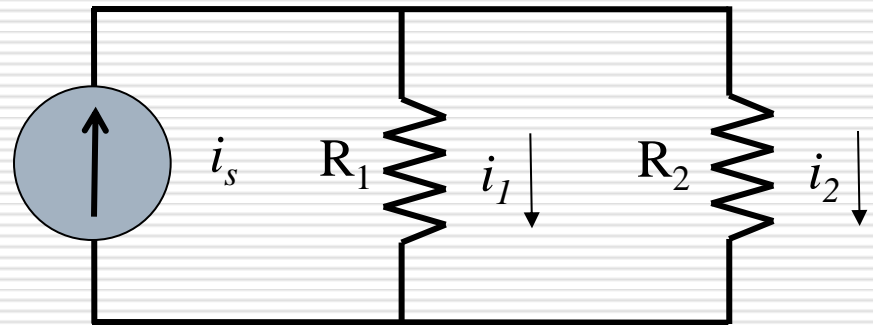
$$i_2 = i_s \left( \frac{R_1}{R_1 + R_2} \right)$$



# Note: Resistors in Series & Parallel

□ Find equivalent resistance

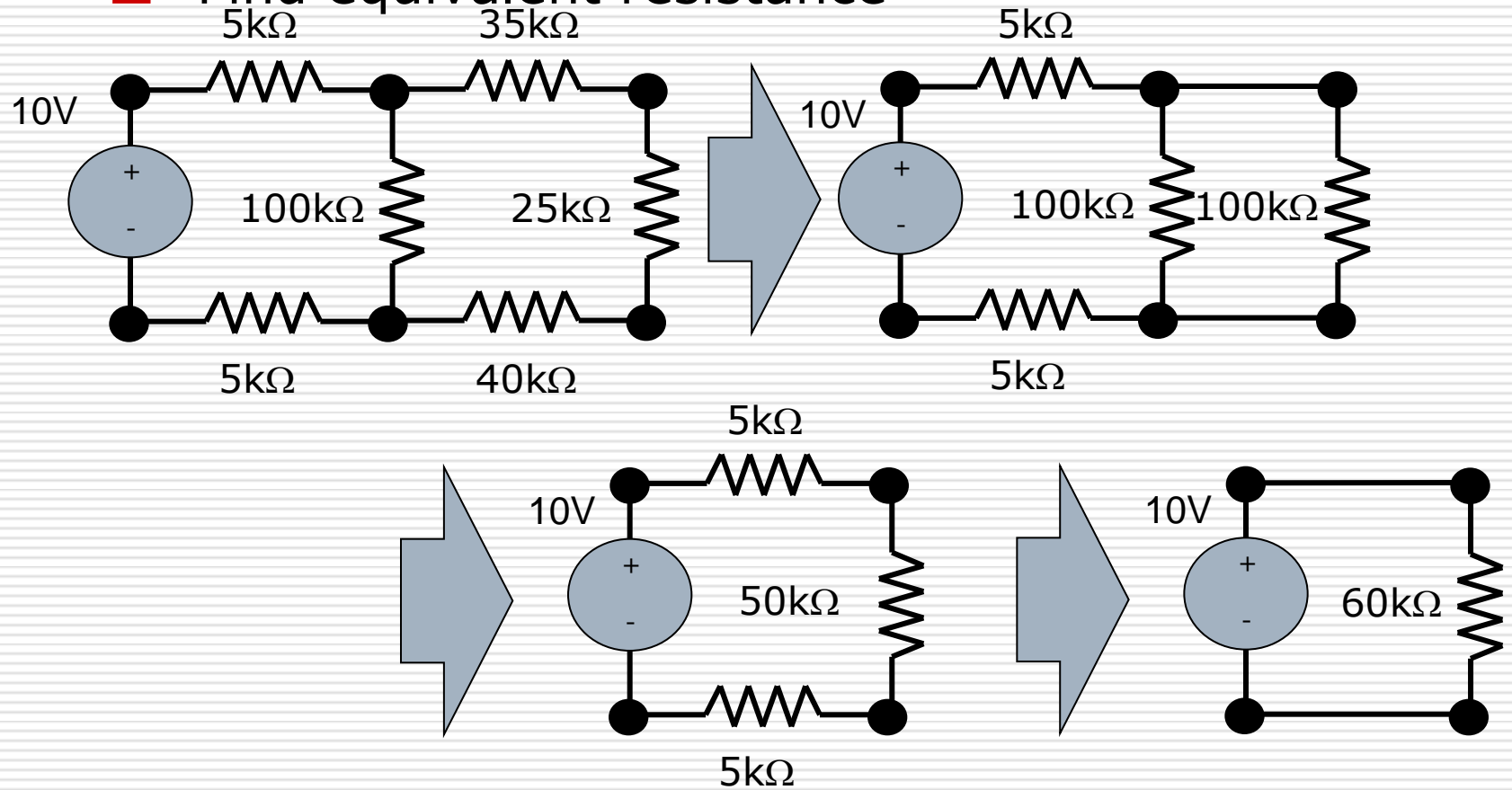

### Example 2-1

Find  $v_1$  and  $v_2$  in the circuit shown in Fig., Also calculate  $i_1$  and  $i_2$  and the power dissipated in the 12- $\Omega$  and 40- $\Omega$  resistors.

### Solution:-

$$12 \parallel 6 = \frac{12 \cdot 6}{12 + 6} = 4 \Omega$$

$$40 \parallel 10 = \frac{40 \cdot 10}{40 + 10} = 8 \Omega$$



$$V_1 = 15 \frac{4}{4 + 8} = 5 \text{ V} \quad V_2 = 15 \frac{8}{4 + 8} = 10 \text{ V}$$

$$i_1 = \frac{V_1}{12 \Omega} = \frac{5 \text{ V}}{12 \Omega} = 416.7 \text{ mA}$$

$$i_2 = \frac{V_2}{40 \Omega} = \frac{10 \text{ V}}{40 \Omega} = 250 \text{ mA}$$


$$P_{12\Omega} = (i_1)^2 \cdot 12 = \frac{(V_1)^2}{12} = 2.083 \text{ W}$$
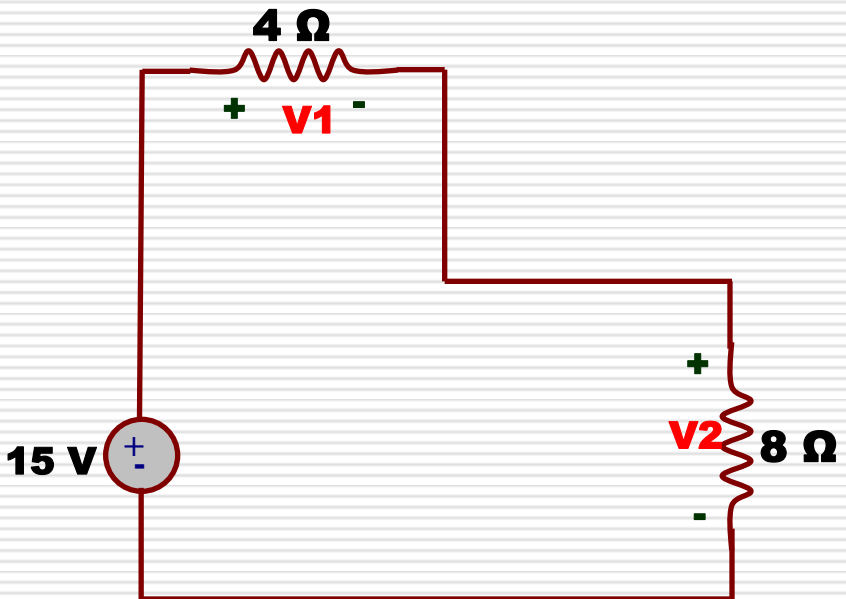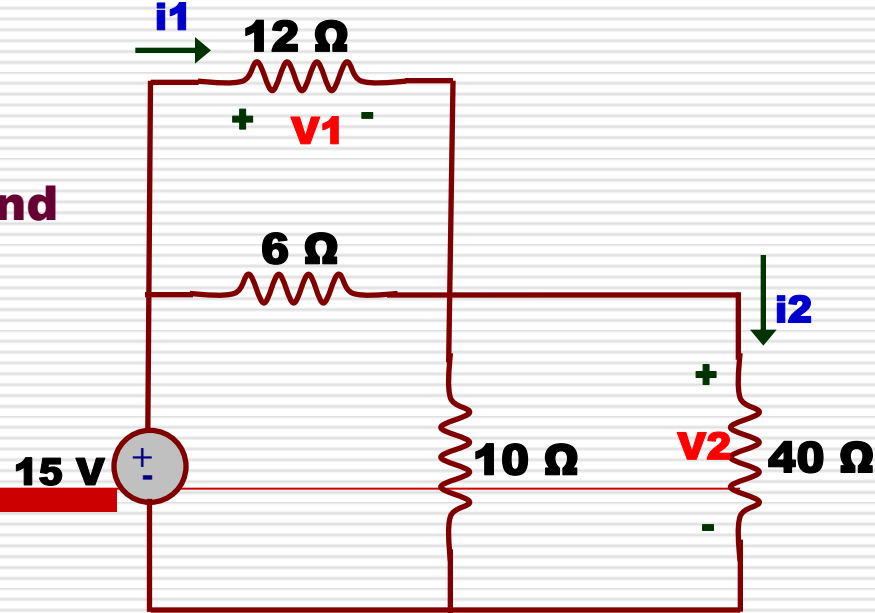
$$P_{40\Omega} = (i_2)^2 \cdot 40 = \frac{(V_2)^2}{40} = 2.5 \text{ W}$$


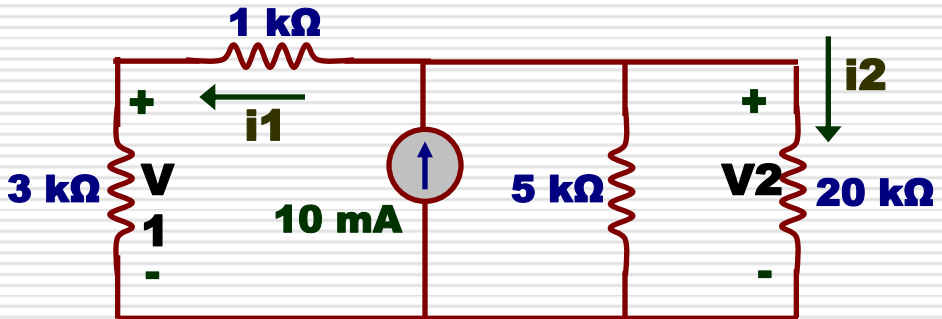
# Example 2.2

For the circuit shown in Fig., find:  
**(a)**  $v_1$  and  $v_2$ , **(b)** the power dissipated in the 3-k and 20-k resistors, and **(c)** the power supplied by the current source.



## Solution:-

~~$$i_1 = i_s \frac{R_{eq}}{4 \text{ k}\Omega} \quad i_2 = i_s \frac{R_{eq}}{20 \text{ k}\Omega} \quad \frac{1}{R_{eq}} = \frac{1}{20 \text{ k}\Omega} + \frac{1}{5 \text{ k}\Omega} + \frac{1}{4 \text{ k}\Omega}$$~~

$$R_{eq} = 2 \text{ k}\Omega \longrightarrow i_1 = 10 \text{ mA} \frac{2 \text{ k}\Omega}{4 \text{ k}\Omega} = 5 \text{ mA} \quad i_2 = 10 \text{ mA} \frac{2 \text{ k}\Omega}{20 \text{ k}\Omega} = 1 \text{ mA}$$

$$V_1 = i_1 3 \text{ k}\Omega = 15 \text{ V}$$

$$V_2 = i_2 20 \text{ k}\Omega = 20 \text{ V}$$

$$P_{3\text{-k}} = (i_1)^2 3 \text{ k}\Omega = \frac{(V_1)^2}{3 \text{ k}\Omega} = 75 \text{ mW}$$



$$P_{20\text{-k}} = (i_2)^2 20 \text{ k}\Omega = \frac{(V_2)^2}{20 \text{ k}\Omega} = 20 \text{ mW}$$

$$P_{10\text{-mA}} = - i_s * V_2 = - 10 \text{ mA} * 20 \text{ V} = - 200 \text{ mW}$$
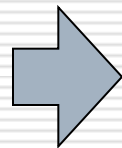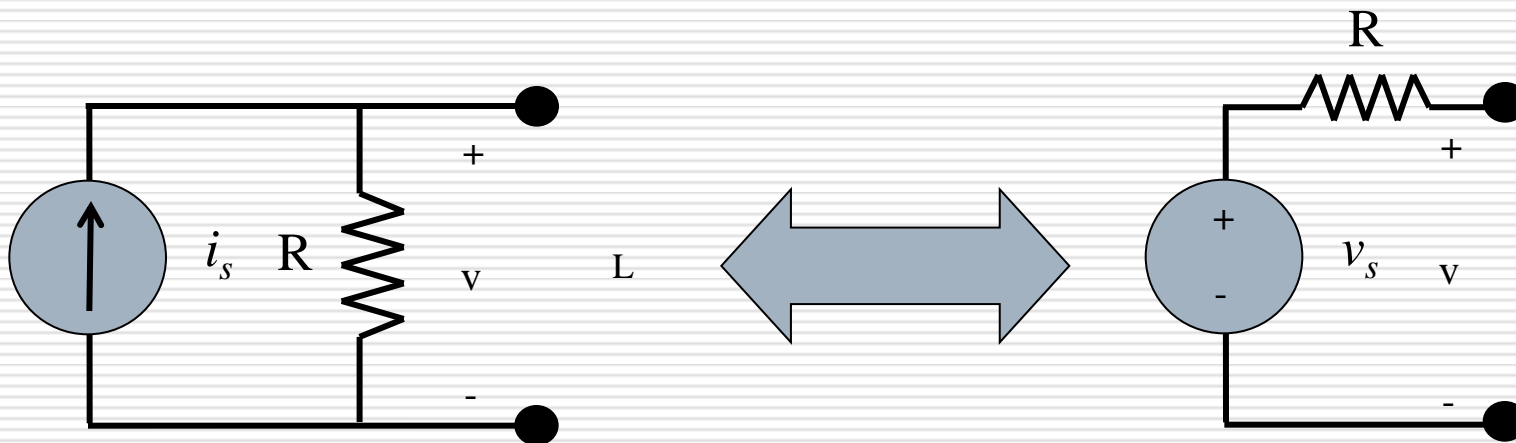
# 2.6 Source Transformation

- We can convert a voltage source with series resistor to a current source with parallel resistor.

If we place a load then the voltage across the load should be the same





$$v_s = i_s R$$






# Source Transformation

□ More simplifications

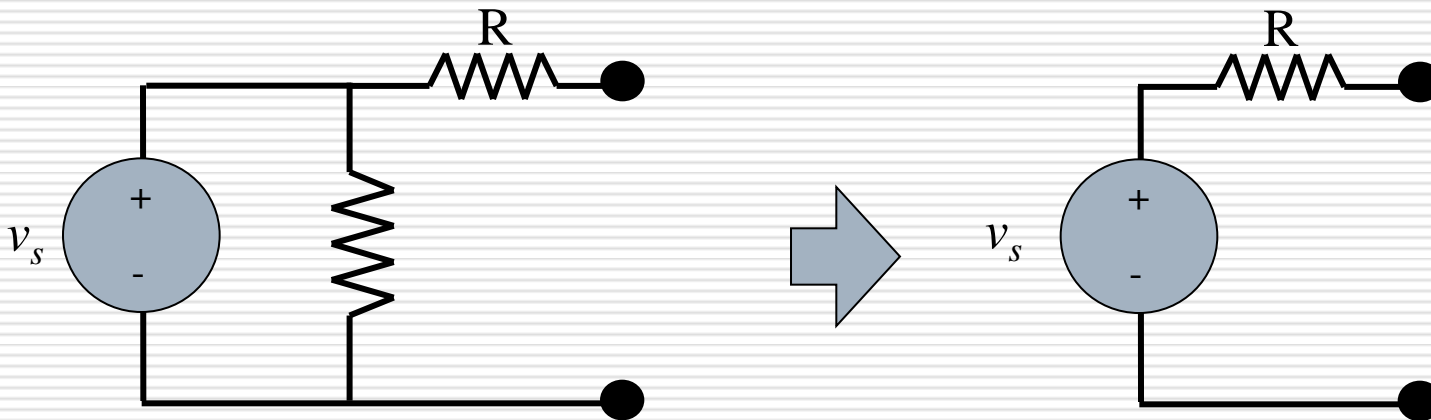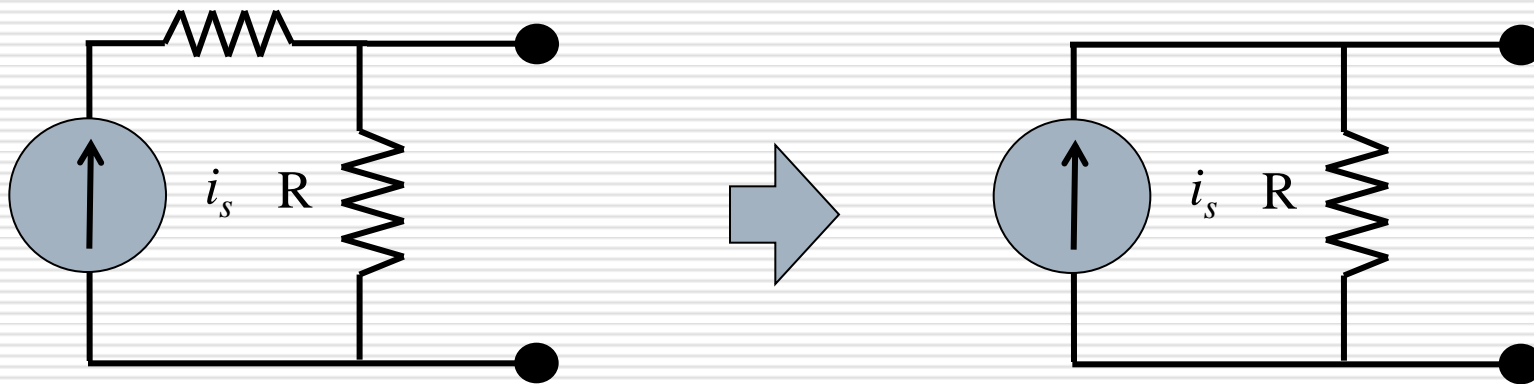



# Source Transformation Example

Find  $v_0$

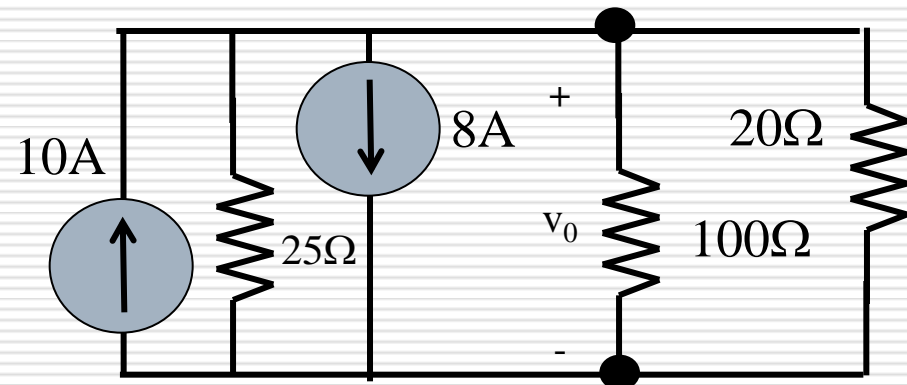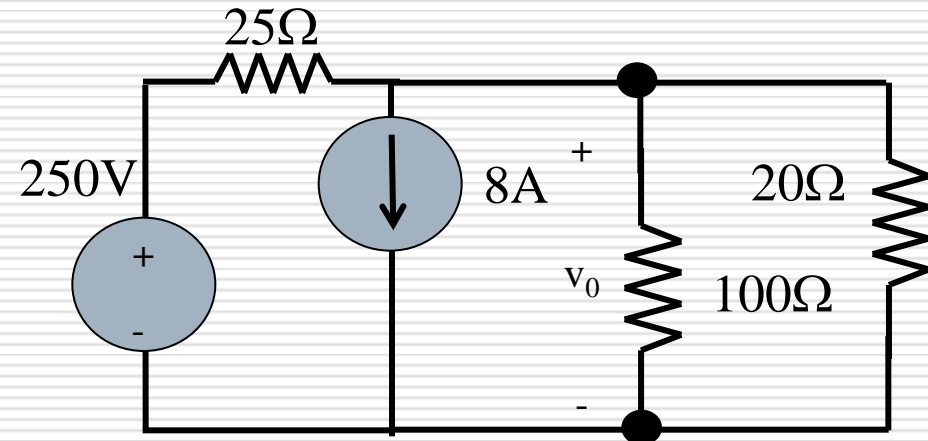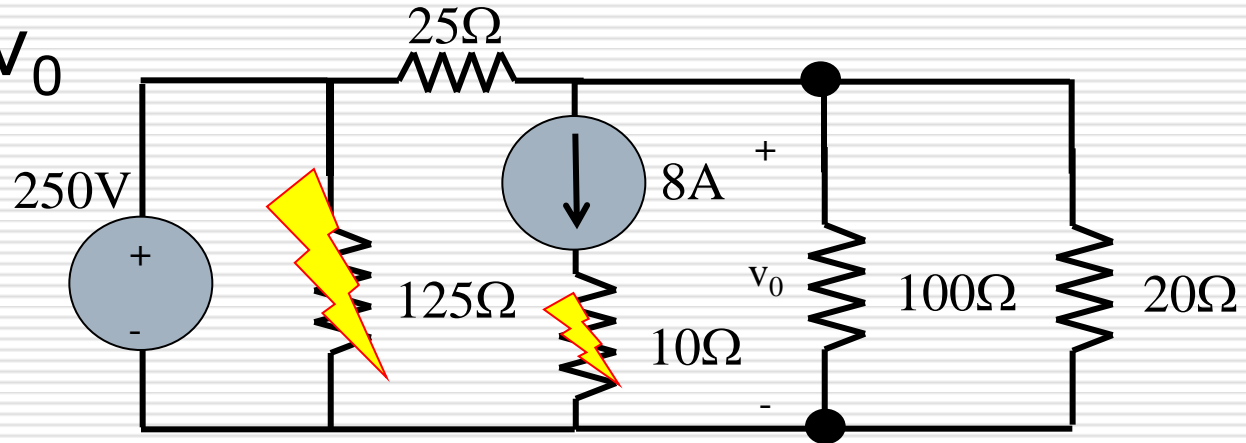

# 2.7 Source Transformation

## Example : Find $V_0$

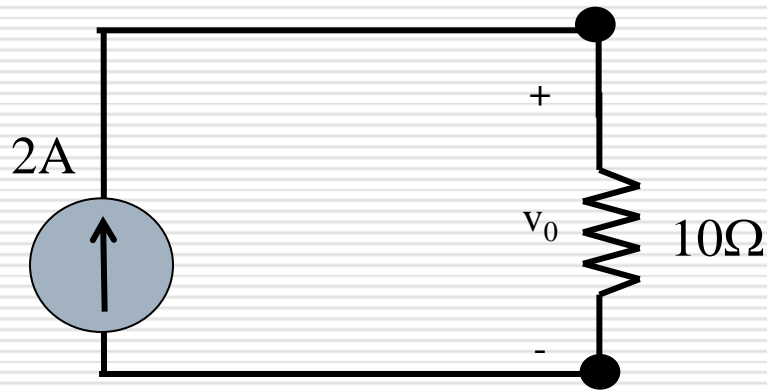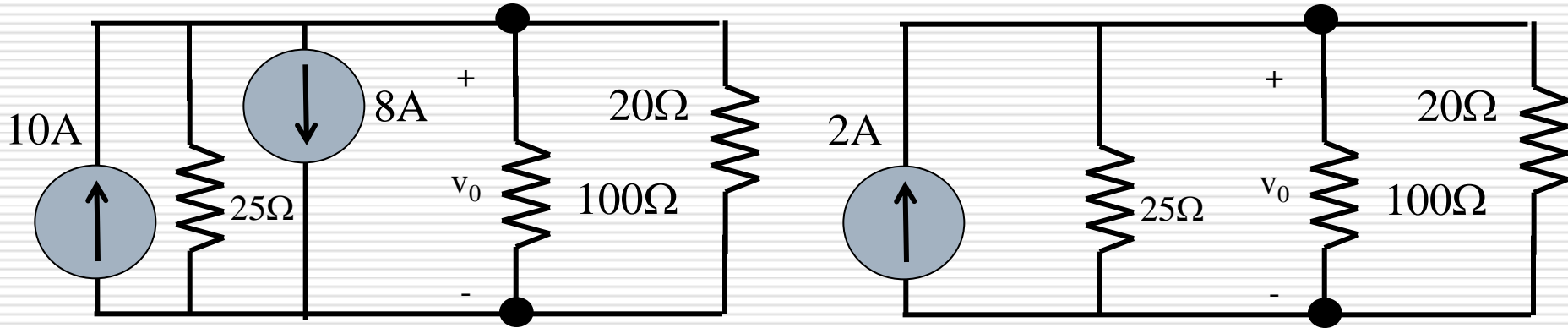

$$V_0 = 20V$$

**Example 2-3**

In the circuit shown in Fig., use the ST to find  $v_o$

**Solution**

$3\text{ A}, 4\text{-}\Omega$  ( $\parallel$ )  $\longrightarrow$   $12\text{ V}, 4\text{-}\Omega$  (Series)

$12\text{ V}, 3\text{-}\Omega$  (Series)  $\longrightarrow$   $4\text{ A}, 3\text{-}\Omega$  ( $\parallel$ )

$4\ \Omega + 2\ \Omega = 6\ \Omega$

$12\text{ V}, 6\text{-}\Omega$  (Series)  $\longrightarrow$   $2\text{ A}, 6\text{-}\Omega$  ( $\parallel$ )





$6\ \Omega \parallel 3\ \Omega = \frac{6 * 3}{6+3} = 2\ \Omega$

Also, current sources in parallel can be (combined) added together according to the current direction, in our case here

$4\text{ A (up)} + 2\text{ A (down)} \longrightarrow 2\text{ A (up)}$

$$i = \frac{2}{2 + 8} (2\text{ A}) = 0.4\text{ A}$$

$v_o = 8 * i = 8 * 0.4 = 3.2\text{ V}$

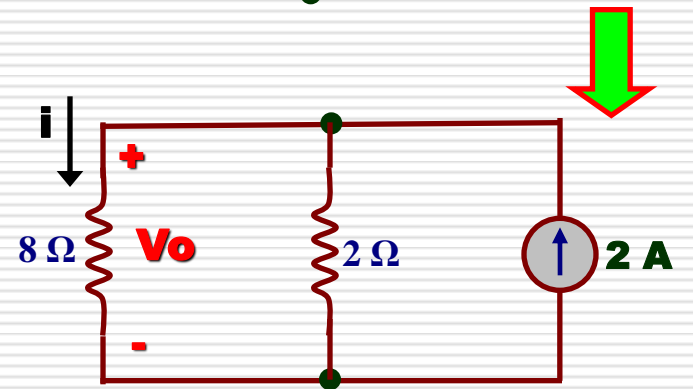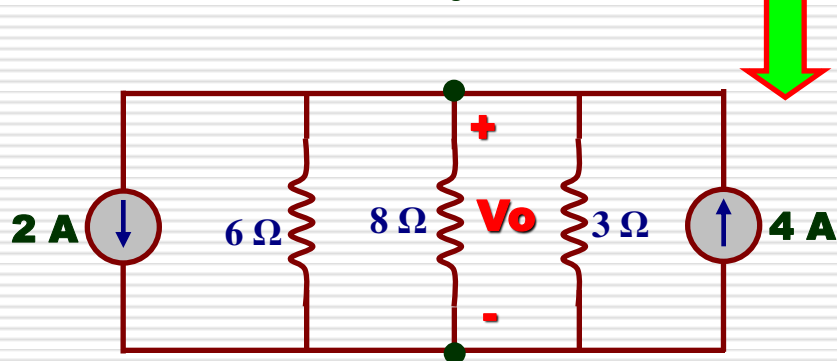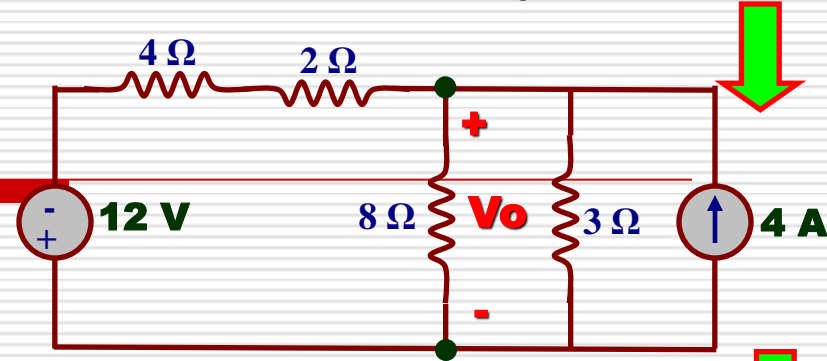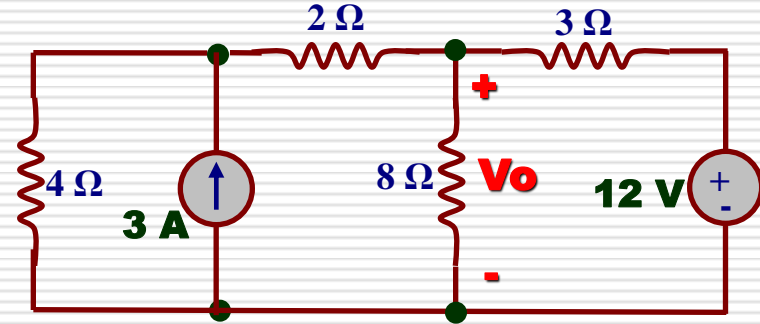

## Example 2.4

In the circuit shown in Fig., calculate P<sub>6V</sub>

### Solution

40 V, 5-Ω (Series) → 8 A, 5-Ω  
(||)

5 Ω || 20 Ω =  $5 * 20 / (5+20) = 4 \Omega$

8 A, 4-Ω (||) → 32 V, 4-Ω  
(Series)

6 Ω + 4 Ω + 10 Ω = 20 Ω

32 V, 20-Ω (Series) → 1.6 A, 20-Ω  
(||)

30 Ω || 20 Ω =  $30 * 20 / (30+20) = 12 \Omega$

1.6 A, 12-Ω (||) → 19.2 V, 12-Ω  
(Series)





$i = 19.2 - 6 / (12 + 4) = 0.825 \text{ A}$

P<sub>6V</sub> = + (6 V) \* (0.825 A) = 4.95 W

(Delivered)

6 V  
2 October 2013

19.2 V  
Dr. MOHAMED HASSAN

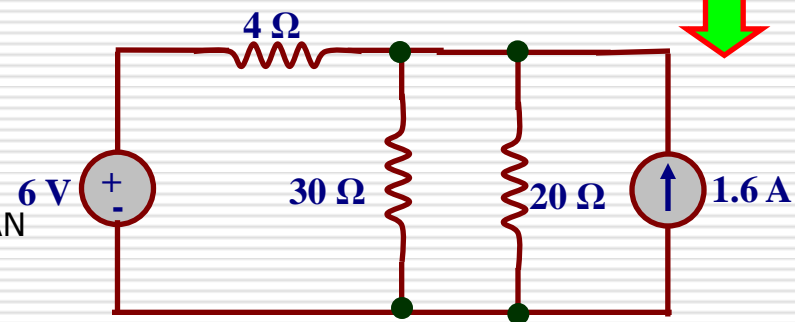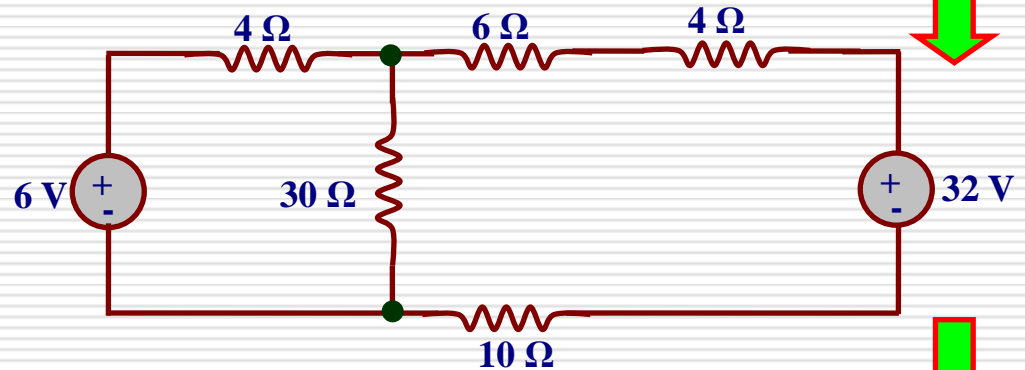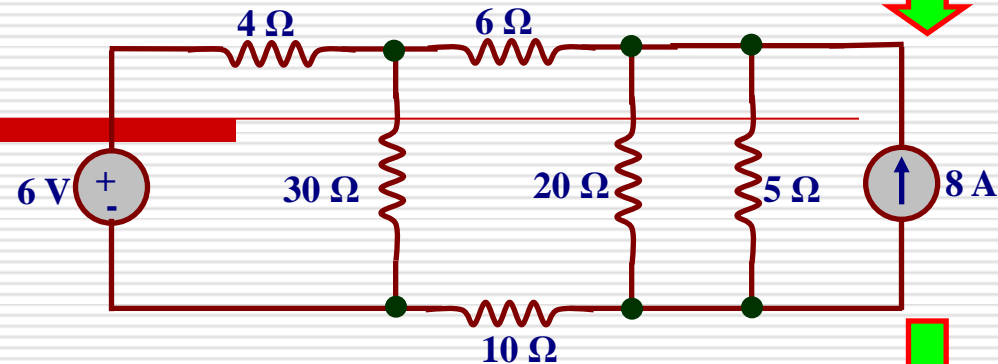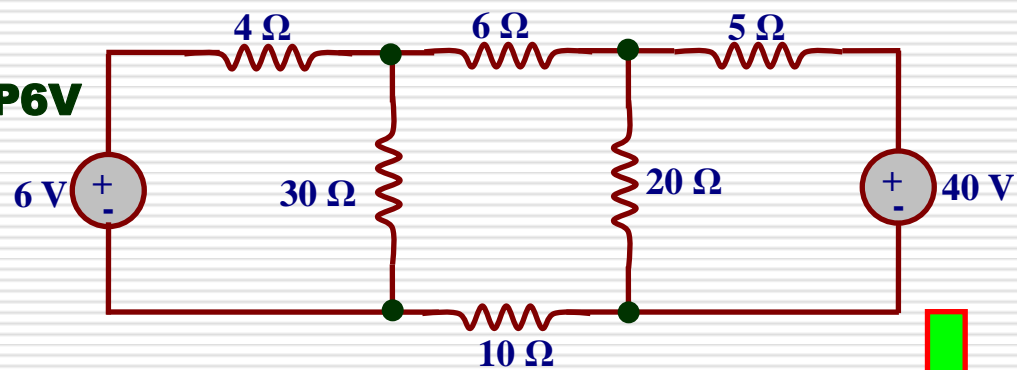


### Example 2.5

In the circuit shown in Fig., use the ST to calculate (a)  $V$  and (b)  $P_{120V}$

### Solution

(a)

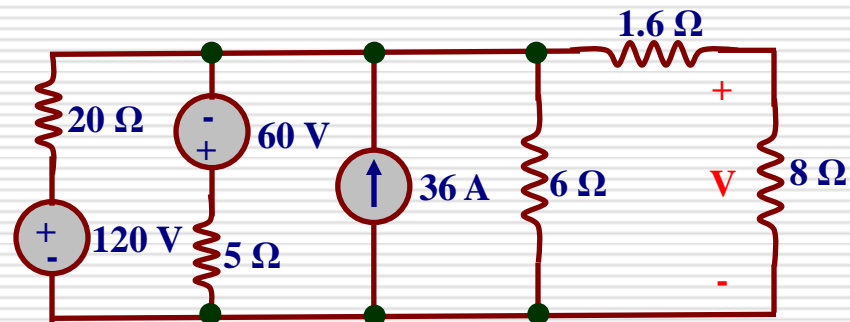

**120 V, 20-Ω (Series)**

**6 A, 20-Ω (||)**

**60 V, 5-Ω (Series)**

**12 A, 5-Ω (||)**

$$20 \Omega \parallel 5 \Omega \parallel 6 \Omega = 2.4 \Omega$$



**6A (up) + 12A (down) + 36A (up)**

**30 (up)**

**30 A, 2.4-Ω (||)**

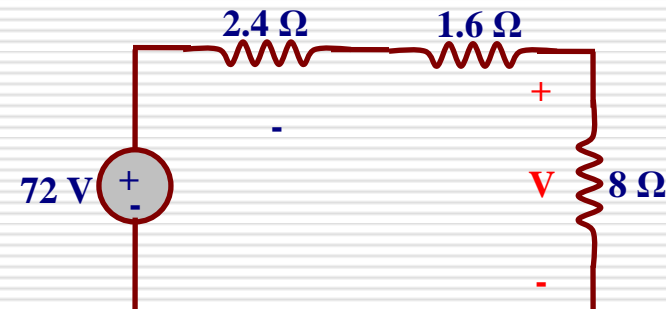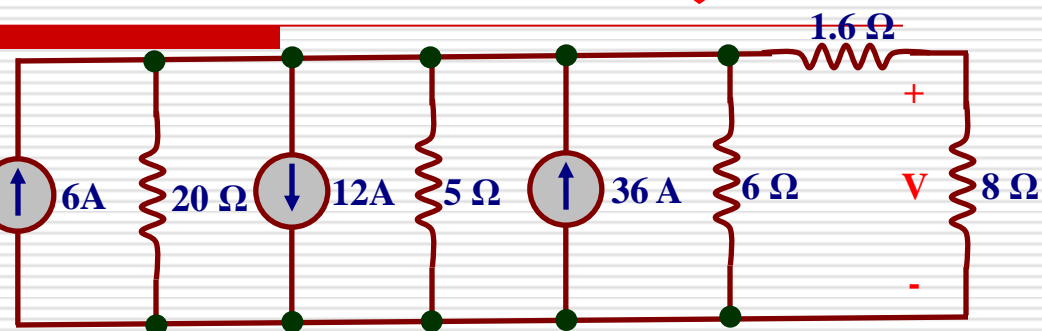**72 V, 2.4-Ω (Series)**

$$V = \frac{72}{2.4 + 1.6 + 8} (8) = 48 \text{ V}$$



**(b)**

**60 V, 5-Ω (Series)**

→ **12 A, 5-Ω (||)**

**5 Ω || 6 Ω || (8 Ω + 1.6 Ω) = 2.124 Ω**




**36A (up) + 12A (down) = 24 (up)**

**24 A, 2.124-Ω (||)**

→ **50.7 V, 2.124-Ω (Series)**

$$i = \frac{120 - 50.7}{20 + 2.124} = 3.12 \text{ A}$$

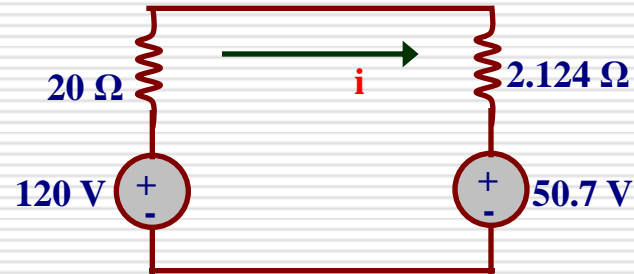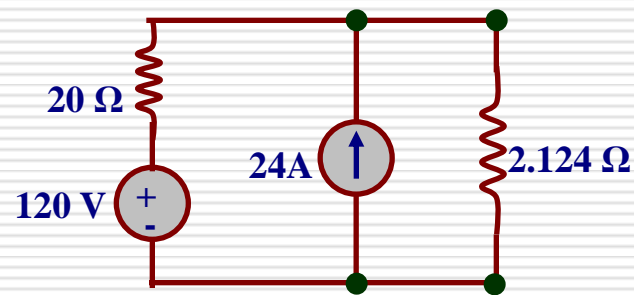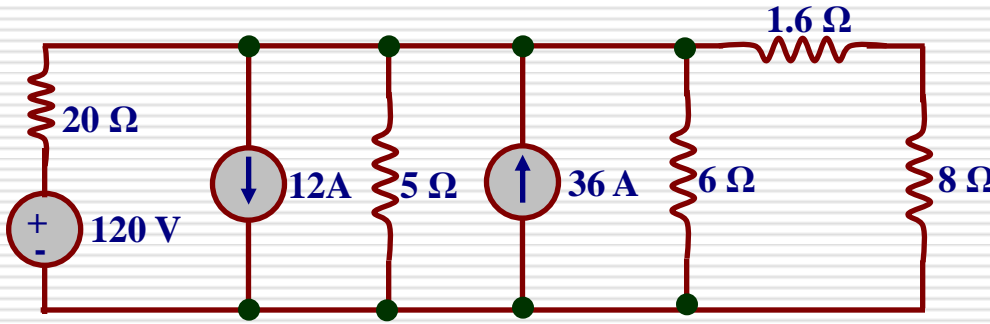**P<sub>120V</sub> = - 120 (3.12) = 374.4 W (Delivered)**



# Example 2.6

In the circuit shown in Fig., use the ST to calculate  $i_O$

**Answer**

$i_O = 1.78 \text{ A}$

