



Sheet 2: Bipolar Differential Pair

1. A bipolar differential pair has $R_C = 1 \text{ K}\Omega$ and $I_{EE} = 1 \text{ mA}$. Calculate the minimum value of $(V_{CC} - V_{CM})$ to avoid saturation, then estimate the upper limit of V_{CM} .
2. A bipolar differential pair has $R_C = 1 \text{ K}\Omega$, $V_{CC} = 2.5 \text{ V}$ and $I_{EE} = 0.5 \text{ mA}$. What is the maximum base voltage if the differential input is large enough to completely steer the tail current.
3. For a bipolar differential pair amplifier, determine the differential input voltage that steers 98% of the tail current to Q_2 .
4. Design a bipolar differential pair amplifier to provide that $V_{od} = (V_{o1} - V_{o2}) = 1 \text{ V}$ when $V_{id} = 10 \text{ mV}$. Where $I_{EE} = 2 \text{ mA}$, $V_{CC} = 10 \text{ V}$.
5. For a bipolar differential pair amplifier, calculate I_{C1} , I_{C2} , and hence $(V_{C2} - V_{C1})$. Where $I_{RC} = 5 \text{ V}$ and $V_{id} = 10 \text{ mV}$