



Sheet 1: MOSFET Differential Pair Amplifier

1. For a differential pair amplifier, $k(W/L) = 4 \text{ mA/V}^2$, $V_t = 0.5 \text{ V}$, $I = 0.4 \text{ mA}$, and $R_D = 2.5 \text{ K}\Omega$.
 - a. Calculate V_{ov}
 - b. Calculate V_{gs}
 - c. What is the highest value of V_{cm} for which Q1 and Q2 remains in saturation
 - d. If I requires a minimum voltage of 0.4 V to operate, what is the lowest value allowed for V_s and hence V_{cm}
 - e. For $V_{cm} = 0$, calculate V_s , i_{D1} , i_{D2} , v_{D1} , and v_{D2}
2. Problem # 7.1 (Sedra)

From problem 2 to 6 Let

$k(W/L) = 3 \text{ mA/V}^2$, $V_t = 0.7 \text{ V}$, $I_{ss} = 0.2 \text{ mA}$, $V_{DD} = V_{SS} = 2.5\text{V}$, and $R_D = 5 \text{ K}\Omega$

3. For a differential pair amplifier, calculate
 - a. The value of v_{id} that causes Q_1 to conduct the entire current I_{ss}
 - b. v_{D1} and v_{D2}
 - c. The differential output voltage.
4. For a differential pair amplifier, calculate the differential voltage gain. Where $g_m = 14 \text{ ms}$ and $R_D = 360 \Omega$.
5. Design a differential pair amplifier for voltage gain of -5 and a power budget of 2 mW subjected th the condition that the stage following the differential pair requires an input CM level of at least 1.7 V.
6. For a differential amplifier, calculate the value of v_{id} that corresponds to each of the following situations
 - a. $i_{D1} = i_{D2} = 0.1 \text{ mA}$
 - b. $i_{D1} = 0.15 \text{ mA}$ and $i_{D2} = 0.05 \text{ mA}$
 - c. $i_{D1} = 0.2 \text{ mA}$ and $i_{D2} = 0$
 - d. $i_{D1} = 0.05 \text{ mA}$ and $i_{D2} = 0.15 \text{ mA}$
 - e. $i_{D1} = 0$ and $i_{D2} = 0.2 \text{ mA}$