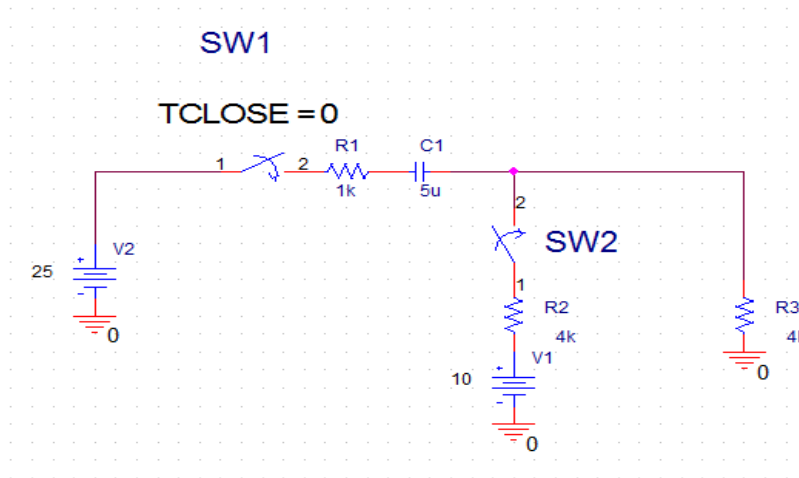


Problem (2-9)


Eng: Hesham Hamdy Gaber

If at $t=0$, SW1 is closed and SW2 is opened, and at $V_o = 10\text{ V}$, SW2 is closed. Calculate $V_o(t)$, $V_c(t)$, and $i(t)$ for the circuit shown in the following figure.



Analytical Solution

@ $t = 0$ the circuit will be

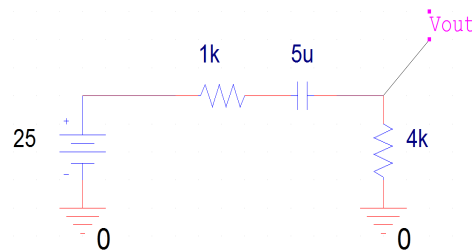

$$\tau = R \cdot C = (1+4)\text{k} \cdot 5\mu = 25\text{m sec.}$$

$$V_o = V_{cc} - V_c - I \cdot R1$$

$$\text{@ } t = 0 \quad V_c = 0,$$

$$I_o = 25 / (1+4) = 5\text{mA.}$$

$$V_o = 25 \cdot 4 / 5 = 20\text{V}$$

$$\text{@ } V_o = 10\text{V}, \quad I = 10 / 4 = 2.5\text{ mA} \rightarrow t = ?$$

$$V_c(t = ?) = V_{cc} - 10 - (2.5\text{ mA}) \cdot (1\text{ k}\Omega) = 25 - 10 - 2.5 = 12.5\text{ V}$$

$$V_c(t = ?) = 12.5 = 25 - [25 - 0]e^{-t/25\text{m}}$$

$$12.5 = 25 e^{-t/25m}$$

$$0.5 = e^{-t/25m}$$


$$\ln(0.5) = -t/25m$$

$$0.693 * 25 = t$$


$$t = 17.33 \text{ m sec}$$

this indicate that after $t = 17.33 \text{ m sec}$ SW2 will open


@ $t = 17.33 \text{ msec}$

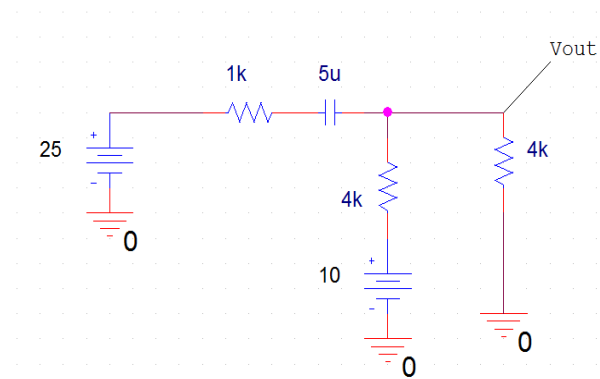

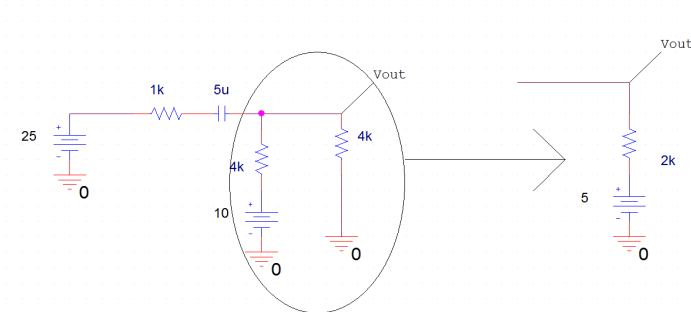By taking thevenin to the last two branches as shown



so the circuit will be

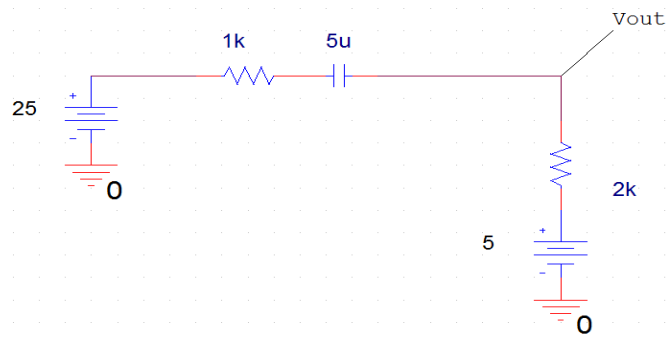

for this conditions


$$V_c(\infty) = 20V$$


$$V_c(\text{initial value for this case}) = 12.5V$$

$V_o(\infty) = 5V$ because the current in the circuit at ∞ equal to zero

So we can draw the waveforms as mentioned in the question

ORCAD SOLUTION

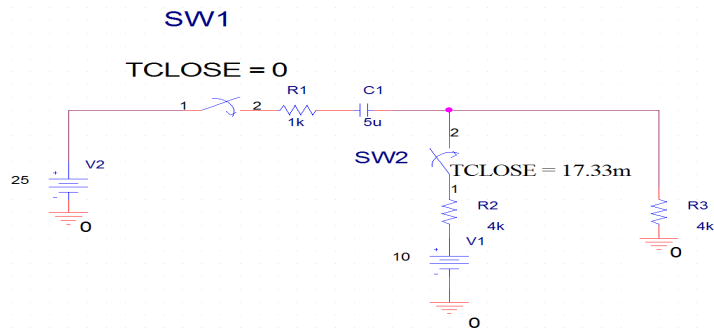

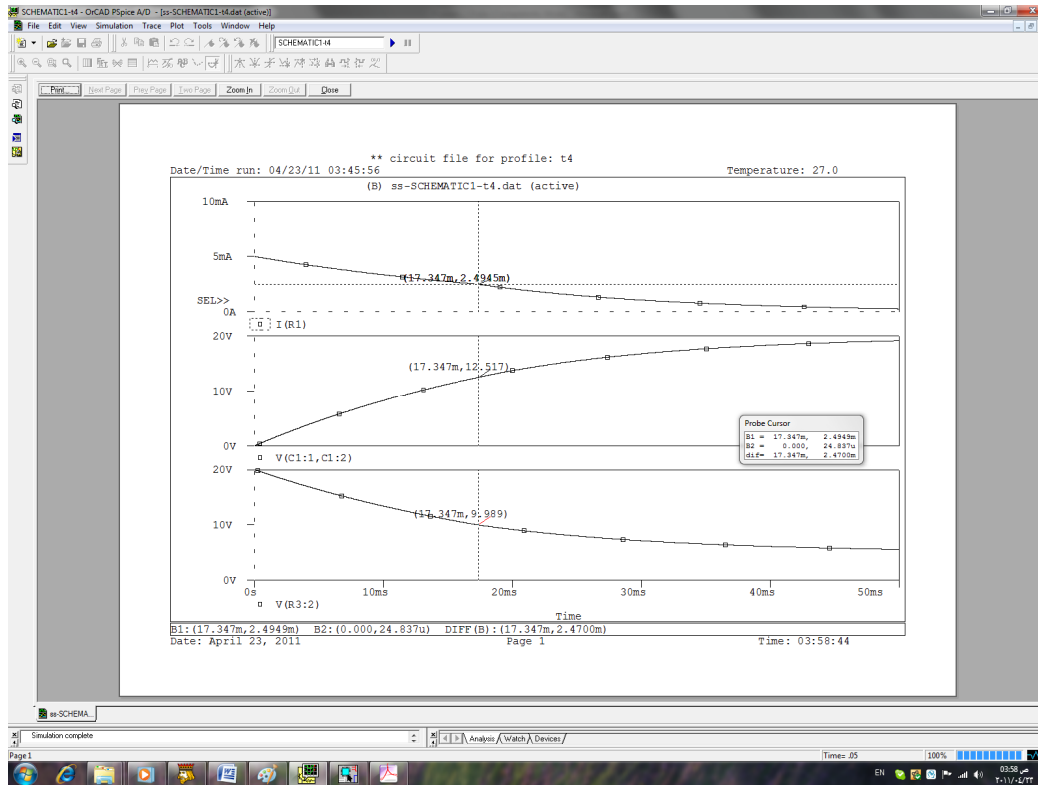

The waveforms as follows: $I(t)$, $V_c(t)$, $V_o(t)$

Note: the breakpoint at $t=17.33\text{ms}$ is not so clear because the two slopes of the two curves are so close to each other but you can check it by zooming at the breakpoint.