



Arab Academy For Science and Technology

Dr./ Mohamed Hassan

Note: The figures, text, etc.. included in slides are borrowed from various books, websites, authors' pages, and other sources for academic purposes only. The authors do not claim any originality.

Term Roadmap :



- Introduction to Signal Processing
- Differentiating and Integrating Circuits (OpAmps)
- Clipping and Clamping Circuits
- Design of analog filters
- Sinusoidal Oscillators
- Multivibrators
- Sampling and Quantization techniques of analog signals
- DACs and ADCs
- Data Acquisition Systems
- Introduction to discrete time transform and DSP
- The Z transform
- Design of Digital Filters



Text Books


Microelectronic circuits

Adel S. Sedra

Kenneth C. Smith

Sixth Edition, copyright 2011

by Oxford University Press

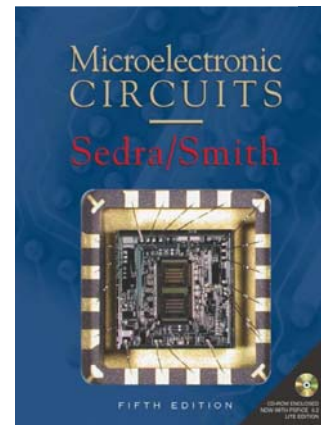


Analog and Digital Signal Processing

H. Baher

Second Edition, copyright 2001

by John Wiley & Sons, LTD

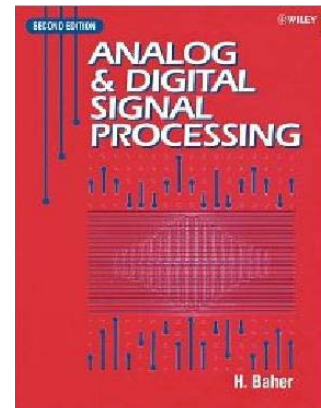

Dr. Mohamed Hassan

Sinusoidal Oscillators

The use of positive feedback that results in a feedback amplifier having closed-loop gain $|A_f|$ greater than 1 and satisfies the phase conditions will result in operation as an oscillator circuit. An oscillator circuit then provides a varying output signal. If the output signal varies sinusoidally, the circuit is referred to as a *sinusoidal oscillator*. If the output voltage rises quickly to one voltage level and later drops quickly to another voltage level, the circuit is generally referred to as a *pulse* or *square-wave oscillator*.

Dr. Mohamed Hassan

Structure of Sinusoidal Oscillators

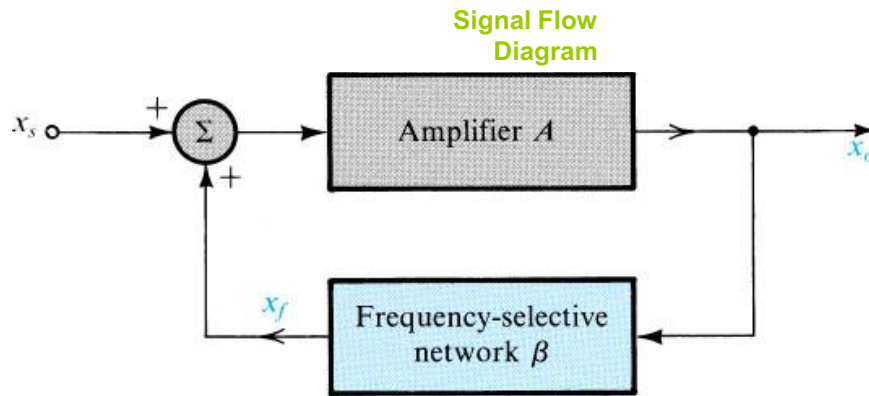


Figure 13.1 basic structure of a sinusoidal oscillator

$$x_f = \beta x_o$$

$$x_i = x_s + x_f$$

$$\therefore A_f(s) \equiv \frac{x_o}{x_s} = \frac{A(s)}{1 - A(s)\beta(s)} = \frac{A(s)}{1 - L(s)} \rightarrow \begin{array}{l} A(s)\beta(s) \dots \text{Loop Gain} \\ A(s) \dots \text{Gain of open-loop amplifier} \\ (s) \dots \text{Freq.-dep. Feedback } \beta \text{ factor} \end{array}$$

Structure of Sinusoidal Linear Oscillators

Characteristic Equation :

$$1 - L(s) = 0$$

$$L(s) = L(j\omega_o) = A(j\omega_o)\beta(j\omega_o) = 1 \angle 0$$

Barhausen Criterion

At a certain frequency f_o , the magnitude of the loop gain is equal to **ONE** & phase of the loop gain is **ZERO** (180 degrees for amount of Feedback due to -ve sign), the circuit thus produces an output for **NO** input (i.e. **OSCILLATES** at this frequency)

Sinusoidal Linear Oscillators

OP AMP RC Osc.

1. Wien-Bridge Oscillator
2. Phase-Shift Oscillator
3. Quadrature Oscillator


LC & Crystal Osc.

1. Colpitts Oscillator
2. Hartley Oscillator
3. Crystal Oscillator

Dr. Mohamed Hassan

I. OP AMP RC Osc.

1- Wien-Bridge Oscillator

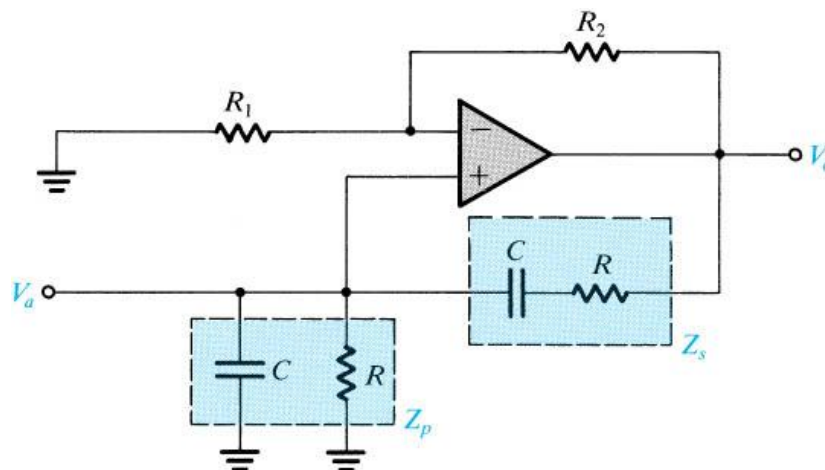

Dr. Mohamed Hassan

1. Wien-Bridge Oscillator

$$L(s) = \left[1 + \frac{R_2}{R_1} \right] \frac{Z_p}{Z_p + Z_s}$$

where $Z_p = \frac{R}{1+sRC}$, $Z_s = R + \frac{1}{sC} = \frac{1+sRC}{sC}$


$$\therefore L(s) = \left[1 + \frac{R_2}{R_1} \right] \frac{\frac{R}{1+sRC}}{\frac{R}{1+sRC} + \frac{1+sRC}{sC}} = \frac{1+sRC}{R} \frac{\left[1 + \frac{R_2}{R_1} \right]}{\left[\frac{R}{1+sRC} + \frac{1+sRC}{sC} \right]}$$

$$= \frac{\left[1 + \frac{R_2}{R_1} \right]}{1 + \left[\frac{1}{sRC} + 2 + sRC \right]} = \frac{1 + \frac{R_2}{R_1}}{3 + sRC + \frac{1}{sRC}}$$

$$\therefore L(j\omega) = \frac{1 + \frac{R_2}{R_1}}{3 + j(\omega RC - \frac{1}{\omega RC})}$$

i.e. $\omega_o = \frac{1}{RC}$

Dr. Mohamed Hassan

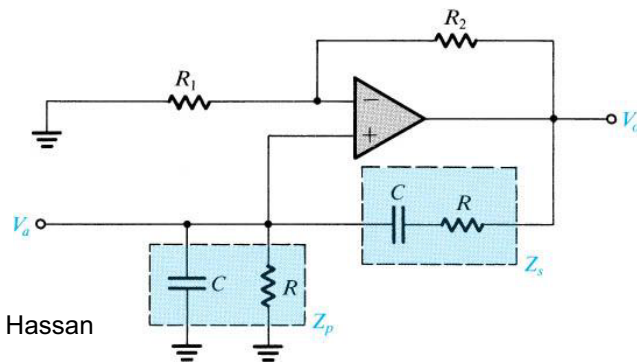

2. Phase-Shift Oscillator


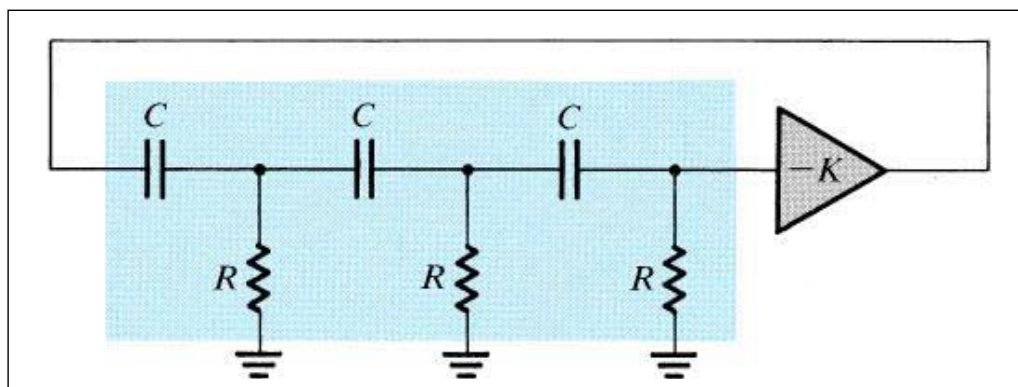
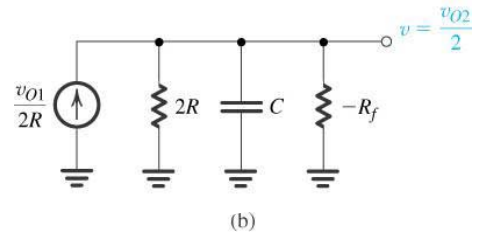


Figure 13.7 A phase-shift oscillator

$$L(j\omega) = \frac{\omega^2 C^2 R R_f}{4 + j(3\omega CR - 1/\omega CR)} \Rightarrow \omega_o = \frac{1}{\sqrt{3}RC}$$

Dr. Mohamed Hassan

3. Quadrature Oscillator

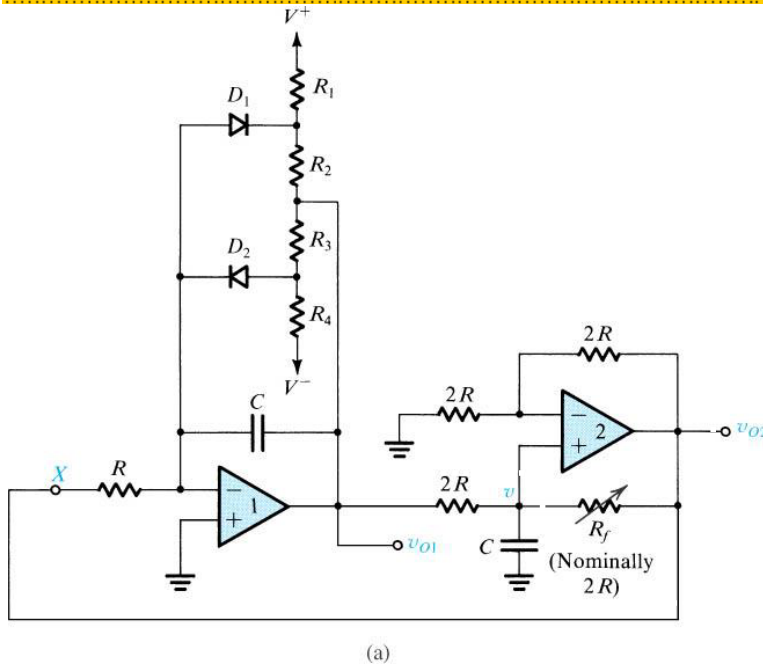

$$L(s) = \frac{V_{o2}}{V_x} = -\frac{1}{sC^2R^2} \Rightarrow \omega_o = \frac{1}{RC}$$

Figure 13.9 (a) A quadrature-oscillator circuit. (b) Equivalent circuit at the input of op amp 2.

II. LC Oscillators

- 1- Used in frequency ranges from 100 KHz to hundreds of MHz
- 2. Higher Q than RC type oscillators

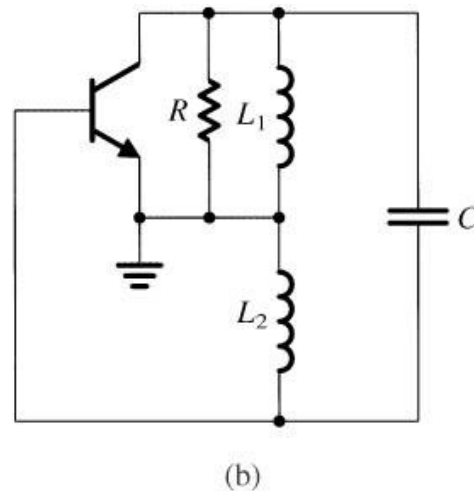
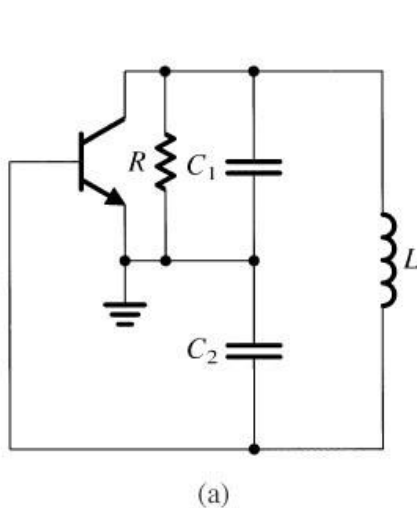


Figure 13.12 Two commonly used configurations of LC-tuned oscillators:

(a) Colpitts

(b) Hartley.

II. 1 Colpitts Oscillator

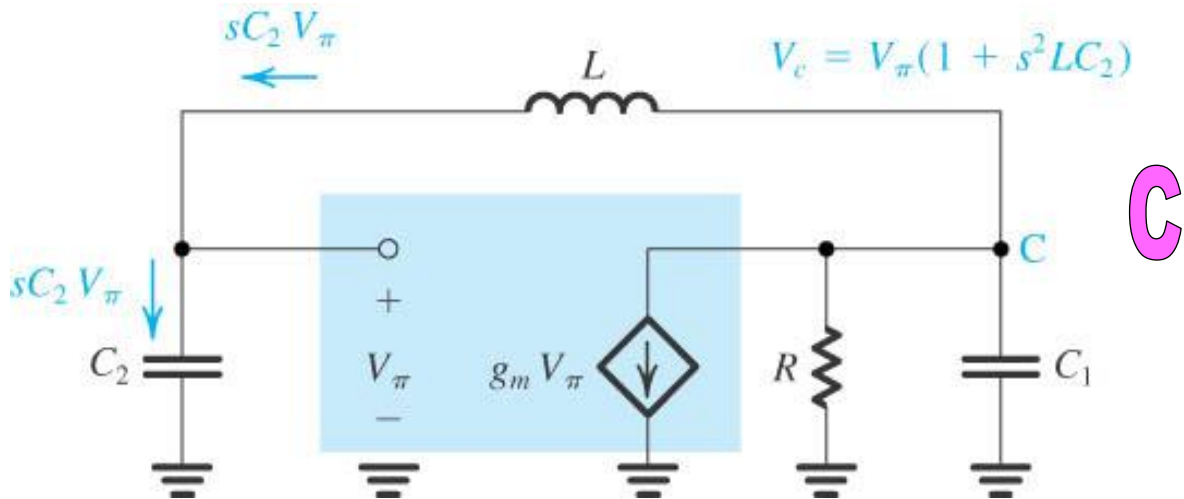


Figure 13.13 Equivalent circuit of the Colpitts oscillator of Fig. 13.12(a).

To simplify analysis, C_{μ} and r_{π} are neglected.

C_{π} to be part of C_2 ,

r_o is included in R (inductor losses).


II. 1 Colpitts Oscillator (cntd)

$$I_L + I_{transistor} + I_{R//C_1} = 0$$

$$\frac{V_{\pi}}{Z_{C_2}} + g_m V_{\pi} + \frac{V_c}{R // C_1} = 0$$

$$sC_2 V_{\pi} + g_m V_{\pi} + \left(\frac{1}{R} + sC_1 \right) (1 + s^2 LC_2) V_{\pi} = 0$$
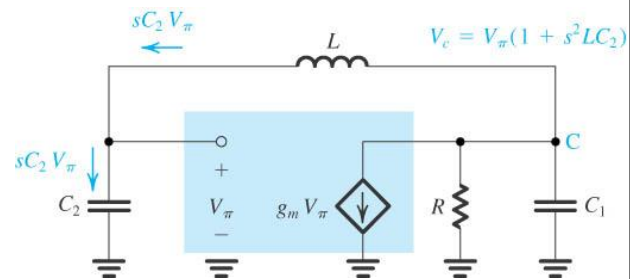
$$\left(g_m + \frac{1}{R} - \frac{\omega^2 LC_2}{R} \right) + j \left(\omega(C_2 + C_1) - \omega^3 LC_1 C_2 \right) = 0$$




$$\text{Imaginary} = 0 \Rightarrow \omega_o = \frac{1}{\sqrt{L \left(\frac{C_1 C_2}{C_1 + C_2} \right)}}$$

$$\text{RealPart} = 0 \Rightarrow \frac{C_2}{C_1} = g_m R$$

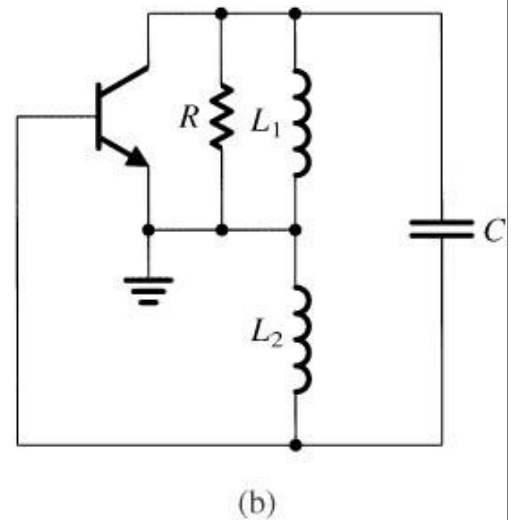II. 2 Hartley Oscillator

$$\text{Imaginary} = 0 \Rightarrow \omega_o = \frac{1}{\sqrt{(L_1 + L_2)C}}$$

$$\text{RealPart} = 0 \Rightarrow \frac{L_2}{L_1} = g_m R$$



Dr. Mohamed Hassan

III. Crystal Oscillators

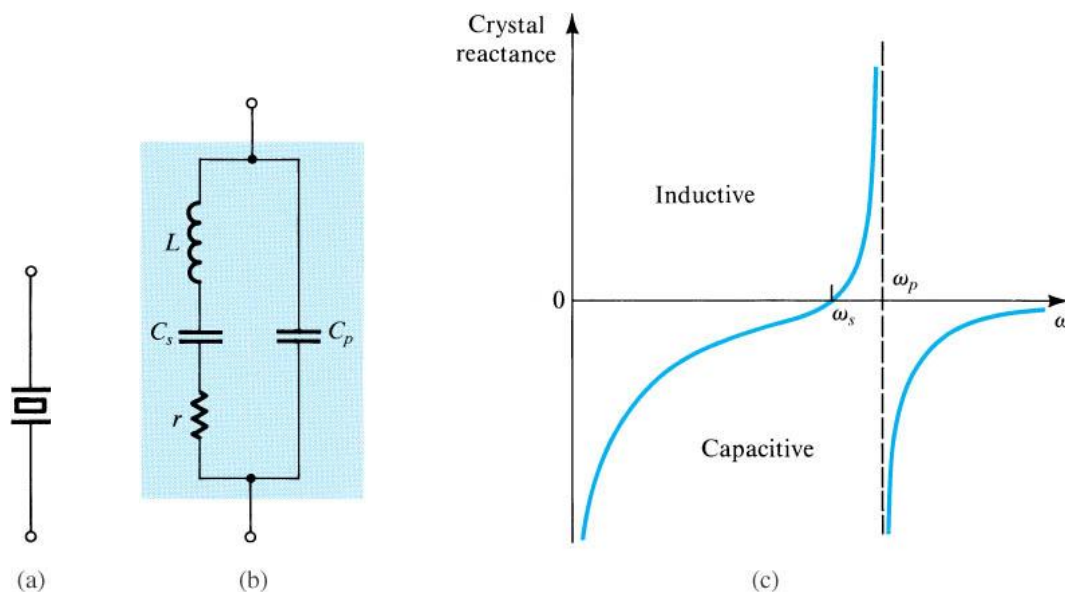


Figure 13.15 A piezoelectric crystal. (a) Circuit symbol. (b) Equivalent circuit. (c) Crystal reactance versus frequency [note that, neglecting the small resistance r , $Z_{\text{crystal}} = jX(\omega)$]. Dr. Mohamed Hassan



Thank you

Dr. Mohamed Hassan