



**Arab Academy for Science & Technology
and Maritime Transport – Cairo Branch
College of Engineering & technology
Mechatronics department**



**EC534 – Analog and Digital Signal processing
Revision sheet**

1. For the series diode configuration of Fig.1 determine V_D , V_R and I_D .

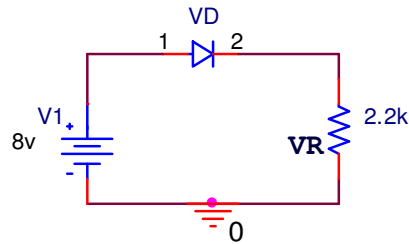


Figure 1

2. For the parallel diode configuration of Fig.2 determine V_D , I_1 , I_{D1} and I_{D2}

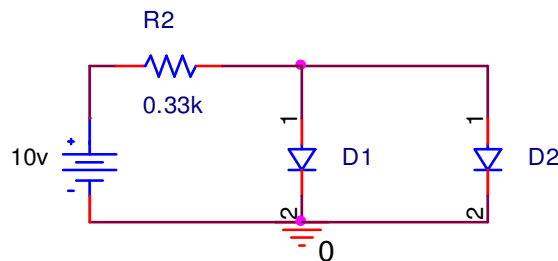


Figure 2

3. for the network of Fig.3
Solve for D.C and A.C analysis, if $V_{BE}=0.7V$ and $\beta = 100$
- a. Determine r_x
 - b. find Z_i
 - c. calculate Z_o
 - d. determine A_v

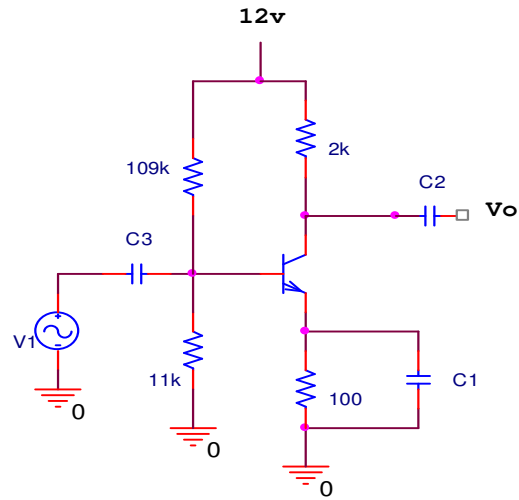


Figure 3

4. What input must be applied to the input of Fig.4 to result in an output of 2.4v?

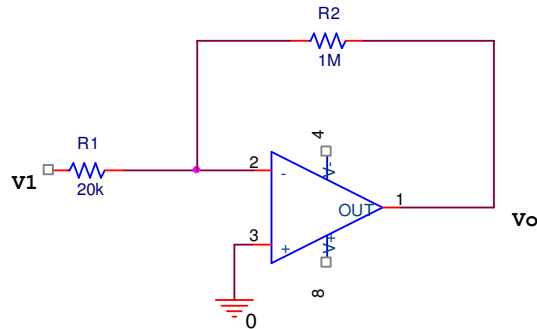


Figure 4

Assignment:

5. Determine I_E , I_B , I_C and V_C for fig.5

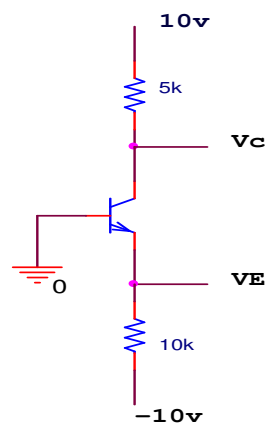


Figure 5

6. Calculate the output voltage of the circuit in Fig.6 for $R_f = 68k\Omega$

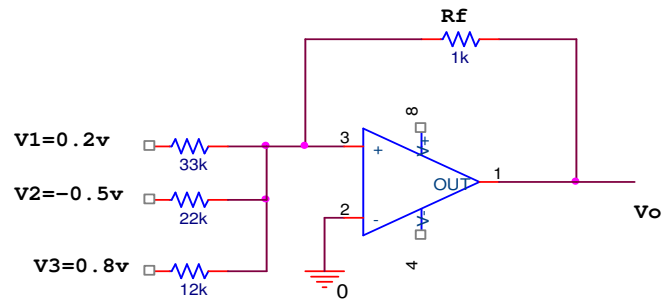


Figure 6

7. Calculate the output voltages V_2 and V_3 in the circuit of Fig.7

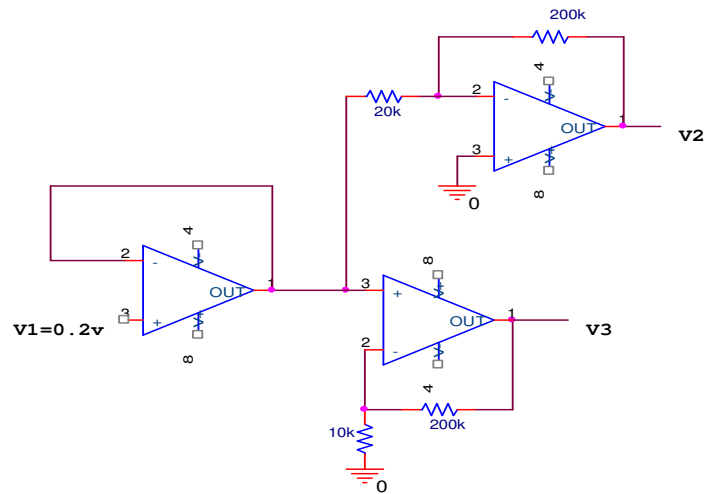


Figure 7