



**Arab Academy for Science & Technology and Maritime Transport**  
**College of Engineering and Technology**

**Department** : Electronics and Communications

**Course** : Electronic Measurements

**Course Code:** EC410

**Lecturer** : Prof. Dr. Ashraf Mamdouh

**GTA** : Eng. Mohamed Gamal

## Problem Set #3

### Operational Amplifiers

- An input signal with 50 V (dc) is amplified using two cascaded identical inverting operational amplifiers with  $R_1 = 50\text{k}\Omega$  and  $R_2 = 100\text{k}\Omega$ .
  - Draw the connection.
  - Calculate the total gain in dB.
  - Calculate the input and output signal levels for each block.
- An input signal with 10 V (dc) is amplified using two cascaded identical non-inverting operational amplifiers with  $R_1 = 50\text{k}\Omega$  and  $R_2 = 100\text{k}\Omega$  (feed back resistance).
  - Draw the connection.
  - Calculate the total gain in dB.
  - Calculate the input and output signal levels for each block.
- Given two signals  $v_1$  and  $v_2$ , draw a connection using an operational amplifier that yields:
  - $v_2 - v_1$
  - $(4/3)v_2 - 3v_1$ .
- Given that  $v_i(t) = 10\text{mv}$  for  $1\text{ms} \leq t \leq 4\text{ms}$  and zero otherwise. This signal is fed to an integrator operational amplifier with  $R = 100\text{k}\Omega$ . What is the value of the capacitor  $C$  to get an output voltage of  $-40\text{mv}$  at  $t = 4\text{ms}$ . Sketch the input and the output voltages.
- The input signal shown in Figure is fed to a differentiator with  $R = 1\text{k}\Omega$  and  $C = 10\mu\text{F}$ . Write expressions and draw the input and the output signals.
- A LPF operational amplifier with  $R_i = 5\text{k}\Omega$ ,  $R_f = 10\text{k}\Omega$  and  $C_f = 1\text{nF}$ , is fed with a signal  $v_i(t) = 10\cos(2\pi 5000t) + 15\cos((2\pi 16000t) + 5\cos((2\pi 50000t))$ . Write an approximate expression for the output signal from the LPF operational amplifier. Calculate the gain in dB at frequency 1000 Hz. Comment on the result.
- A HPF operational amplifier with  $R_i = 5\text{k}\Omega$ ,  $R_f = 10\text{k}\Omega$ , and  $C_i = 1\text{nF}$ , is fed with a signal  $v_i(t) = 10\cos(2\pi 100t) + 15\cos((2\pi 32000t) + 5\cos((2\pi 80000t))$ . Write an approximate expression for the output signal from the HPF operational amplifier. Calculate the gain in dB at frequency 100 Hz. Comment on the result.

