



Department : Electronics and Communications

Course : Electronic Measurements

Course Code: EC410

Lecturer : Prof. Ashraf Mamdouh

GTA : Eng. Mohamed Gamal

Problem Set #4

Oscillators and LF Generators

- 1- A 5 V sin wave is fed from Wein bridge oscillator to the attenuator circuit illustrated in Fig.1. Calculate the values of R_a , R_b , and R_c to give output voltage ranges of 0-0.1 V and 0-1 V. The current drained from the oscillator is 1 mA and the input bias current to the operational amplifier is 500 nA.

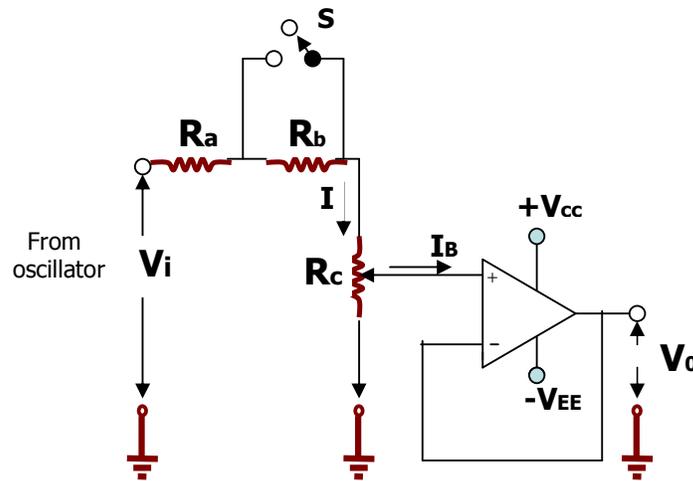


Fig. 1

- 2- A Wein bridge oscillator circuit, as shown in Fig. 2, has the following components: R changes from $500\ \Omega$ to $5\ k\Omega$ and $C = 300\ nF$. Calculate the minimum and maximum output frequency. Explain how can you increase the frequency range by a factor of 20 (assume the same values of R).

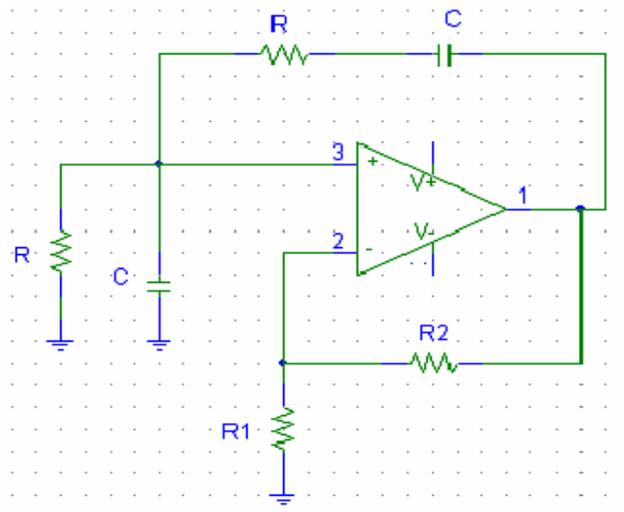


Fig. 2

- 3- A Wein bridge oscillator circuit, as in Fig. 2, has the following components: R changes from 200Ω to $3k\Omega$ and $C = 250nF$. Calculate the minimum and maximum output frequency and determine the new capacitor values required to give $f_{\max} = 300\text{ Hz}$.
- 4- The Wein bridge circuit modification is shown in Fig. 3 has $R_1 = 400\Omega$, $R_3 = 330\Omega$, and $R_4 = 470\Omega$. Determine the minimum and maximum values of the gain.

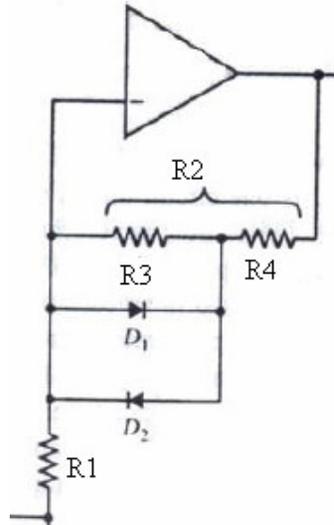


Fig. 3

- 5- For the LF square wave converter shown in Fig. 4, what is the function of the diodes. What is the value of the output voltage when:
- The zener diodes have $V_z = 7.1\text{ V}$ and the diodes are Silicon types ($V_D = 0.7\text{ V}$).
 - The zener diodes have $V_z = 6.6\text{ V}$ and the diodes are Germanium types ($V_D = 0.5\text{ V}$).
 - The zener diodes have $V_z = 7\text{ V}$ and the diodes are ideal diodes ($V_D = 0\text{ V}$).


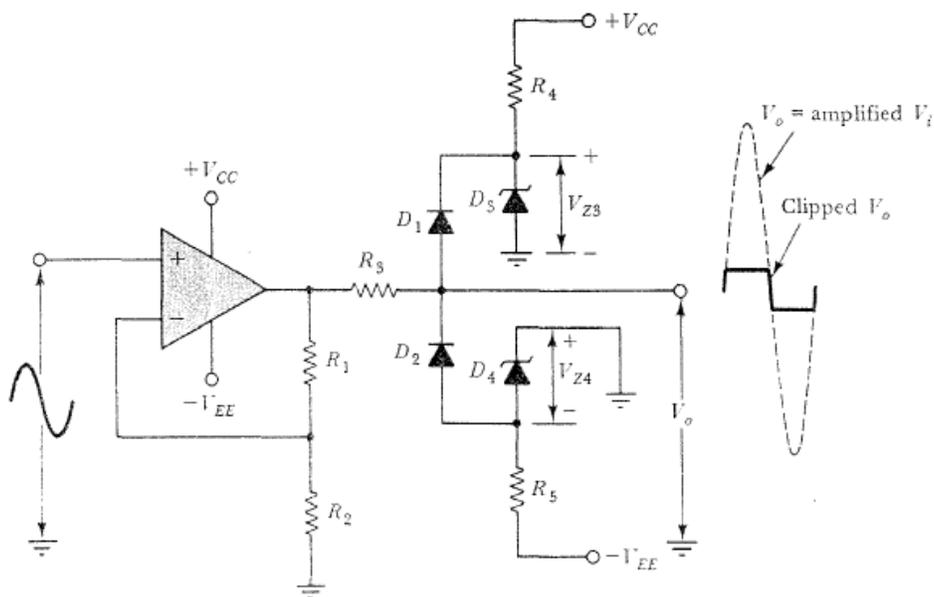



Fig. 4

6- For the shown block diagram:

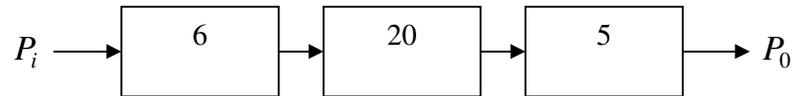

- What is the absolute value of the total gain.
- What is the value of the total gain in dB.
- If $P_i = 2W$, what is the input and the output power in dBm for each block

7- For the shown block diagram:

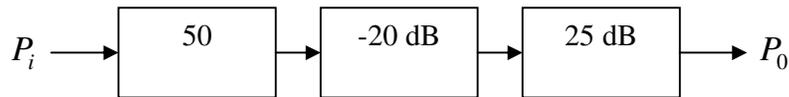

- What is the absolute value of the total gain.
- What is the value of the total gain in dB.
- If $P_i = 4W$, what are the input and the output power in dB for each block.
- Repeat (c) in case of dBm.