



**COLLEGE OF ENGINEERING & TECHNOLOGY**

**Department: Electronics and Communications Engineering**

**Lecturer: Associate Prof. Dr. Hussein H. M. Ghouz**

**Course: Microwave Technology**

**Course Code: EC546**

**Date : Sat., Dec., 13, 2014**

**Time : 1 Hours**

**Total Marks : 20**

**12<sup>th</sup> Exam (Fall-2014/2015)**

**Question No. 1: (6-Mark):**

Design an Equal-ripple **3-order bandpass filter** with the following specifications: **(3-Mark)**  $f_o=6.0$  GHz,  $Z_o=50 \Omega$ ,  $bandwidth=2000$  MHz, and  $Ripple=0.5dB$ . The coefficients of **ER LP** proto-type filter is given by :{ **1.000, 1.5963, 1.0967, 1.5963, 1.000**}. Select the proper method to implement the designed filter and then, sketch roughly its frequency response **(3-Mark)**

**Question No. 2: (14-Mark):**

- (a) Discuss the different implantation methods of the most commonly used direction couplers in practice, then, define and explain: coupling factor, directivity, and isolation **(4-Mark)**
- (b) A resistive T-junction power divider circuit has a ratio of “**a:b**” power division. Assume, the source impedance is  $Z_s$ , and the characteristic impedance of each arm is  $Z_o$  ( $Z_s > Z_o$ ). Find the optimum series resistance values of each arm such that all ports are matched. Compute the magnitude and phase of the S-parameters and the power loss in this case **(5-Mark)**
- (c) A single-hole waveguide directional coupler is designed to operate in dominant mode TE<sub>10</sub>. Assume rectangular waveguides are filled with a dielectric material of  $\epsilon_r=10.0$  and the desired coupling factor is **15.0** dB. The required output ports are as follows: **port#2**(through), **port#3** (isolated), and **port#4** (coupled). Assume, the waveguides cross section is  $axb=1.070 \times 0.430$ cm<sup>2</sup>. Select the correct frequency from the following frequencies to design the required directional coupler: { $f_o=3.0, f_o=6.0, f_o=22.0$ } GHz, and then derived a closed form equations for location and radius of the hole aperture **(5-Mark)**

**Bonus Question: (6-Mark additional to added to the 7<sup>th</sup> Grade):**

A single section coupled line coupler with a coupling factor of 15 dB, a system impedance of **50 Ω**, and a center frequency of **5 GHz**, is desired to be realized on FR-4 substrate edge-coupled microstrip configuration, with  $\epsilon_r=4.4$  and  $d=1.6$  mm. Find the necessary strip widths and separation using the Impedance-Table given below. Assume the voltage source is  $V_o=10$  volt peak-to-peak and the line lengths is  $\lambda/4$ , find the power at each port. Sketch roughly the directivity and the coupling from **4** to **6** GHz.

		$Z_{oe}$				$Z_{oe}$			
		W/d				S/d			
		54	57	60	63	54	57	60	63
$Z_{00}$	40	2.0	1.9	1.8	1.7	0.05	0.06	0.07	0.08
	43	1.7	1.6	1.5	1.4	0.08	0.09	0.10	0.21
	46	1.5	1.5	1.4	1.3	0.10	0.15	0.20	0.25
	49	1.4	1.3	1.2	1.1	0.15	0.20	0.30	0.35
	51	1.3	1.2	1.1	1.0	0.20	0.25	0.28	0.38

**P.T.O**

## Formula Sheet

$$A_{10}^+ = -jTr_o^3 \left( T^+ \sin^2(\pi S/a) - T^0 \cos^2(\pi S/a) \right)$$

$$A_{10}^- = -jTr_o^3 \left( T^- \sin^2(\pi S/a) - T^0 \cos^2(\pi S/a) \right)$$

$$T = \omega A / P_{10} \quad T^0 = \left( 4\pi^2 \mu_o / Z_{10}^2 \beta^2 a^2 \right)$$

$$k_{cmn} = \sqrt{(m\pi/a)^2 + (n\pi/b)^2}$$

$$\epsilon_o = 10^{-09} / (36\pi) \text{ F/m}$$

$$T^+ = \left( 2\epsilon / 3 - 4\mu_o / 3Z_{10}^2 \right)$$

$$T^- = \left( 2\epsilon / 3 + 4\mu_o / 3Z_{10}^2 \right)$$

$$P_{10} = ab / Z_{10} \quad k = \omega / v$$

$$Z_{10} = k\eta / \beta \quad \beta = \sqrt{k^2 - k_c^2}$$

$$\mu_o = 4\pi \times 10^{-07} \text{ H/m}$$

Filter Type	Frequency Transformation	Impedance Scaling
<b>LPF</b>  <b>BPF</b>	$L_k \longrightarrow L_k = L_k / (\omega_o \Delta)$ $C_k \longrightarrow C_k = \Delta / (\omega_o L_k)$ $C_k \longrightarrow L_k = \Delta / (\omega_o C_k)$ $C_k \longrightarrow C_k = C_k / (\omega_o \Delta)$ $\Delta = (\omega_2 - \omega_1) / \omega_o$	$L_k \longrightarrow L_k R_o$ $C_k \longrightarrow C_k / R_o$
	$(1/\Delta)(\omega/\omega_o - \omega_o/\omega) \longrightarrow \omega$	