



COLLEGE OF ENGINEERING & TECHNOLOGY

Department: Electronics and Communications Engineering

Lecturer: Associate Prof. Dr. Hussein H. M. Ghouz

Course: Microwave Technology

Course Code: EC546

Date : Thur. Jan., 15, 2015

Time : 2 Hours

Total Marks : 40

Answer the Following Questions (Fall-2014/2015)

Question No. 1: (15-Mark):

Three bipolar-junction transistors have the following scattering parameters at $f_0=6.0$ GHz:

BJT1: $S_{11}=0.55 \angle -140^\circ$, $S_{21}=2.6 \angle 50^\circ$, $S_{12}=0.01 \angle 60^\circ$, $S_{22}=0.6 \angle -65^\circ$

BJT2: $S_{11}=0.75 \angle -110^\circ$, $S_{21}=1.5 \angle 25^\circ$, $S_{12}=0.33 \angle 50^\circ$, $S_{22}=-0.85 \angle -45^\circ$

BJT3: $S_{11}=1.20 \angle -80^\circ$, $S_{21}=2.4 \angle 55^\circ$, $S_{12}=0.44 \angle 35^\circ$, $S_{22}=0.75 \angle -115^\circ$

- Select one of the given **BJT** elements to design a microwave amplifier having a maximum gain of **12.0** dB at f_0 **(8-Mark)**
- Design the input-output matching circuits using a single shunt-stub terminated by short circuit (use smith chart paper) **(4-Mark)**
- If S_{12} is assumed to be approximate zero, find the maximum transducer power gain that can be achieved by the selected transistor in this case **(3-Mark)**

Question No. 2: (15-Mark):

- Draw the general block-diagram of a microwave transistor-oscillator. Discuss the required conditions to have steady-state-oscillation **(3-Mark)**
- Check the stability of a GaAs-FET transistor characterized by the following scattering parameters at $f_0=6.0$ GHz: $S_{11}=0.9 \angle -90^\circ$, $S_{21}=6.1 \angle 80^\circ$, $S_{12}=0.5 \angle 70^\circ$, $S_{22}=0.6 \angle -40^\circ$. Draw the input and output stability circles on the smith-chart paper. Is it possible to use this transistor as an oscillator at $f_0=6.0$ GHz **(6-Mark)**
- Explain the basic idea of microwave mixer, and then state the different types of microwave mixers. Draw the general circuit diagram of a microwave balanced mixer circuit, and then, explain its principles of operation **(6-Mark)**

Question No. 3: (5-Mark):

- Design a maximally flat (**MF**) bandpass filter with the following specifications: **(2-Mark)**

$$f_0=3.0 \text{ GHz}, Z_0=50 \Omega, \text{ and bandwidth}=1000 \text{ MHz}$$

The coefficients of **MF LP** proto-type filter is given by :{ **1.0, 2.0, 1.0, 1.0**}

- Implement the designed filter and then, sketch roughly its frequency response **(3-Mark)**

Question No. 4: (5-Mark):

A single-hole waveguide directional coupler is designed to operate in dominant mode TE_{10} . Assume rectangular waveguides are filled with a dielectric material of $\epsilon_r=10.0$ and the desired coupling factor is **20.0** dB. The required output ports are as follows: **port#2**(through), **port#3** (isolated), and **port#4** (coupled). Assume, the waveguides cross section is $axb=1.070 \times 0.430 \text{ cm}^2$. Select the correct frequency from the following frequencies to design the required directional coupler: { $f_0=6.0, f_0=10.0, f_0=14.0$ } GHz, and then derived a closed form equations for location and radius of the hole aperture

P.T.O



Formula Sheet

Filter Type	Frequency Transformation	Impedance Scaling
BPF	$L_k \longrightarrow L_k = L_k / (\omega_0 \Delta)$ $C_k = \Delta / (\omega_0 L_k)$	$L_k \longrightarrow L_k R_o$ $C_k \longrightarrow C_k / R_o$
	$C_k \longrightarrow L_k = \Delta / (\omega_0 C_k)$ $C_k = C_k / (\omega_0 \Delta)$	
	$\Delta = (\omega_2 - \omega_1) / \omega_0$	
	$(1/\Delta)(\omega/\omega_0 - \omega_0/\omega) \longrightarrow \omega$	

Stability Test and Circles

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|} \quad |\Delta| = |S_{11}S_{22} - S_{12}S_{21}| \quad C_L = \frac{(S_{22} - \Delta S_{11}^*)^*}{|S_{22}|^2 - |\Delta|^2} \quad R_L = \frac{|S_{12}S_{21}|}{|S_{22}|^2 - |\Delta|^2}$$

$$C_S = \frac{(S_{11} - \Delta S_{22}^*)^*}{|S_{11}|^2 - |\Delta|^2} \quad R_S = \frac{|S_{12}S_{21}|}{|S_{11}|^2 - |\Delta|^2} \quad \Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} \quad \Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S}$$

Amplifier Design Equations

$$G_{Tmax} = G_S G_o G_L \quad G_S = \frac{1}{1 - |\Gamma_S|^2} \quad G_o = |S_{21}|^2 \quad G_L = \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2} \quad \Gamma_S = \frac{B_1 \pm \sqrt{B_1^2 - 4|C_1|^2}}{2C_1}$$

$$\Gamma_L = \frac{B_2 \pm \sqrt{B_2^2 - 4|C_2|^2}}{2C_2} \quad B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 \quad B_2 = 1 + |S_{22}|^2 - |S_{11}|^2 - |\Delta|^2$$

$$C_1 = S_{11} - \Delta S_{22}^* \quad C_2 = S_{22} - \Delta S_{11}^*$$

Coupler Design Equations

$$A_{10}^+ = -jTr_o^3 \left(T^+ \sin^2(\pi S/a) - T^o \cos^2(\pi S/a) \right) \quad T^+ = \left(2\varepsilon/3 - 4\mu_o/3Z_{10}^2 \right) \quad \varepsilon_o = 10^{-09} / (36\pi) \text{ F/m}$$

$$A_{10}^- = -jTr_o^3 \left(T^- \sin^2(\pi S/a) - T^o \cos^2(\pi S/a) \right) \quad T^- = \left(2\varepsilon/3 + 4\mu_o/3Z_{10}^2 \right) \quad \mu_o = 4\pi \times 10^{-07} \text{ H/m}$$

$$T = \omega A / P_{10} \quad T^o = \left(4\pi^2 \mu_o / 3Z_{10}^2 \beta^2 a^2 \right) \quad P_{10} = ab / Z_{10} \quad k = \omega / v$$

$$k_c = \sqrt{(m\pi/a)^2 + (n\pi/b)^2}$$

$$Z_{10} = k\eta / \beta \quad \beta = \sqrt{k^2 - k_c^2}$$

GoodLuck