



Arab Academy for Science & Technology
and Maritime Transport – Cairo Branch
College of Engineering & technology
Electronics & Communication Engineering Department



EC443 EM Transmitting Media

Instructor: Prof. Esmat Abdel Fattah
Tutorial : Eng. Sherif Eldyasti

Problems Set #3

"Graphical Solution for Transmission Line Problems"

P3.1 A lossless line having an air dielectric has a characteristic impedance of 400Ω . The line is operating at 200 MHz and $Z_{in} = 200 - j200 \Omega$. Use analytical methods & the Smith chart to find: (a) S, (b) Z_L , if the line is 1 m long; (c) the distance from the load to the nearest voltage maximum.

P3.2 The normalized load on a lossless transmission line is $2 + j1$. the wavelength of the signal is 20 m. Let $l = 20$ m and make use of the Smith chart to find: (a) the shortest distance from the load to a point at which $Z_{in} = r_{in} + j0$, where $r_{in} > 1$; (b) Z_{in} at this point. (c) the line is cut at this point and the portion containing Z_L is thrown away. A resistor $r = r_{in}$ of part (a) is connected across the line. What is the S on the remainder of the line? (d) what is the shortest distance from this resistor to a point at which $Z_{in} = 2 + j1$?

P3.3 A 300Ω transmission line is short-circuited at $z = 0$. A voltage maximum equals 10 v is found at $z = -25$ cm, and the minimum voltage equals zero at $z = -50$ cm. Use the Smith chart to find Z_L (WITH THE SHORT CIRCUIT REPLACED BY THE LOAD) if the voltage readings are:

- (a) $V_{max} = 12$ v at $z = -5$ cm, and $V_{min} = 5$ v.
- (b) $V_{max} = 17$ v at $z = -20$ cm and $V_{min} = 0$ v.

Homework Assignment:

H3.1 The characteristic admittance ($Y_0 = 1/Z_0$) of a lossless transmission line is 20 mS. The line is terminated in a load $Y_L = 40 - j20$ mS. Make use of the Smith chart to find: (a) S. (b) Y_{in} if $l = 0.15\lambda$; (c) the distance in wavelengths from Y_L to the nearest voltage maximum.

H3.2 The wavelength on a certain lossless transmission line is 10 cm. If the normalized input impedance is $Z_{in} = 1 + j2$, use the Smith chart to determine:

- (a) S
- (b) Z_L if the line length is 12 cm.
- (c) X_L if $Z_L = 2 + jX_L$ where $X_L > 0$.

Good Luck ☺