



**Arab Academy for Science & Technology  
and Maritime Transport – Cairo Branch  
College of Engineering & technology  
Electronics & Communication Engineering Department**



**EC443 EM Transmitting Media**

**Instructor: Prof. Esmat Abel Fattah  
Tutorial : Eng. Sherif El Dyasti**

**Problems Set #1**

**P1.1** The parameters of a certain transmission line operating at  $6 \times 10^8$  rad/s are :  
 $L=0.4 \mu\text{H/m}$ ,  $C=40 \text{ Pf/m}$ ,  $G=80 \text{ mS/m}$ , and  $R=20 \Omega/\text{m}$ .

- (a) Find  $\beta$ ,  $\gamma$ ,  $\alpha$ , and  $Z_0$ .  
(b) If a voltage wave travels 20 m down the line, what percentage of the original wave amplitude remains, and by how many degrees is its phase shifted.

**P1.2** A lossless transmission line having  $Z_0=120 \Omega$  is operating at  $\omega=5 \times 10^8$  rad/s. If the velocity on the line is  $2.4 \times 10^8$  m/s, find:

- (a)  $L$ ; (b)  $C$ ; (c) Let the load impedance be represented by the inductance of  $0.6 \mu\text{H}$  in series with a  $100 \Omega$  resistance. Find the reflection coefficient & VSWR.

**P1.3** Two characteristics of a certain lossless transmission line are  $Z_0=50 \Omega$  and  $\gamma=j 0.2 \pi$  1/m at  $f=60 \text{ MHz}$ : (a) Find  $L$  &  $C$  for the line. (b) A load impedance has a value of  $60+j80 \Omega$  is located at  $z=0$ . What is the shortest distance from the load to a point at which  $Z_{in}=R_{in}+j0$  ?

---

***HomeWork Assignment#1:***

**H1.1** The propagation constant of a lossy transmission line is  $1+j 2$  1/m, and the characteristic impedance is  $20 \Omega$  at  $\omega=1 \text{ Mrad/s}$ . Find  $L, C, R$ , and  $G$  for the line.

**H1.2** 1.2 A lossless transmission line with  $Z_0=60 \Omega$  is being operated at 60 MHz. The velocity on the line is  $3 \times 10^8$  m/s. If the line is short-circuited at the  $z=0$ , find  $Z_{in}$  at  $z=$ :  
(a) -1 m; (b) -2 m; (c) -2.5 m; (d) -1.25m

Good Luck ☺