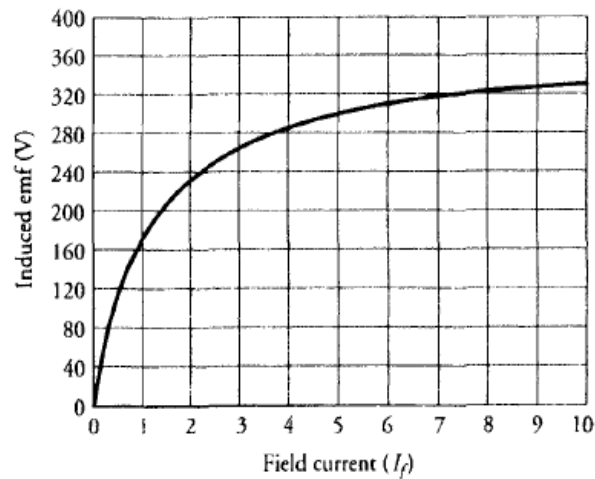


Sheet 6**DC Generators**

1. A 240-kW, 240-V, 6-pole, 600-rpm, separately excited generator is delivering the rated load at the rated voltage. The generator has  $R_a = 0.01 \Omega$ ,  $R_f = 30 \Omega$ ,  $V_f = 120 \text{ V}$ ,  $N = 500$  turns per pole, and  $P_r = 10 \text{ kW}$ . Its magnetization curve is given below. Determine:
- The induced emf at full load.
  - The power and the torque developed.
  - The applied torque and efficiency
  - The external resistance in the field winding.



2. A 50 kW, 250 V shunt generator has an armature and field winding resistances of  $0.02 \Omega$  and  $150 \Omega$  respectively. The friction, windage and core losses are 1500 W at full load. Calculate:
- Load current
  - Field current
  - Armature current
  - Voltage regulation
  - Shunt field copper loss
  - Armature copper loss
  - Efficiency

3. A 50 KW, 250 series generator has an armature resistance of  $0.02 \Omega$  and a series field resistance of  $0.045 \Omega$ . The friction, windage, and core losses are 2.5 KW. At rated load calculate:
- Armature current
  - Induced emf
  - Armature copper losses
  - Total copper losses
  - Generator efficiency
4. A 10 KW, 230V self-excited shunt generator, delivering rated load, has an armature circuit voltage drop that is 6 percent of the terminal voltage and a shunt field current equal to 4 percent of the rated load current. Calculate the resistance of the armature circuit and that of the field circuit.
5. The OCC of a DC shunt generator when driven at 400 rpm is as follows:

Field current (A)	2	3	4	5	6	7	8	9
E.M.F (V)	110	155	186	212	230	246	260	271

Find:

- The emf to which the machine will excite when the field resistance is  $34 \Omega$ .
  - The critical value of the shunt field resistance.
  - The critical speed when the field circuit resistance is  $34 \Omega$ .
  - The additional resistance required in the field circuit to reduce the emf to 220 V.
6. The following figures were obtained from an open circuit test on a shunt generator driven at 1000 rpm.

Field current (A)	1	1.5	2	2.5	3
E.M.F (V)	104	119	130	138	145

If the field resistance is  $50 \Omega$ , find graphically:

- The terminal voltage on open circuit when the speed is 1000 rpm.
- The terminal voltage on open circuit when the speed is 750 rpm.
- The additional field resistance required so that the machine builds up 89 V when the speed is 750 rpm.