

Electrical Machines II

Week 4: Transformer Efficiency, Maximum Efficiency Criterion and Phasor diagram


Transformer Losses and Efficiency

Transformer efficiency is defined as

$$\eta = \frac{P_{out}}{P_{in}} \times 100\% \qquad \eta = \frac{P_{out}}{P_{out} + P_{loss}} \times 100\%$$

Types of losses incurred in a transformer:

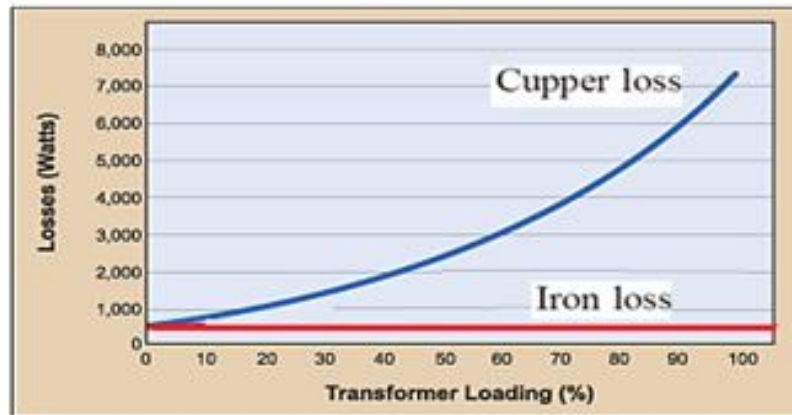- 1- Copper I^2R losses --- Load dependant
- 2- Core losses (hysteresis losses and eddy current losses), also known as no-load losses. Core losses are load **in-** dependent.



Transformer Losses and Efficiency

Transformer efficiency may be calculated using the following:

$$\eta = \frac{V_2' I_2' \cos \varphi_2'}{V_2' I_2' \cos \varphi_2' + I_2'^2 R_{eq} + P_c} \times 100\%$$

For maximum efficiency,

Differentiation of
efficiency with
respect to load
current



$$\frac{d\eta}{dI_2'} = 0$$

$$\frac{d\eta}{dI_2'} = \frac{[V_2' I_2' \cos \varphi_2' + I_2'^2 R_{eq} + P_c] (V_2' \cos \varphi_2') - [V_2' I_2' \cos \varphi_2'] [V_2' \cos \varphi_2' + 2I_2' R_{eq} + 0]}{[V_2' I_2' \cos \varphi_2' + I_2'^2 R_{eq} + P_c]^2} \times 100\%$$

Transformer Losses and Efficiency

$$\frac{d\eta}{dI_2'} = \frac{[V_2' I_2' \cos \varphi_2' + I_2'^2 R_{eq} + P_c](V_2' \cos \varphi_2') - [V_2' I_2' \cos \varphi_2'] [V_2' \cos \varphi_2' + 2I_2' R_{eq} + 0]}{[V_2' I_2' \cos \varphi_2' + I_2'^2 R_{eq} + P_c]^2} \times 100\%$$

$$0 = [V_2' I_2' \cos \varphi_2' + I_2'^2 R_{eq} + P_c](V_2' \cos \varphi_2') - [V_2' I_2' \cos \varphi_2'] [V_2' \cos \varphi_2' + 2I_2' R_{eq} + 0]$$

$$0 = [V_2' I_2' \cos \varphi_2' + I_2'^2 R_{eq} + P_c] - I_2' [V_2' \cos \varphi_2' + 2I_2' R_{eq}]$$

$$-P_c = V_2' I_2' \cos \varphi_2' + I_2'^2 R_{eq} - V_2' I_2' \cos \varphi_2' - 2I_2'^2 R_{eq}$$

$$-P_c = -I_2'^2 R_{eq}$$

$$P_c = I_2'^2 R_{eq}$$

$$I_2' |_{\eta_{\max}} = \sqrt{\frac{P_c}{R_{eq}}}$$

No-load core losses

**For maximum efficiency, at a load such that
copper losses = iron losses**

Transformer Voltage regulation

Because a real transformer has series impedance within it, the output voltage of a transformer varies with the load even if the input voltage remains constant. The voltage regulation of a transformer is the change in the magnitude of the secondary terminal voltage from no-load to full-load.

$$\% \text{Voltage Regulation} = \frac{V_s[\text{no-load}] - V_s[\text{full-load}]}{V_s[\text{full-load}]} \times 100$$

$$\approx \frac{V_p[\text{no-load}] - V_p[\text{full-load}]}{V_p[\text{full-load}]} \times 100$$

Referred to the primary side


Single phase Transformer Phasor diagram

$$V_1 = V_2' + I_2'(R_{eq} + jX_{eq})$$


$$V_1 = V_2' + I_2'R_{eq} + jI_2'X_{eq}$$

Very useful in determining the sources of voltage drop and voltage regulation calculation

Lagging p.f

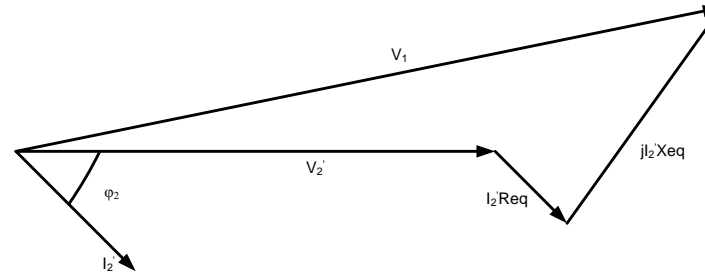

unity p.f

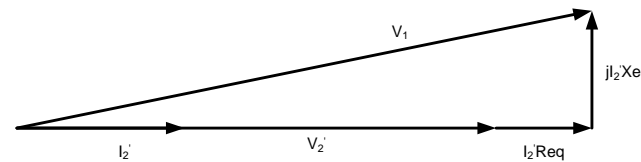

leading p.f

