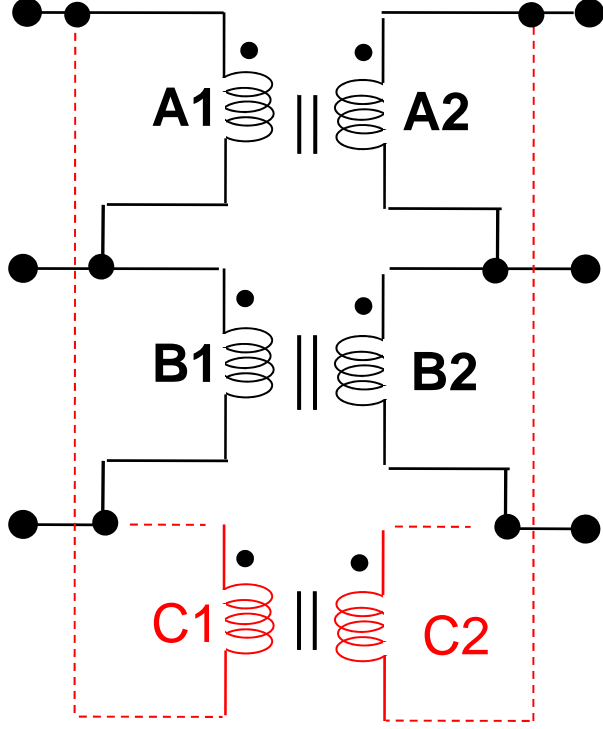


Open delta


Fed from Three phase source



Supplying Three phase load

Open delta


Fed from Three phase source

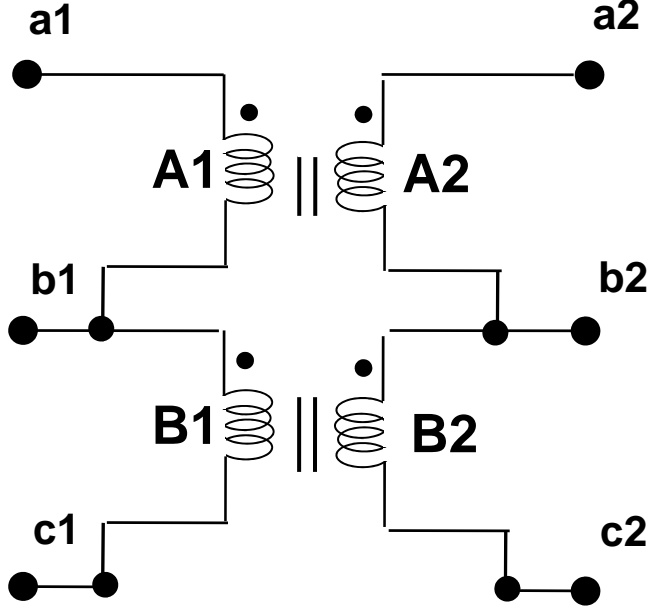


Supplying Three phase load

Open delta

Fed from Three phase source

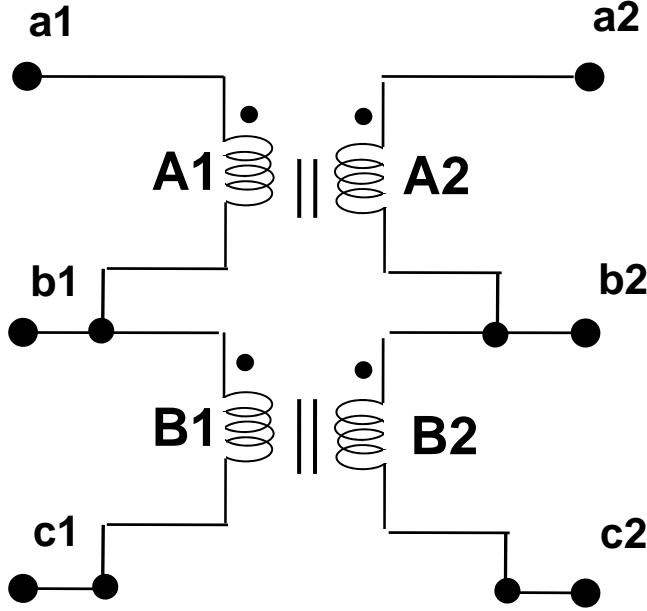


Supplying Three phase load


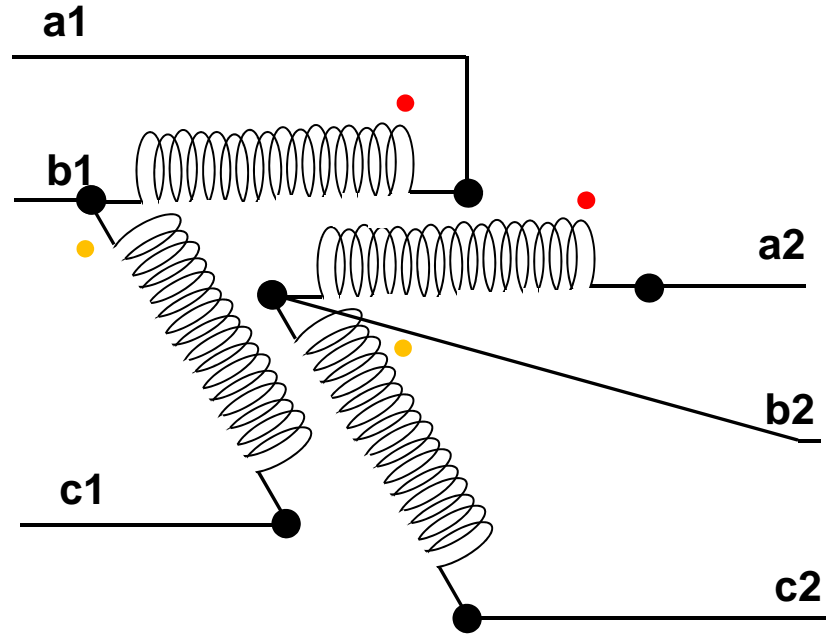


Open delta

Fed from Three phase source

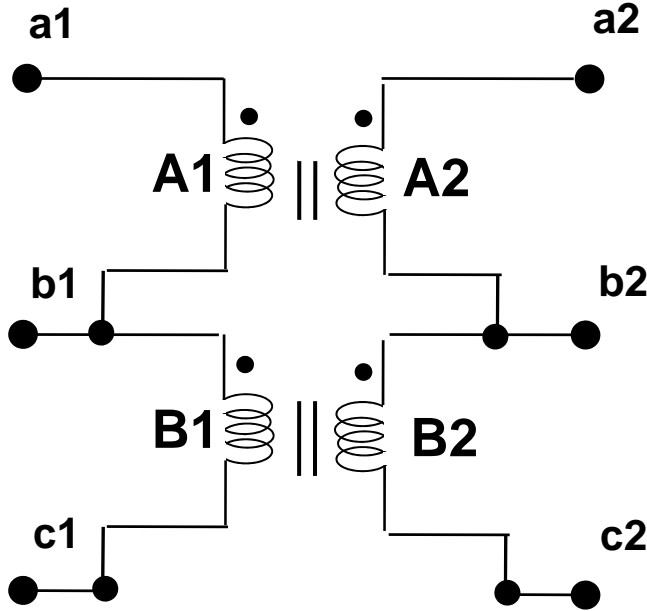


Supplying Three phase load

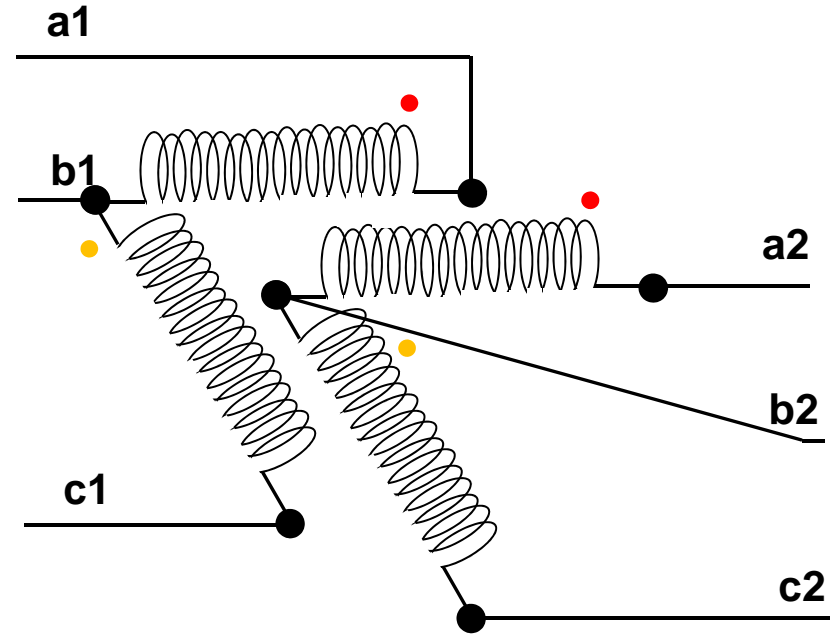
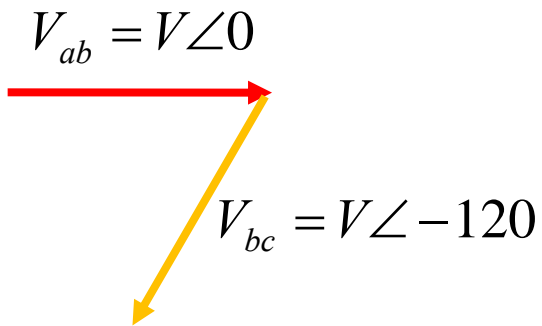


Open delta

Fed from Three phase source

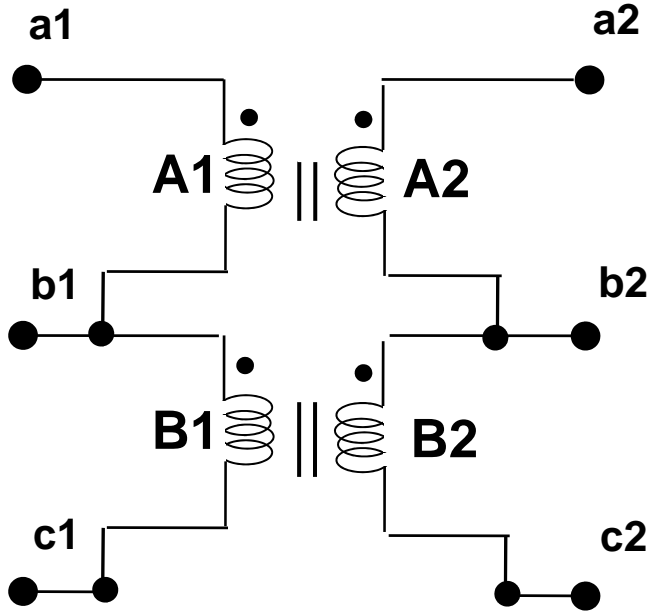


Supplying Three phase load

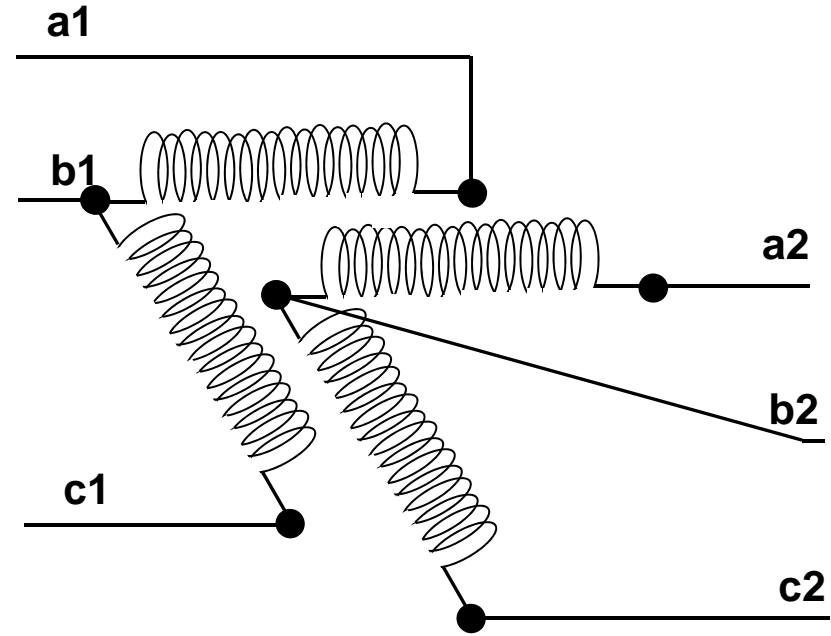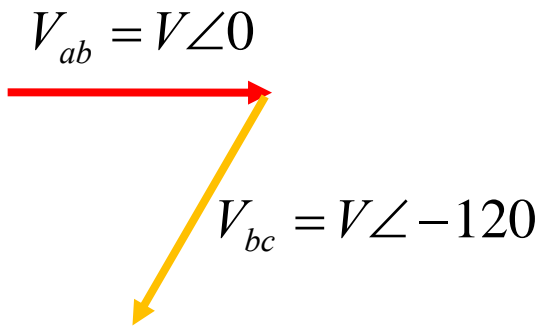



Applying KVL in loop $a_2b_2c_2a_2$:

Open delta

Fed from Three phase source

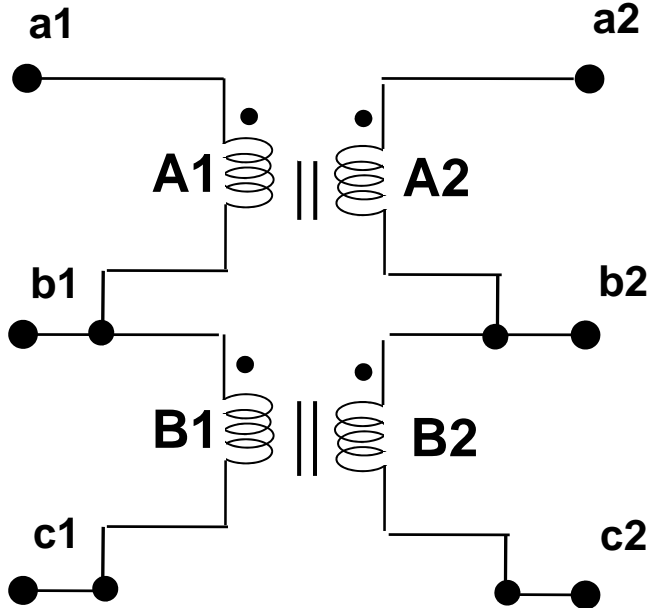



Supplying Three phase load

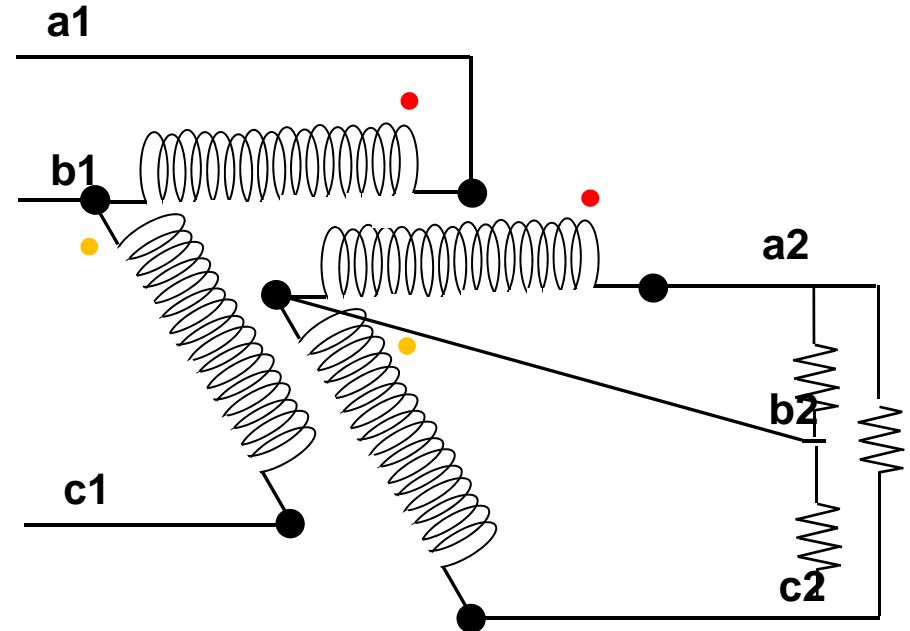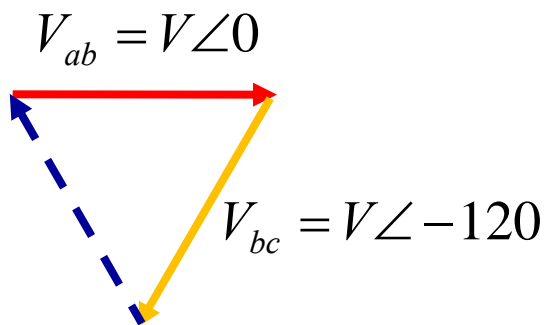



Applying KVL in loop $a_2b_2c_2a_2$:

$$\begin{aligned}
 V_{ca} &= -[V_{ab} + V_{bc}] \\
 &= -V\angle 0 - V\angle -120 \\
 &= -V + 0.5V + j0.866V \\
 &= (0.5 + j0.866)V \\
 &= V\angle 120
 \end{aligned}$$

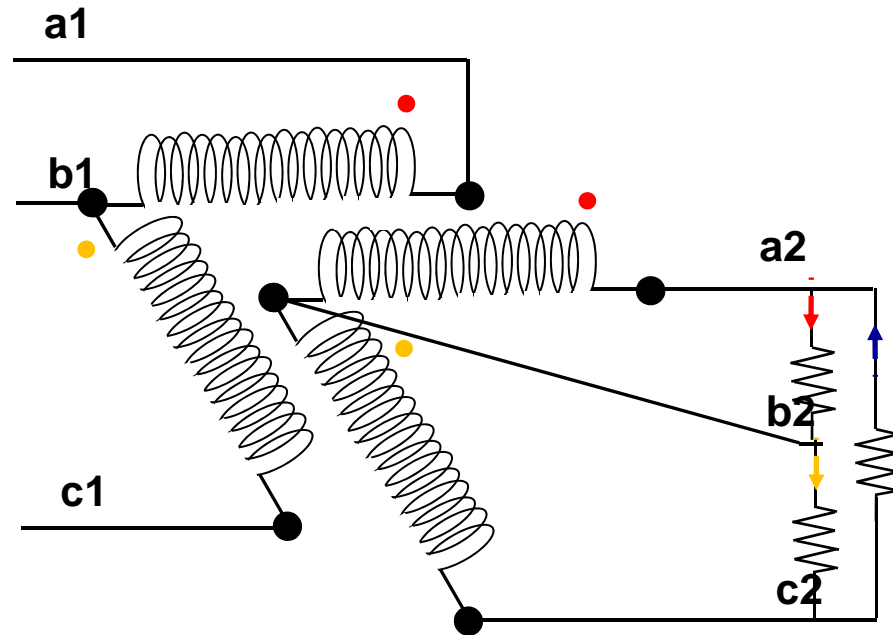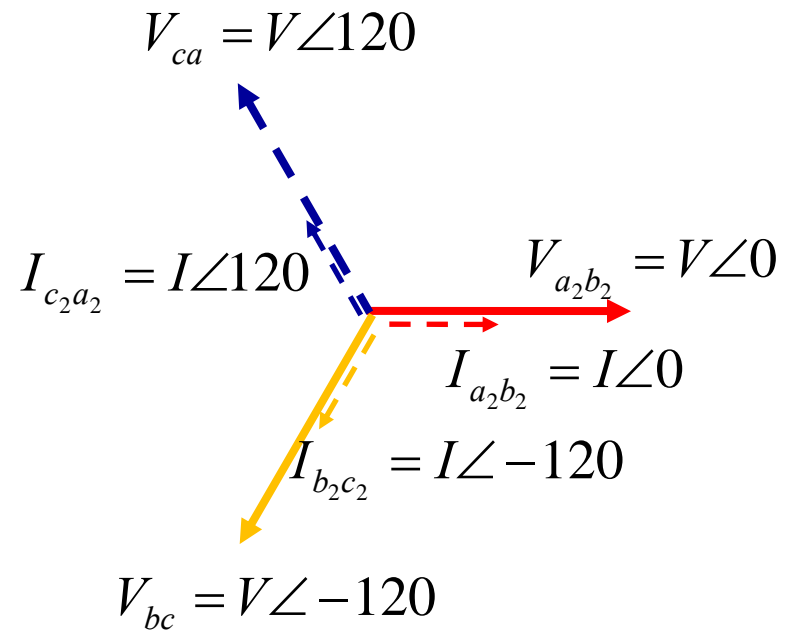
Phase load currents and line currents in open delta:



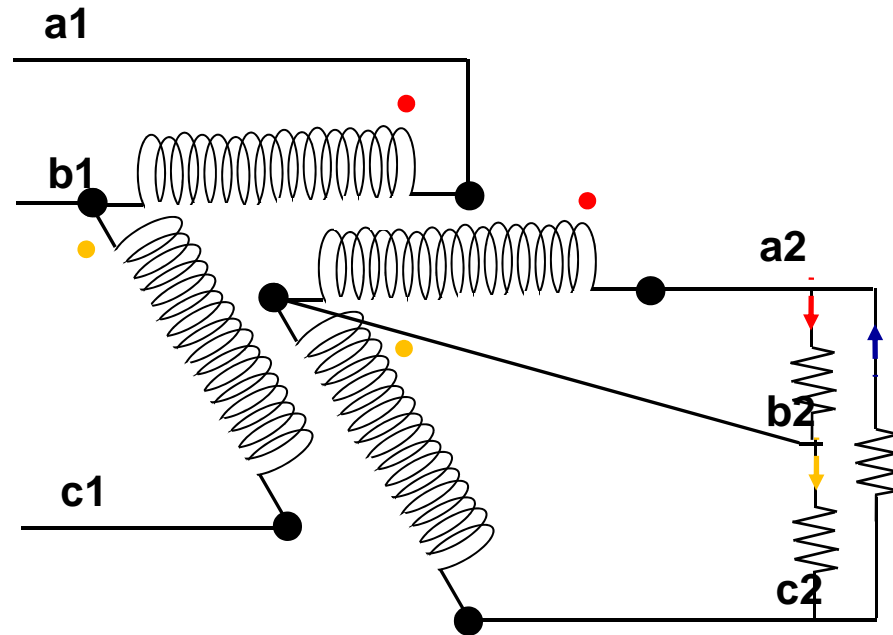
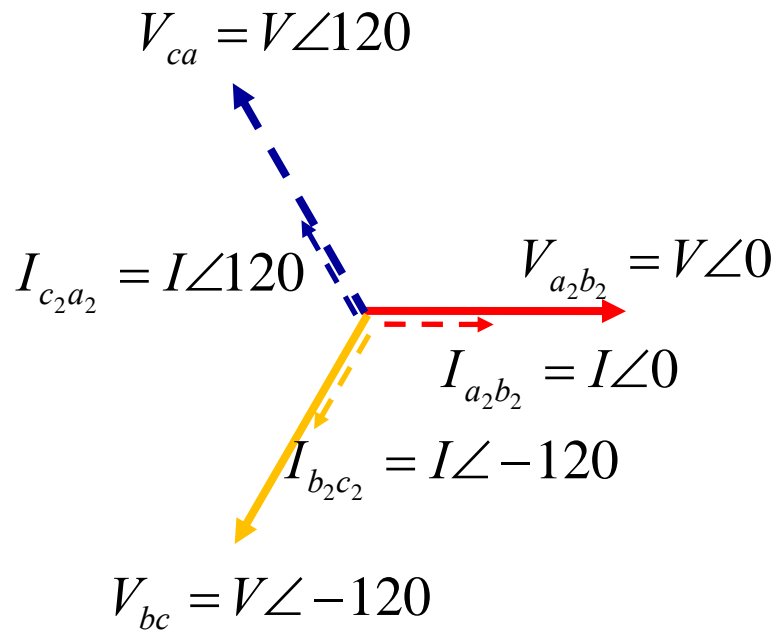
Phase load currents and line currents in open delta:


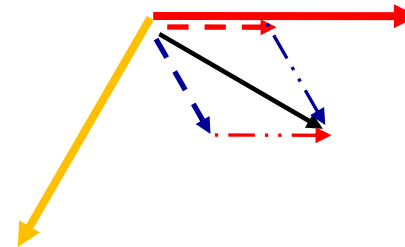
$$I_{a_2} = I_{a_2b_2} - I_{c_2a_2} = I\angle 0 - I\angle 120 = I\angle -30$$



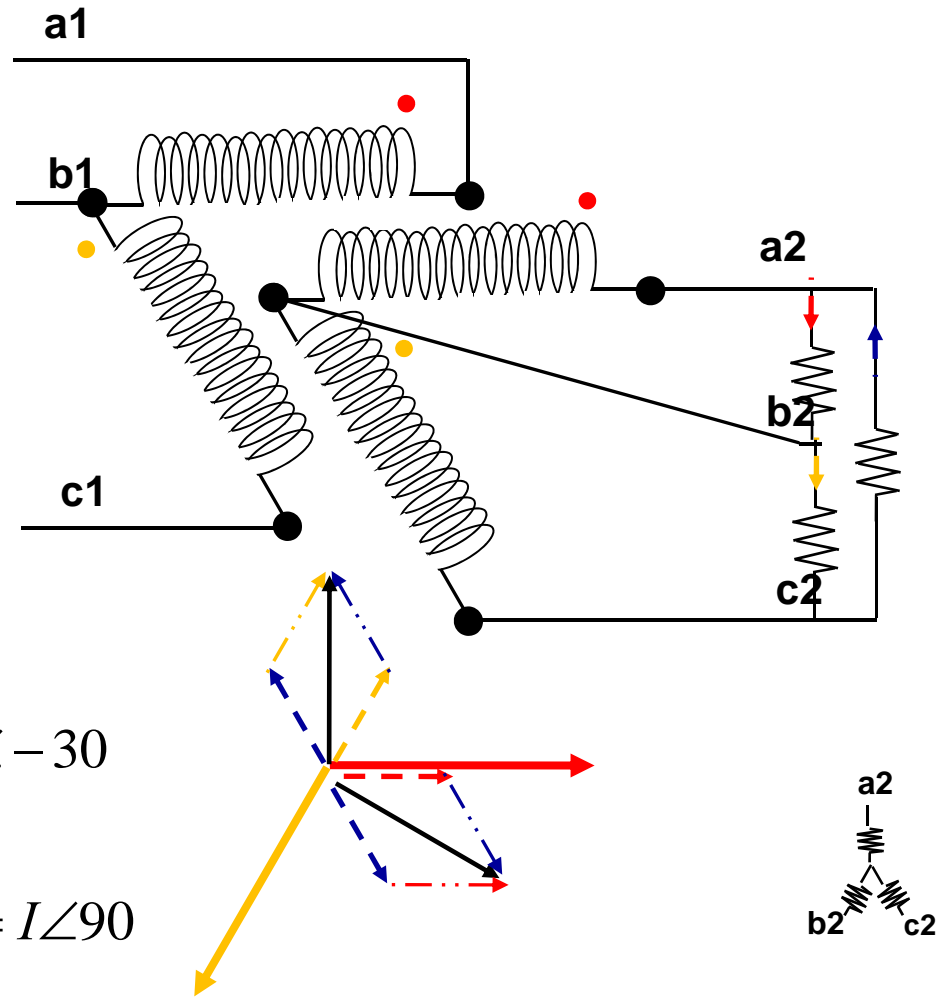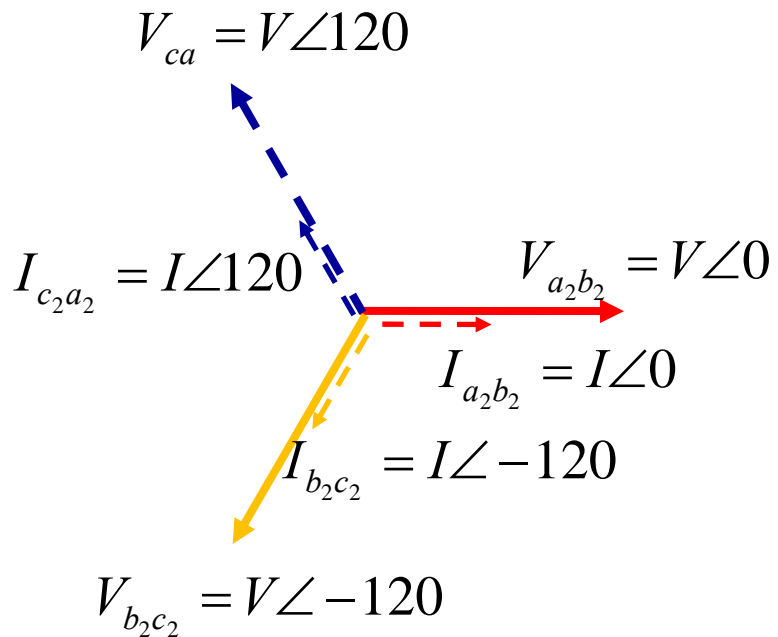Phase load currents and line currents in open delta:



$$I_{a_2} = I_{a_2b_2} - I_{c_2a_2} = I\angle 0^\circ - I\angle 120^\circ = I\angle -30^\circ$$

$$I_{c_2} = I_{c_2a_2} - I_{b_2c_2} = I\angle 120^\circ - I\angle -120^\circ = I\angle 90^\circ$$


N.B.: Line currents have the same values and angles even if the load was star connected

Active & reactive power of open delta:

1st Transformer :

$$V_{a_2b_2} = V \angle 0$$

$$I_{a_2} = I \angle -30$$

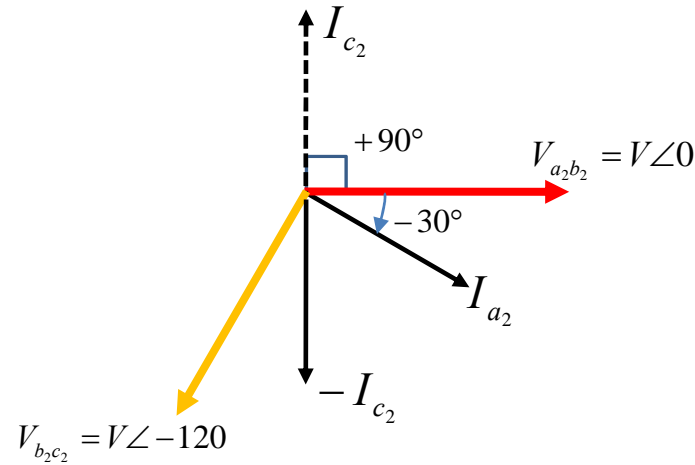


2nd Transformer :

$$V_{bc} = V \angle -120$$

$$I_{c_2} = I \angle 90$$

$$-I_{c_2} = I \angle -90$$
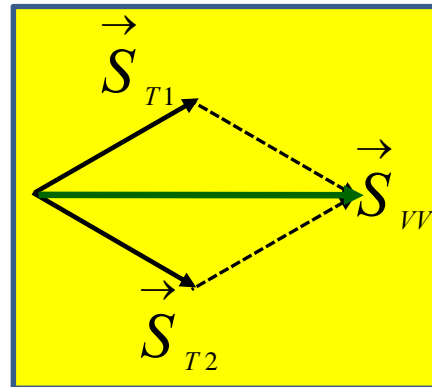
$$\begin{aligned} S_{T1} &= V_{a_2b_2} I_{a_2}^* \\ &= (V \angle 0)(I \angle 30) \\ &= VI \angle 30 \end{aligned}$$




$$\begin{aligned} S_{T2} &= V_{b_2c_2} (-I_{c_2})^* \\ &= (V \angle -120)(I \angle 90) \\ &= VI \angle -30 \end{aligned}$$

$$\vec{S}_{VV} = \vec{S}_{T1} + \vec{S}_{T2} = \sqrt{3} V_{Line} \times I_{Line}$$

$$\vec{Q}_{T1} = -\vec{Q}_{T2} = \frac{1}{2} (V_{Line} \times I_{Line})$$

De-rating of open delta

Fed from Three phase source

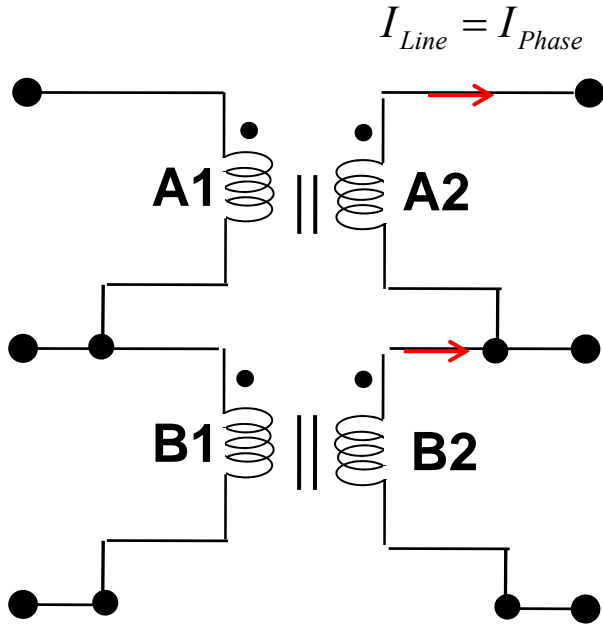


Supplying Three phase load

$$S_{\Delta\Delta} = 3V_{phase} \times I_{Phase}$$

De-rating of open delta

Fed from Three phase source

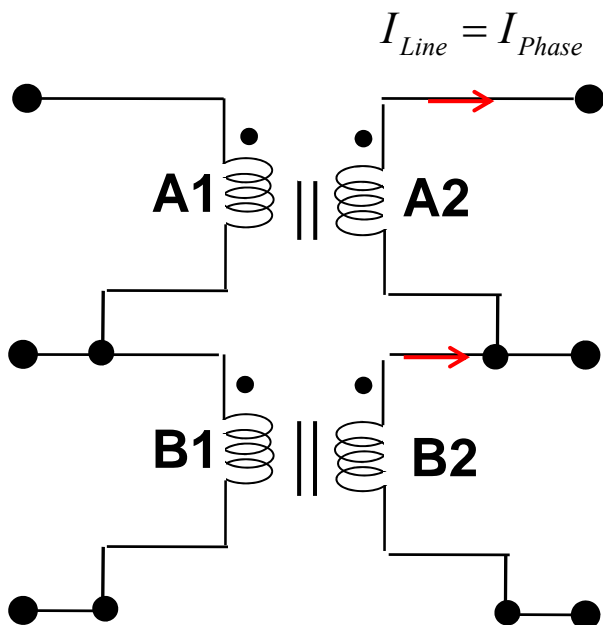

Supplying Three phase load

$$S_{\Delta\Delta} = 3 V_{phase} \times I_{Phase}$$


$$\vec{S}_{vw} = \vec{S}_{T1} + \vec{S}_{T2} = \sqrt{3} V_{Line} \times I_{Line}$$

$$= \sqrt{3} V_{Line} \times (I_{Phase})$$

$$= \sqrt{3} V_{Line} \times I_{Phase}$$

De-rating of open delta

Fed from Three phase source

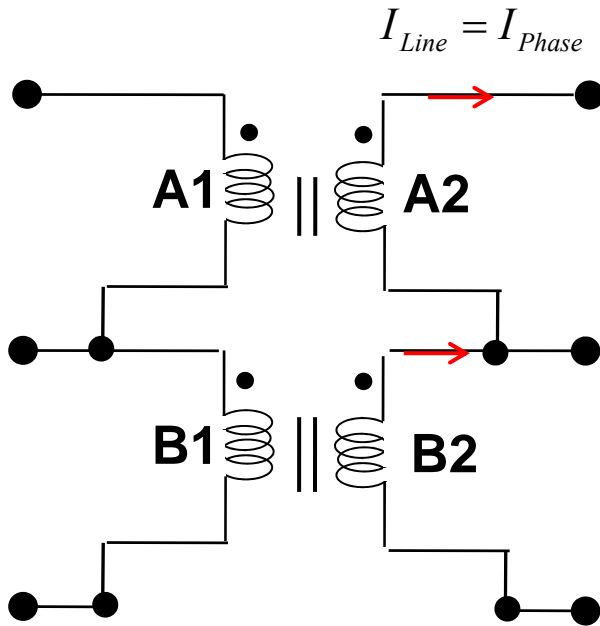

Supplying Three phase load

$$S_{\Delta\Delta} = 3 V_{phase} \times I_{Phase}$$

$$\vec{S}_{VV} = \vec{S}_{T1} + \vec{S}_{T2} = \sqrt{3} V_{Line} \times I_{Line}$$

$$= \sqrt{3} V_{Line} \times (I_{Phase})$$

$$= \sqrt{3} V_{Line} \times I_{Phase}$$

$$\therefore \frac{S_{VV}}{S_{\Delta\Delta}} \approx \frac{1}{\sqrt{3}} \approx 57.7\%$$

Open delta

Disadvantages:


- De-rated operation, 57.7% of $\Delta\Delta$ bank; $\times (3/2) = 86.6\%$ of the capacity of the remaining two transformers

-Average P.F. of V bank < Load P.F. (~ 86.6% of balanced load P.F.);


The two transformers operate at different power factors; for a balanced load P.F. of $\cos\phi$, one transformer has a P.F. of $\cos(30-\phi)$ while the other has a P.F. of $\cos(30+\phi)$, accordingly voltage regulation differs.

- Accordingly, increasing load (even if perfectly balanced), causes terminal secondary voltages to be unbalanced

Fed from Three phase source

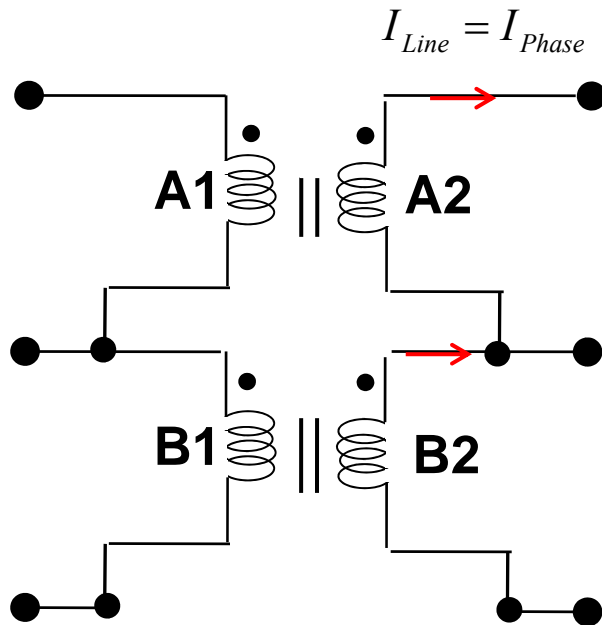

Supplying Three phase load

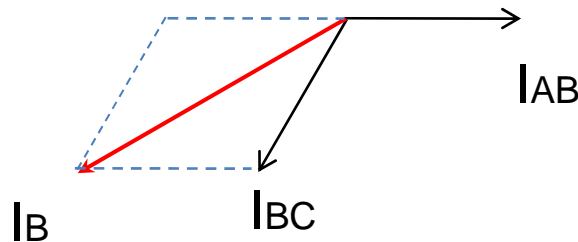

Two single phase 150 kVA, 7200/600 V transformers are connected in open delta configuration. Find the maximum three phase load supplied.

Rated Secondary current of either transformer = $150\,000 / 600 = 250\text{ A}$
This current should not be exceeded whatever was the type of connection,
Accordingly:

$$(S_{Load})_{\text{maximum}} = \sqrt{3}VI = \sqrt{3} \times 600 \times 250 = 260\text{kVA}$$


$$\text{Available rating of two transformers} = 2 \times 150 = 300\text{kVA}$$

$$\% \text{ Derating} = 260/300 = 86.6\%$$

One transformer is producing reactive power, while the other is consuming reactive power. This energy exchange between the two transformers is the reason for limited power output of 57.7% instead of an expected 66.7%

Open Y – Open Delta


Fed from Three phase source

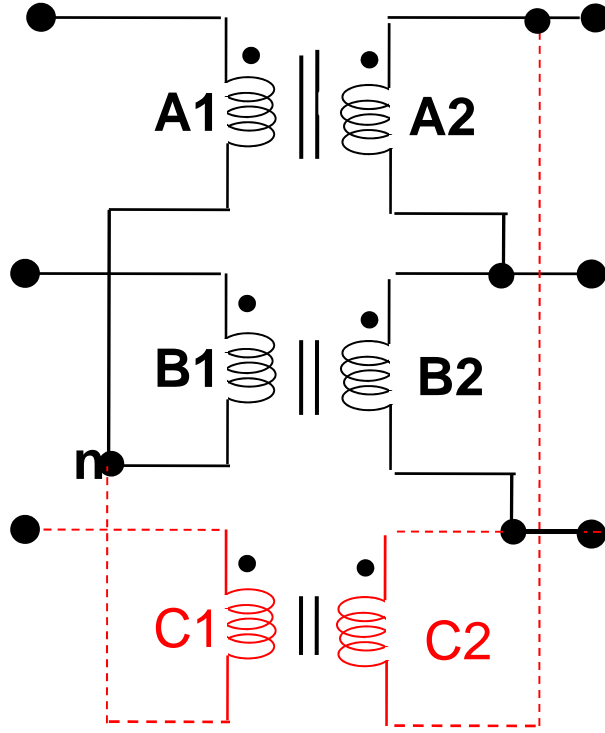

Supplying Three phase load

Open Y – Open Delta

Fed from Three phase source

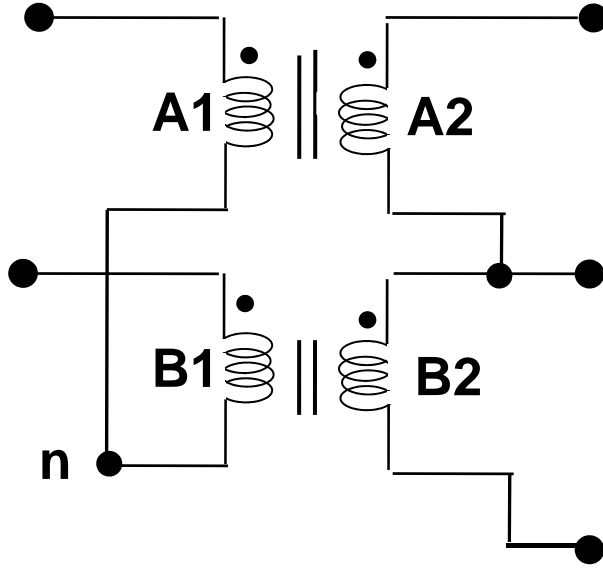

Supplying Three phase load

Disadvantages:

- Very large return current flow in neutral of primary