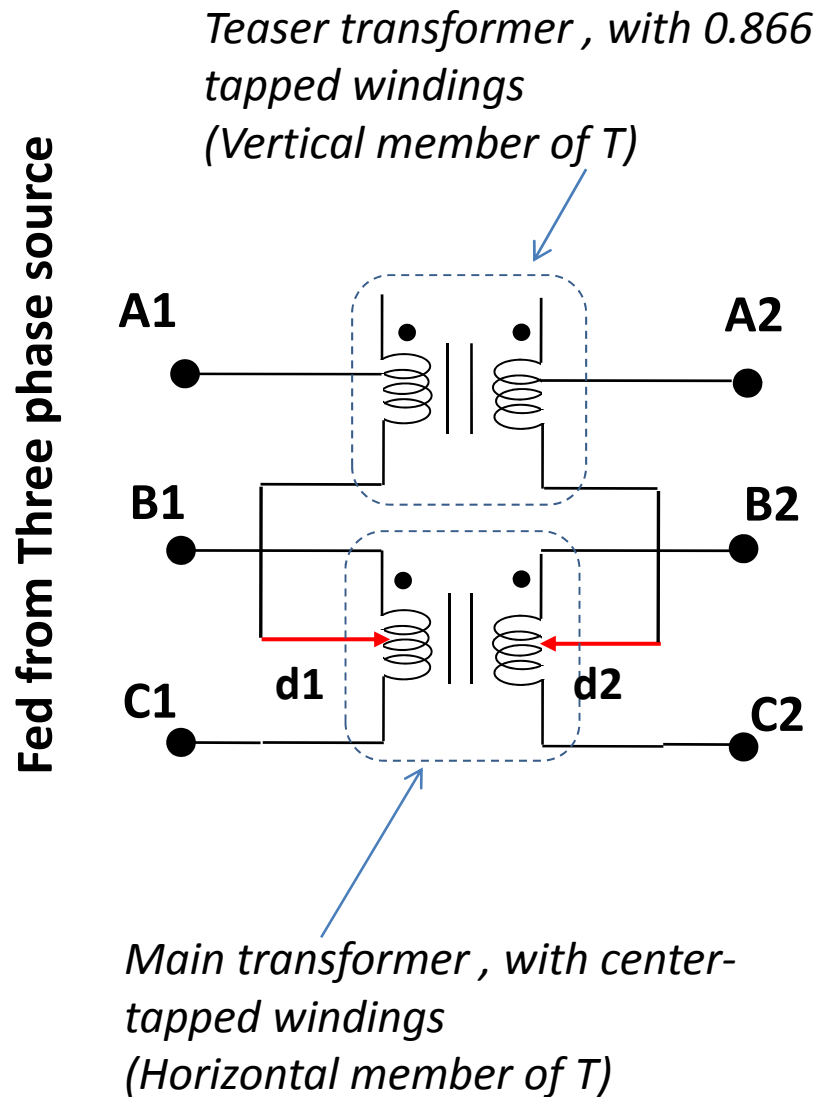





Scott Connection (T-T)



Supplying Three phase load

Advantages:

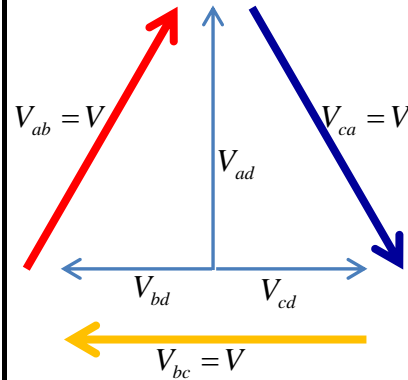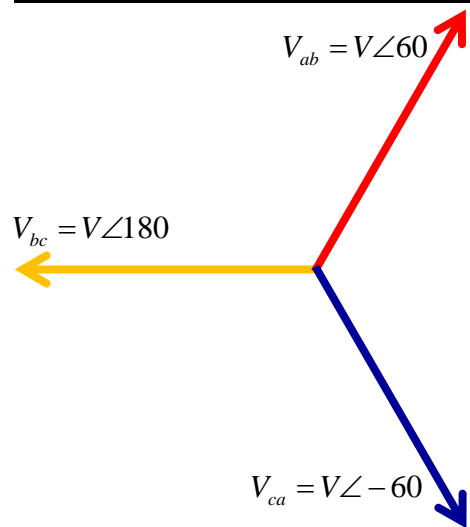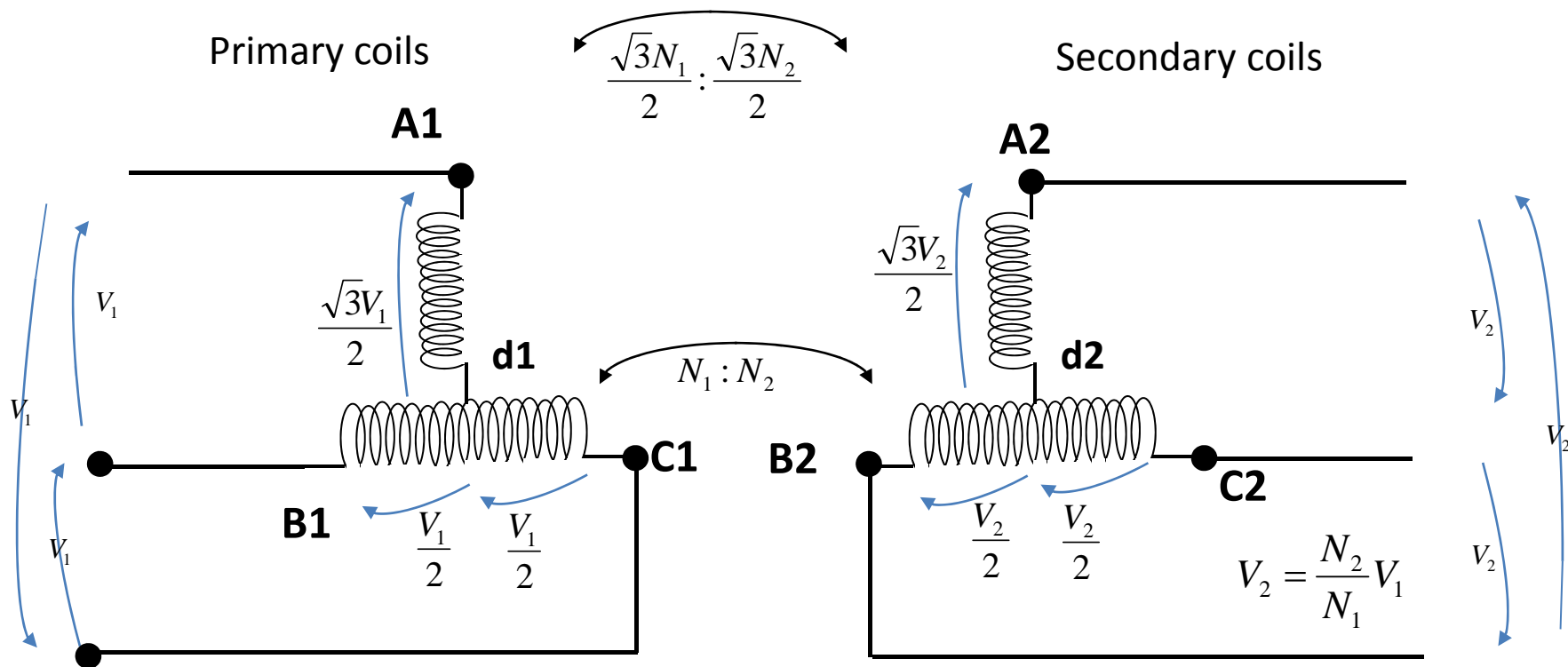- Compared to open delta and open Y -open delta, a neutral can be connected to both of the primary and secondary sides





KVL in loop $d_1 b_1 a_1 d_1$:


$$\begin{aligned} V_{a_1 d_1} &= V_{b_1 d_1} + V_{a_1 b_1} \\ &= V_1 \angle 60 + \left(\frac{V_1}{2}\right) \angle 180 \\ &= \left[\left(0.5 + j\frac{\sqrt{3}}{2}\right) + (-0.5 + j0)\right] V_1 \\ &= j\frac{\sqrt{3}}{2} V_1 = \frac{\sqrt{3}}{2} V_1 \angle 90 \end{aligned}$$

KVL in loop $d_2 a_2 c_2 d_2$:
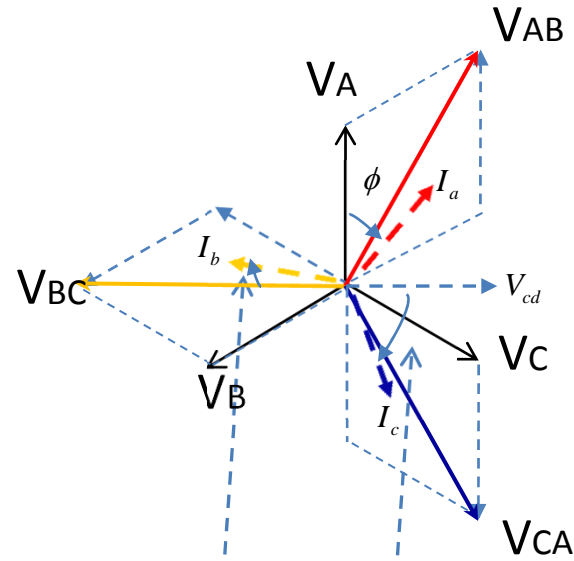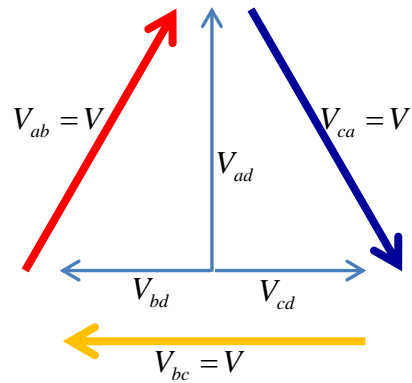
$$\begin{aligned} V_{c_2 a_2} &= -V_{a_2 d_2} + V_{c_2 d_2} \\ &= -\frac{\sqrt{3}}{2} V_2 \angle 90 + \left(\frac{V_2}{2}\right) \angle 0 \\ &= \left[-j\frac{\sqrt{3}}{2} + (+0.5 + j0)\right] V_2 \\ &= \left[0.5 - j\frac{\sqrt{3}}{2}\right] V_2 = V_2 \angle -60 \end{aligned}$$



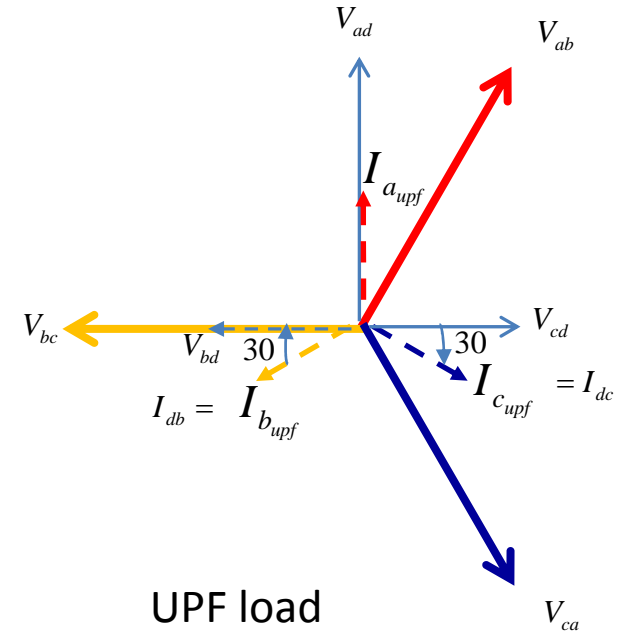
For a balanced load P.F. of $\cos \phi$, the teaser current lags or leads the voltage by ϕ , while one half of the main transformer has a P.F. of $\cos(30-\phi)$, and the other half has a P.F. of $\cos(30+\phi)$



UPF load

Three phase to two phase conversion:

Via modified Scott connection:

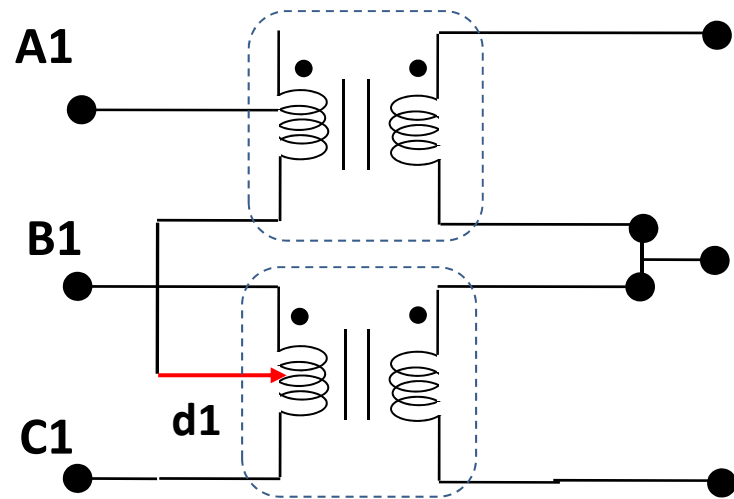

Turns ratio:


$$\text{Main:} \quad N_1 : N_2$$

$$\text{Teaser:} \quad \frac{\sqrt{3}}{2} N_1 : N_2$$


$$\text{i.e:} \quad N_1 : 1.15N_2$$

Taps are applied in primary windings only, while full secondary windings are utilized. The teaser primary tap is adjusted to 86.6% to provide equal in magnitude with phase quadrature two phase secondary voltages .


3φ→2φ conversion (cont.):

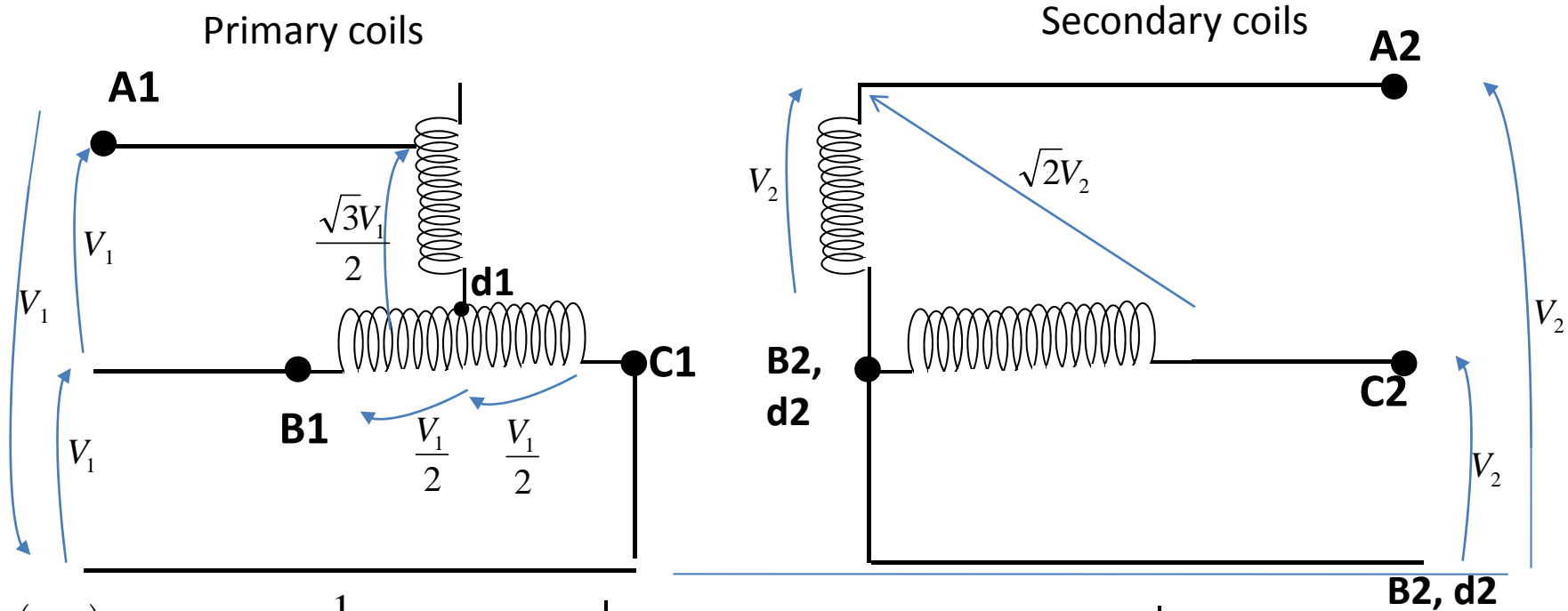

$$\begin{aligned}
 (I_{d_1c_1})_{total} &= I_{M_1} \angle 0 - \frac{1}{2} I_{T_1} \angle 90 \\
 &= \left(\frac{N_2}{N_1}\right) I_2 \angle 0 - \frac{1}{2} \left(\frac{N_2}{\frac{\sqrt{3}}{2} N_1}\right) I_2 \angle 90 \\
 &= I_1 \angle 0 - \frac{1}{\sqrt{3}} I_1 \angle 90 \\
 &= \left| \sqrt{I_1^2 + \left(\frac{1}{\sqrt{3}} I_1\right)^2} \right| \angle 30 = \left| \frac{2}{\sqrt{3}} I_1 \right| \angle 30
 \end{aligned}$$

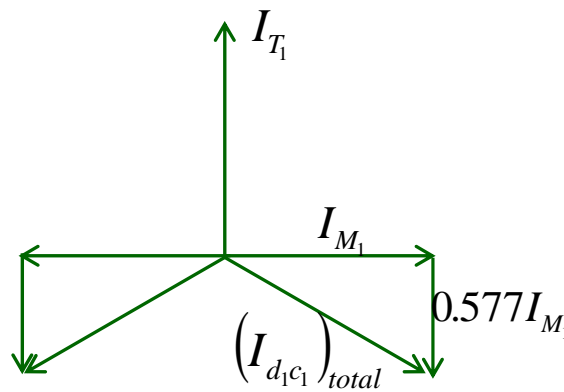

Balanced primary currents

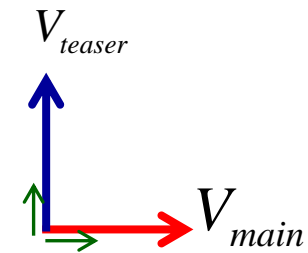

Secondary V, I
(for UPF load)


Two transformers fed from a 440 V 3phase supply in a Scott fashion to operate two single phase 200 V loads with a total demand of 150 kVA. Find the necessary turns ratios and the secondary and primary currents.

$$(N_2 / N_1)_{main} = 200 / 440 = 0.4545$$

$$(I_{main})_{Secondary} = (I_{teaser})_{Secondary} = \frac{150000/2}{200} = 375A$$

$$(I_{main})_{PrimaryBalancingComponent} = (N_2 / N_1)_{main} \times (I_{main})_{Secondary} \\ = 0.4545 \times 375 = 170.45A$$
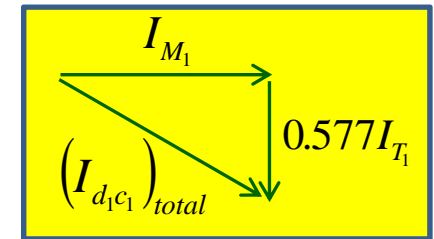
$$(N_2 / N_1)_{Teaser} = \frac{N_{2Main}}{\frac{\sqrt{3}}{2} N_{1Main}} \approx 1.15 \times (N_2 / N_1)_{main} = 0.5227$$



$$(I_{teaser})_{Primary} = (N_2 / N_1)_{Teaser} \times (I_{teaser})_{Secondary} = 0.5227 \times 375 = 196A$$

$$\text{Ineffective teaser current component in primary main} = \frac{1}{2} (I_{teaser})_{Primary} = 98A$$

$$\text{Total current in each half of primary main} = \sqrt{(98)^2 + (170.45)^2} = 196A$$

A two phase, 7.5 kW , 240 V, 60 Hz , 0.8 power factor motor has a 83% efficiency. The motor is fed from 600V three phase distributor through a Scott connected transformer bank. Find the following:

- The current in each 2- phase line
- The current in each 3- phase line