

## Course Contents

- Basic dc circuit elements, series and parallel Networks
- Ohm's law and Kirchoff's laws
- Nodal Analysis
- Mesh Analysis
- Source Transformation Method
- Superposition Theory
- Thevenin's Theorem and Norton Theorem
- Maximum Power Transfer
- Alternating current Fundamentals and AC generation
- RMS value, average value, form factor and crisp factor
- Phasor concept
- Relation between voltage and current in resistor, capacitor and inductor
- Response of RL and RC circuits
- Sinusoidal response of RLC circuit
- Series Resonance

Memristive systems

## Introduction

- Electrical systems pervade our lives; they are found in home, school, workplaces, factories, and transportation vehicles-everywhere.
- A circuit model is used to connect our visualization to our analysis of a physical system.
- The challenge is to develop models that will predict the physical behaviour of real components accurately and result in mathematical equations that can be solved.

Inductor  
 $v_L = L di$

Memristor  
 $v_M = M di$

Memristive systems

## Basic Electrical Quantities

Basic quantities: current, voltage and power.

### Electric current:

Electric current in a wire is defined as the net amount of charge that passes through the wire per unit time, and is measured in amperes (A).

$$i = \frac{dq}{dt}$$

where

$i$  = current in amperes


$q$  = charge in coulombs

$t$  = time in sec.


- 1 Ampere = 1 Coulomb per second (C/s)
- Current in circuits physically realized by movement of electrons.
- Direction of current must be specified by an arrow.

Memristive systems

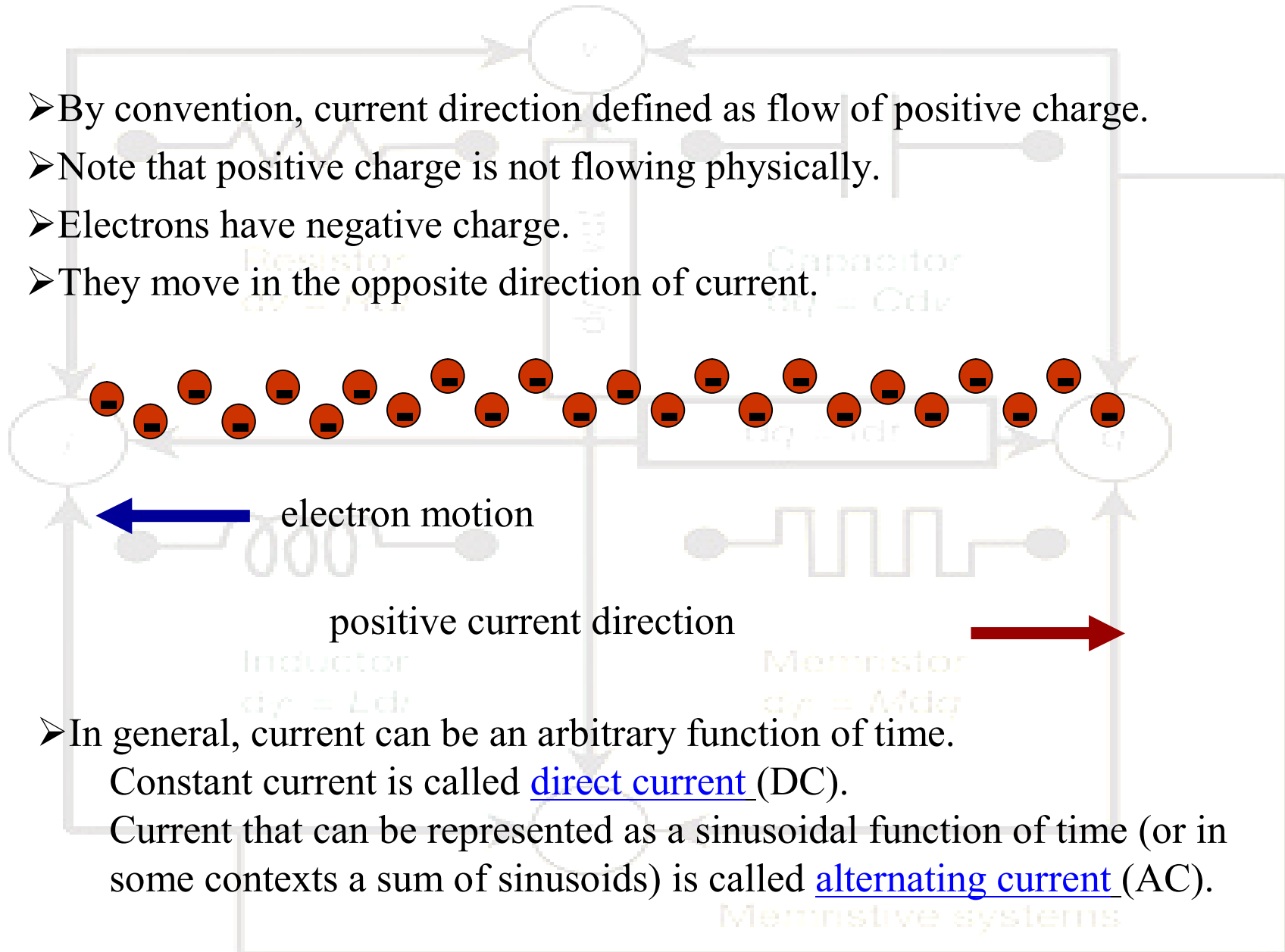- By convention, current direction defined as flow of positive charge.
- Note that positive charge is not flowing physically.
- Electrons have negative charge.
- They move in the opposite direction of current.



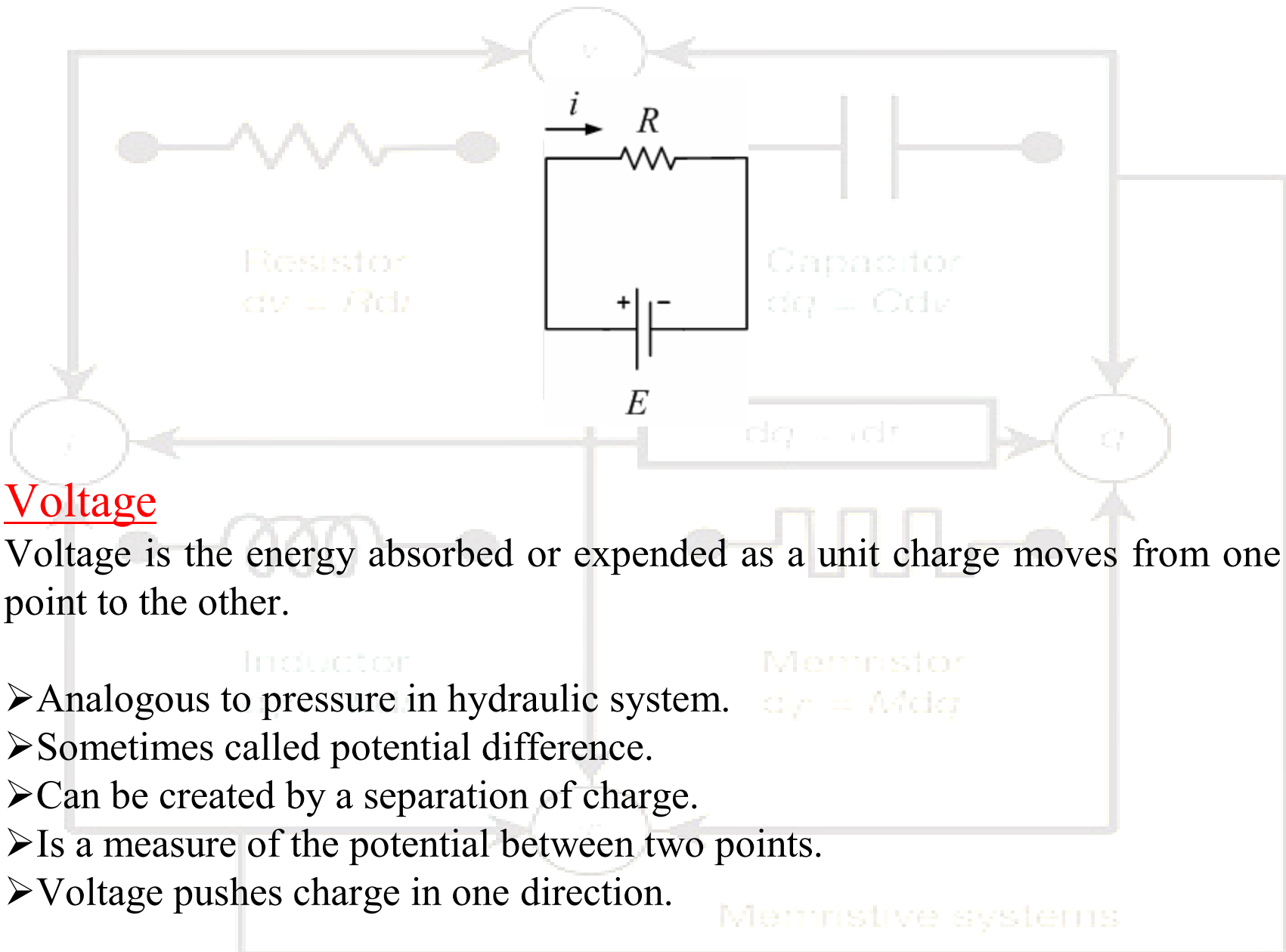- In general, current can be an arbitrary function of time.  
Constant current is called direct current (DC).  
Current that can be represented as a sinusoidal function of time (or in some contexts a sum of sinusoids) is called alternating current (AC).



## Voltage

Voltage is the energy absorbed or expended as a unit charge moves from one point to the other.

- Analogous to pressure in hydraulic system.
- Sometimes called potential difference.
- Can be created by a separation of charge.
- Is a measure of the potential between two points.
- Voltage pushes charge in one direction.

- We use polarity (+ and – on batteries) to indicate which direction the charge is being pushed
- Voltage is the energy required to move a unit charge through an element, measured in volts (V)


$$v = \frac{d\omega}{dq}$$


where

$v$  = voltage in volts

$\omega$  = energy in Joules

$q$  = charge in coulombs

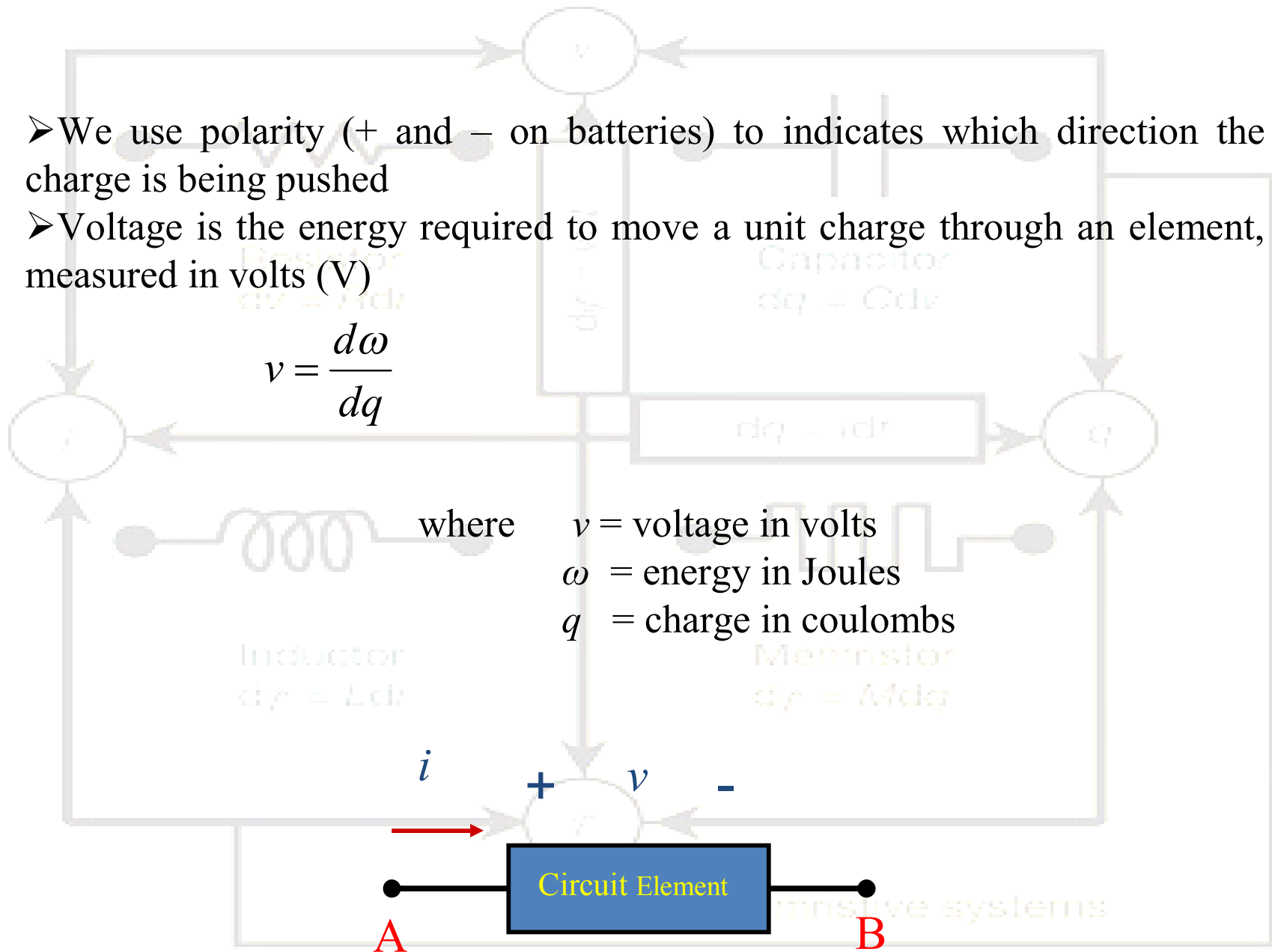

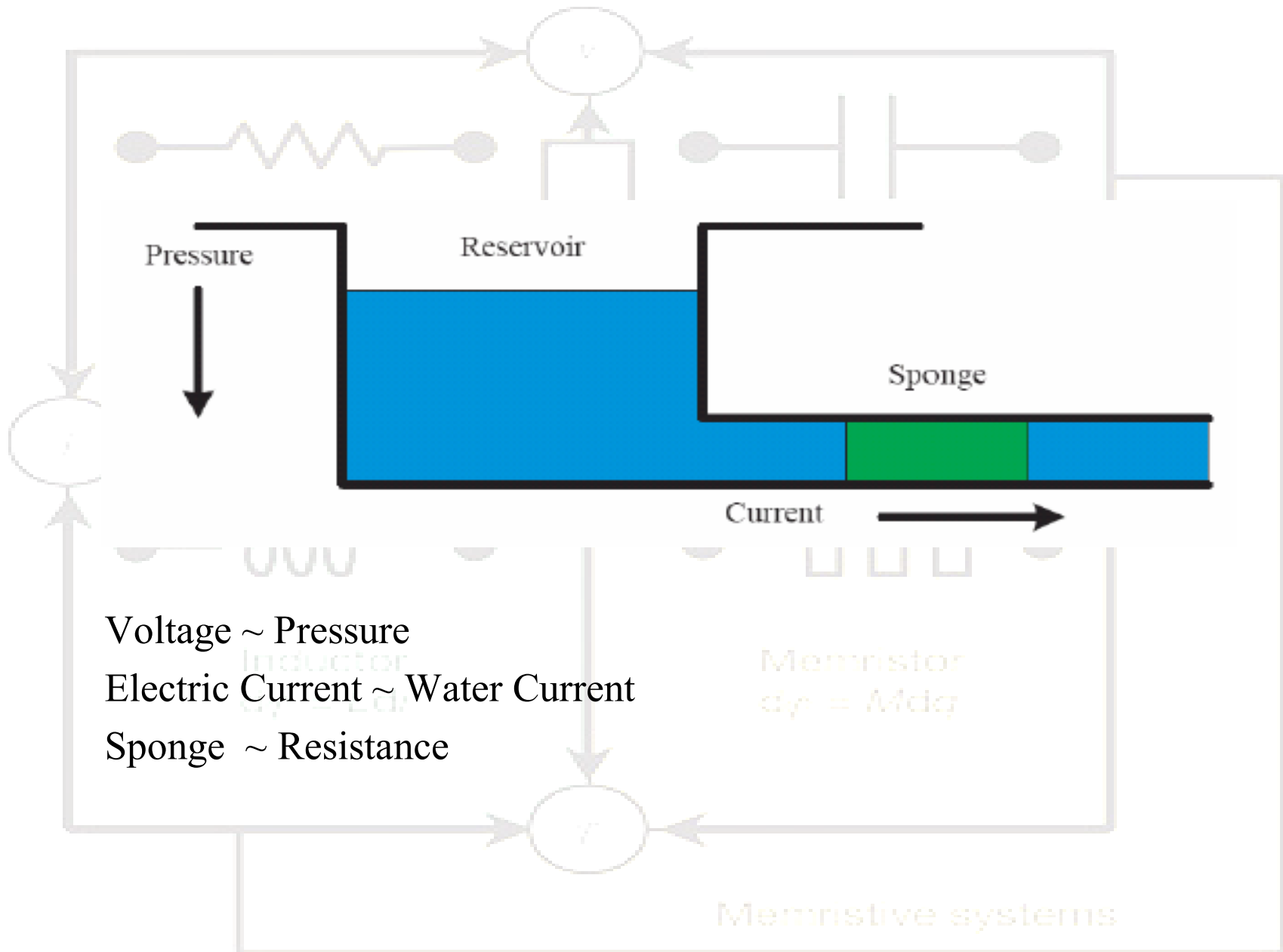



## Electrical Power

Time rate of expending or absorbing energy and is measured by Watts.

$$p = \frac{d\omega}{dt}$$

$$p = \left( \frac{d\omega}{dq} \right) \left( \frac{dq}{dt} \right) = vi$$

where

$p$  = power in watts

$\omega$  = energy in Joules

$t$  = time in seconds

$q$  = charge in coulombs

$i$  = current in amperes

$v$  = voltage in volts

By convention


- Circuit elements that **absorb** power have a **positive** value of  $p$ .
- Circuit elements that **produce** power have a **negative** value of  $p$ .

## Elements of electrical circuits
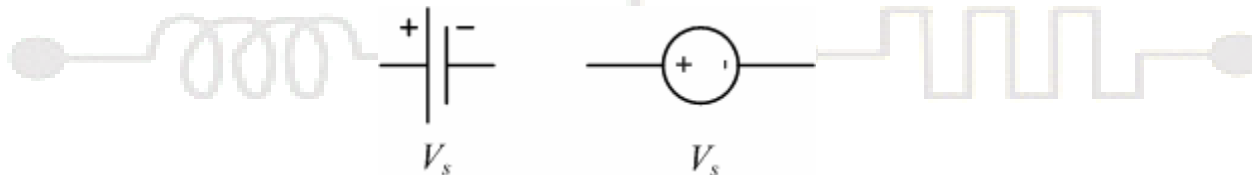
### Active elements

Active elements are the elements that can generate energy or power, such as voltage and current sources.

➤ Ideally, a voltage source produces  $V_s$  volts regardless of the current absorbed or produced by the connected device.




➤ Ideally, a current source produces  $I_s$  amps regardless of the current in the connected device.


➤ In a particular circuit, there can be active elements that absorb power – for example, a battery being charged.

## Passive elements

passive elements are the elements that can not generate energy, such as resistors, capacitors and inductors.
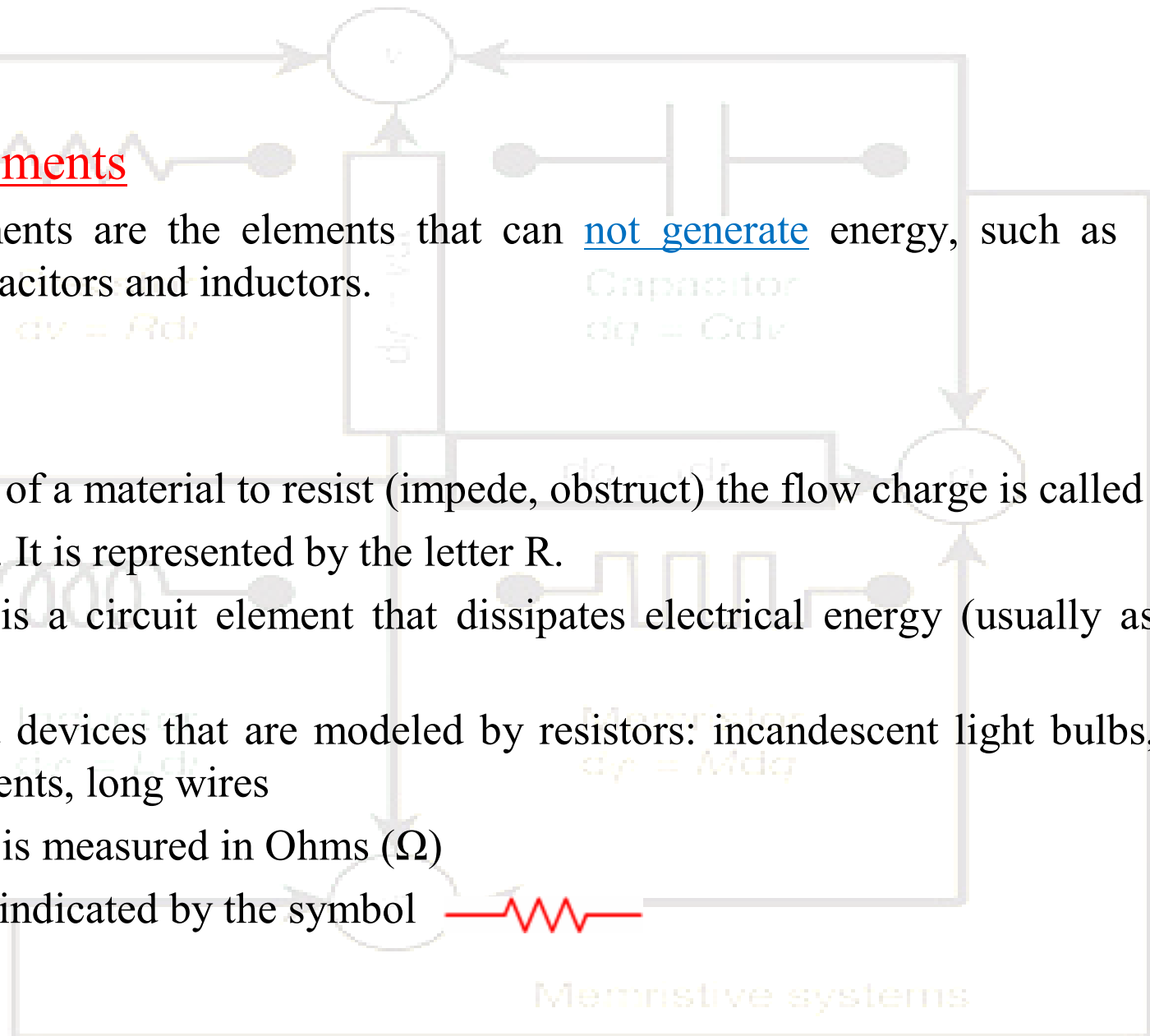
### resistors

- The ability of a material to resist (impede, obstruct) the flow charge is called its resistivity. It is represented by the letter R.
- A resistor is a circuit element that dissipates electrical energy (usually as heat)
- Real-world devices that are modeled by resistors: incandescent light bulbs, heating elements, long wires
- Resistance is measured in Ohms ( $\Omega$ )
- Resistor is indicated by the symbol 



➤ Resistance of a wire depends on some factors like as length ( $L$ ), cross-sectional area ( $A$ ) and resistivity of material ( $\rho$ ).

Resistor  
dq = Rdr

$$R = \frac{\rho L}{A}$$

Capacitor  
dq = Cdv

Where

$\rho$  resistivity in  $\Omega \cdot m$

$L$  length in m

$A$  cross-section area in  $m^2$

➤ The conductance ( $G$ ) of a pure resistor is the reciprocal of its resistance. The unit of conductance is the siemens (S) or mho ( $\text{U}$ ).

Inductor  
dq = Ldi

Memristor  
dq = Mdi

$$G = \frac{1}{R}$$

Memristive systems

## Ohm's Law

**Ohm's law** states that the current through a conductor between two points is directly proportional to the potential difference or voltage across the two points, and inversely proportional to the resistance between them.


➤ The mathematical equation that describes this relationship is:

$$i = \frac{v}{R}$$

where  $v$  is the potential difference measured across the resistance in units of volts;  $i$  is the current through the resistance in units of amperes and  $R$  is the resistance of the conductor in units of ohms.


Memristive systems

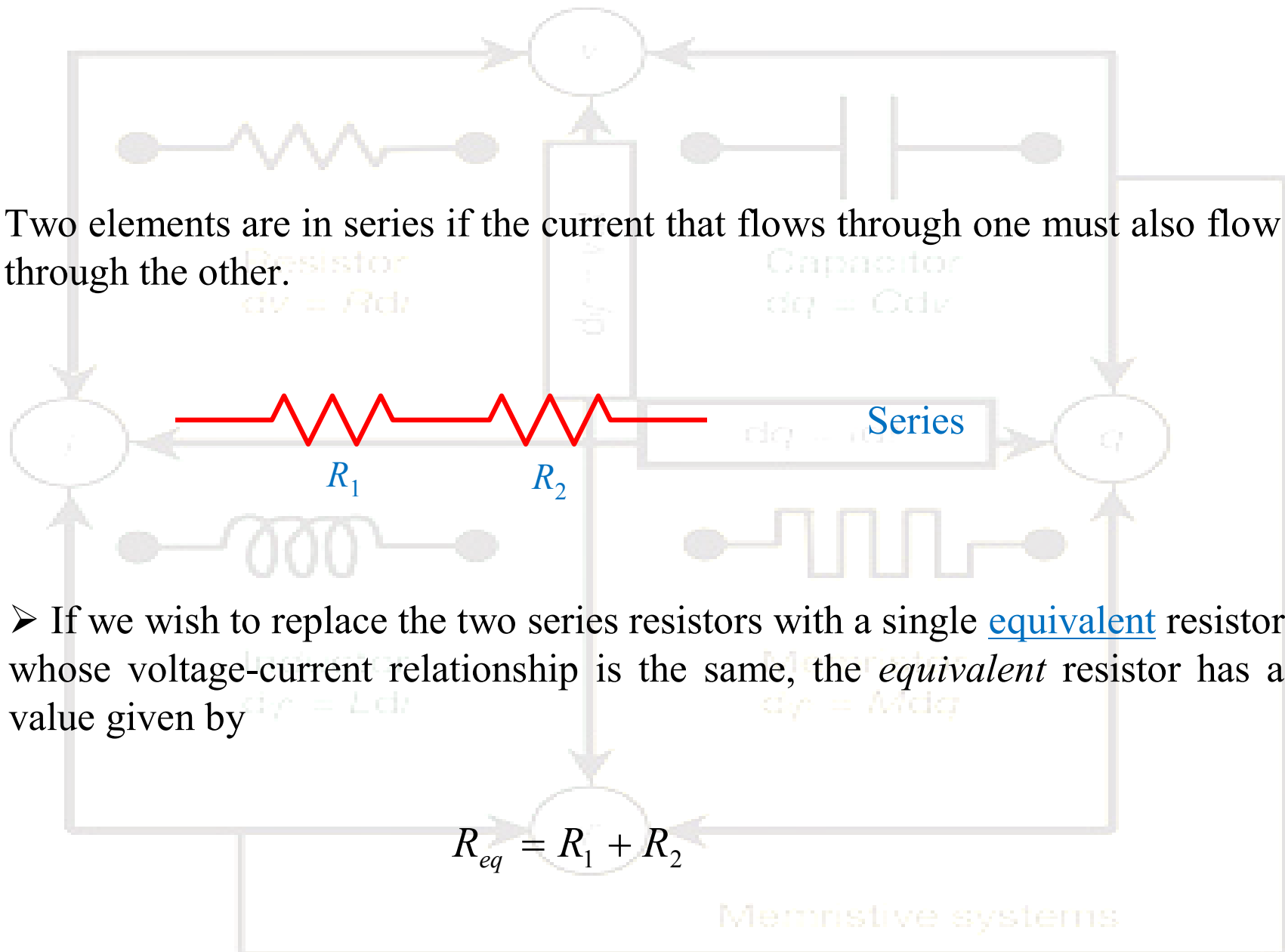Two elements are in series if the current that flows through one must also flow through the other.




➤ If we wish to replace the two series resistors with a single equivalent resistor whose voltage-current relationship is the same, the *equivalent* resistor has a value given by

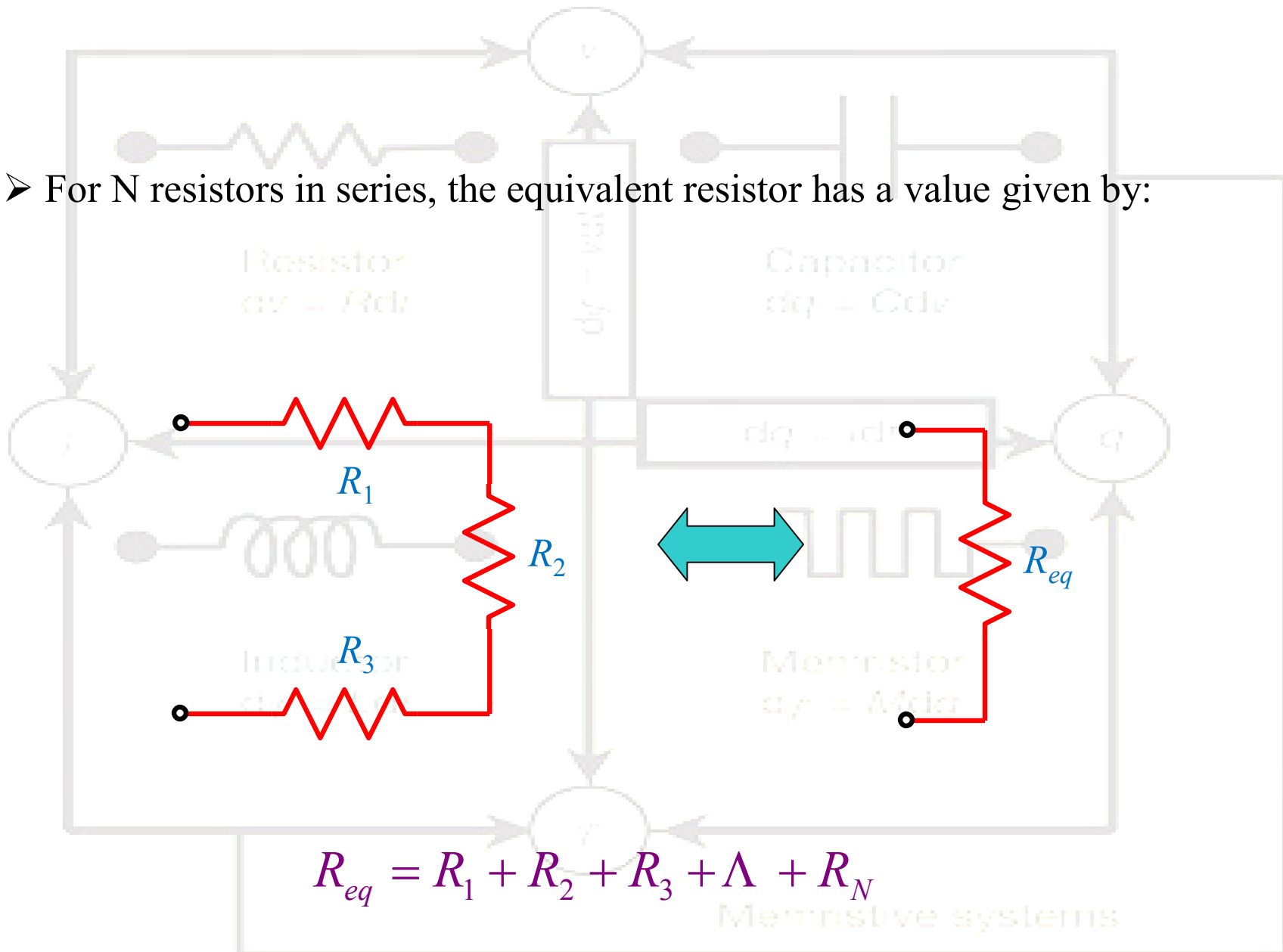➤ For N resistors in series, the equivalent resistor has a value given by:



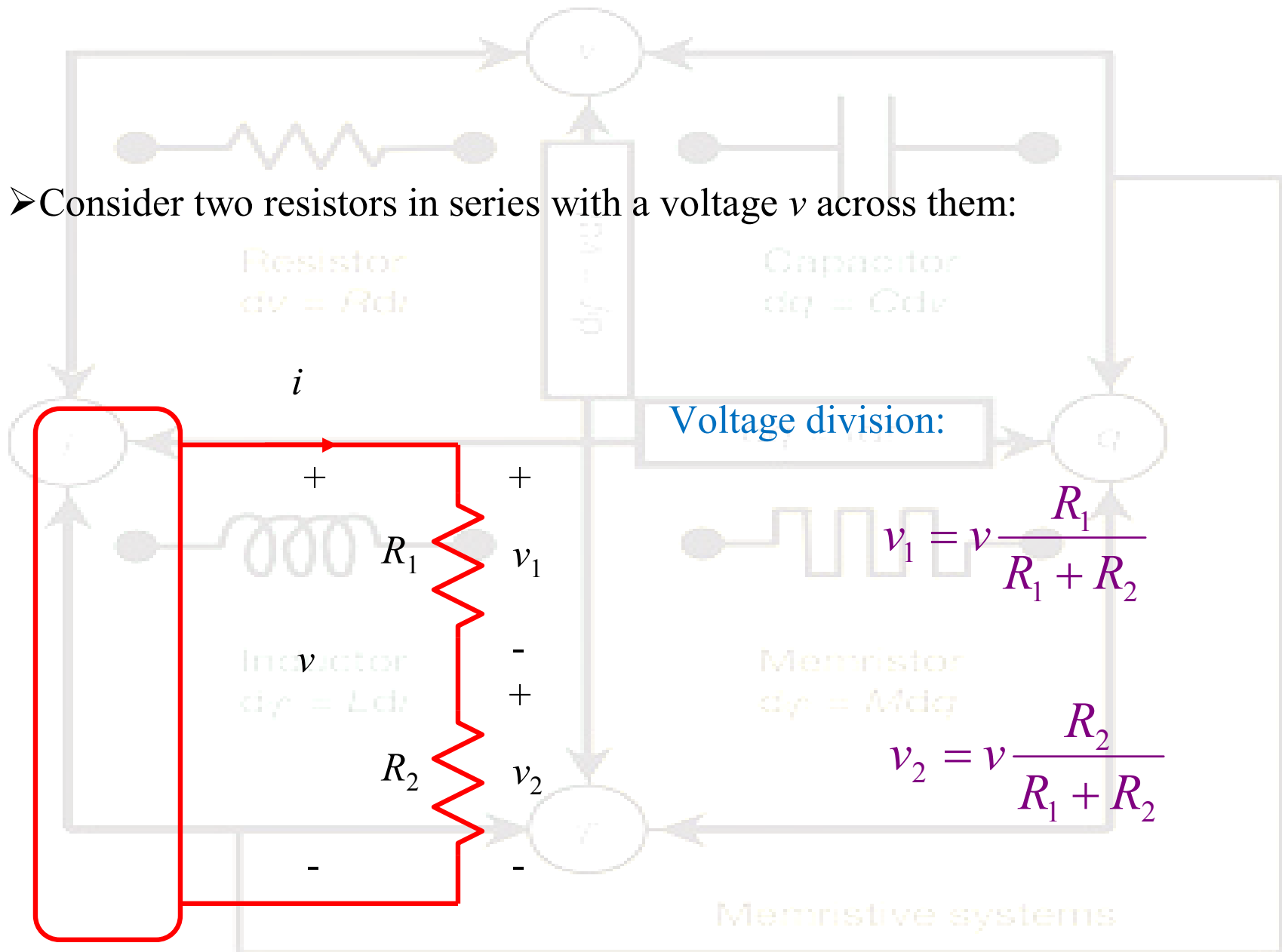
➤ Consider two resistors in series with a voltage  $v$  across them:




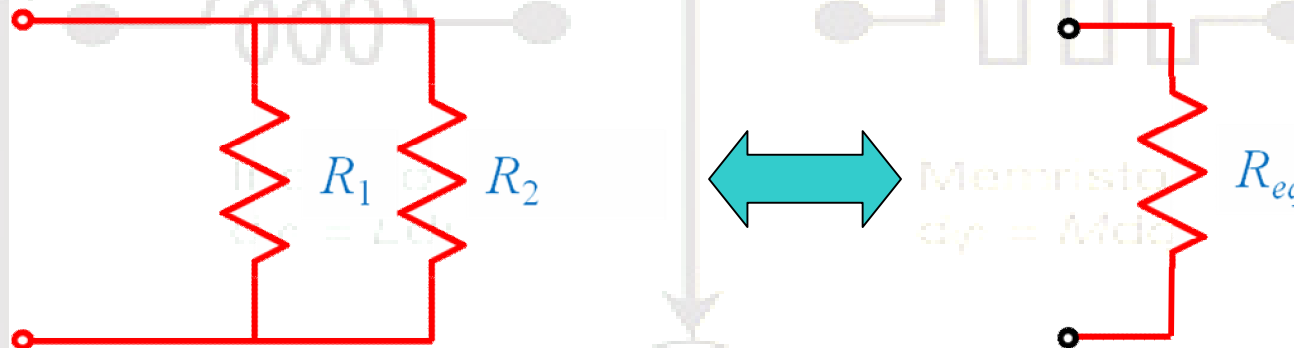
## Resistors in Parallel

- When the terminals of two or more circuit elements are connected to the same two nodes, the circuit elements are said to be in parallel.
- If we wish to replace the two parallel resistors with a single equivalent resistor whose voltage-current relationship is the same, the *equivalent* resistor has a value given by



$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

➤ Consider two resistors in parallel with a voltage  $v$  across them:

