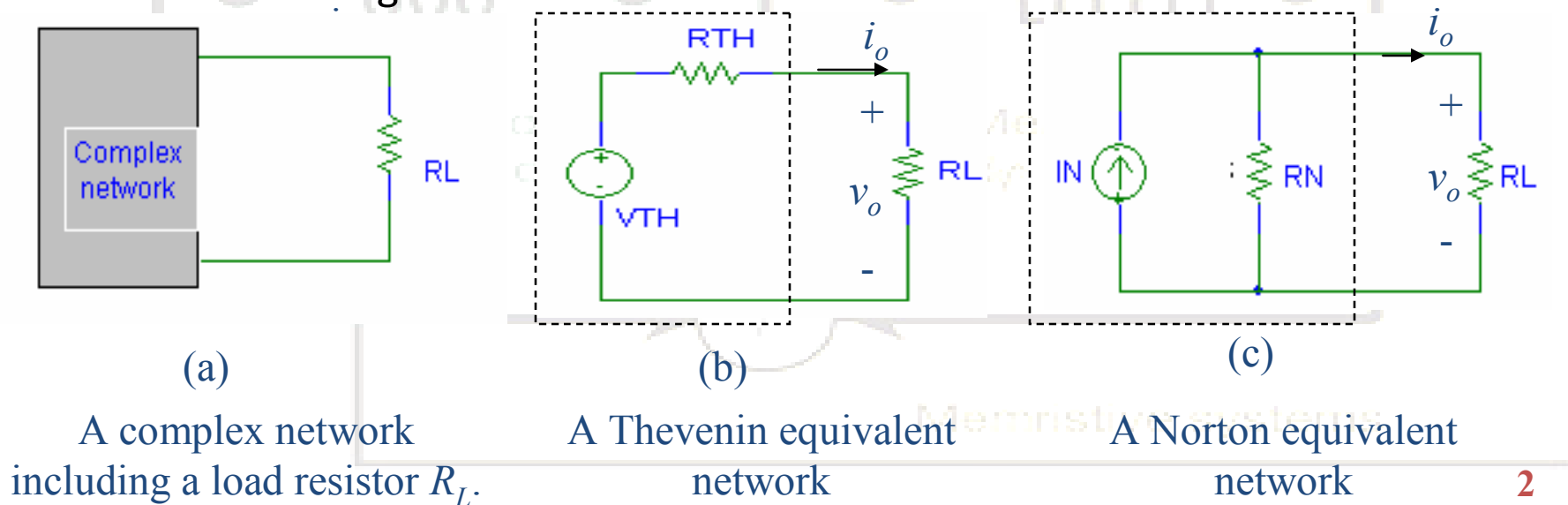


Thevenin and Norton theorems

- Thevenin theorem tells us that we can replace the entire network, exclusive of the load resistor, by an equivalent circuit that contains only an independent voltage source in series with a resistor in such a way that the current-voltage ($i-v$) relationship at the load resistor is unchanged.
- Norton theorem tells us that we can replace the entire network, exclusive of the load resistor, by an equivalent circuit that contains only an independent current source in parallel with a resistor in such a way that the current-voltage ($i-v$) relationship at the load resistor is unchanged.



Thevenin Theorem

- How to determine $v_{TH}(t)$ and R_{TH} for a particular circuit.
- It is helpful to note that if we connect no load and therefore $i_o(t) = 0$, then we can determine $v_{TH}(t)$ from

$$v_{TH}(t) = v_{opencircuit}(t) \equiv v_{oc}(t)$$


where $v_{oc}(t)$ is called the open circuit voltage

- If we short circuit the two terminals to force $v_o(t) = 0$, then we get


$$\frac{v_{TH}(t)}{R_{TH}} = i_{shortcircuit}(t) \equiv i_{sc}(t)$$

- If $v_{TH}(t) \neq 0$, then $i_{shortcircuit}(t) \neq 0$ and we find

$$R_{TH} = \frac{v_{oc}(t)}{i_{sc}(t)}$$




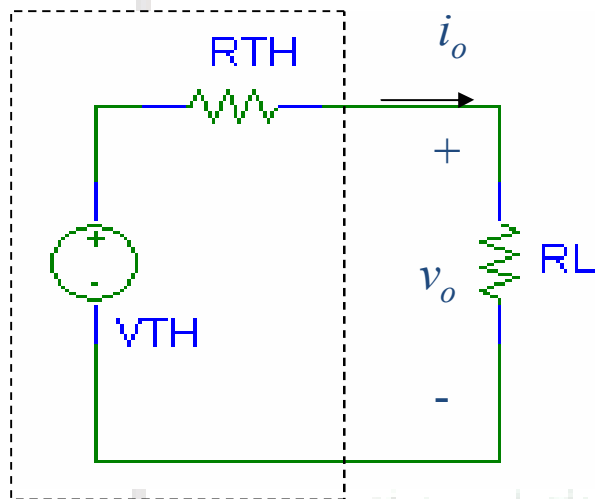


Case 1 example 1

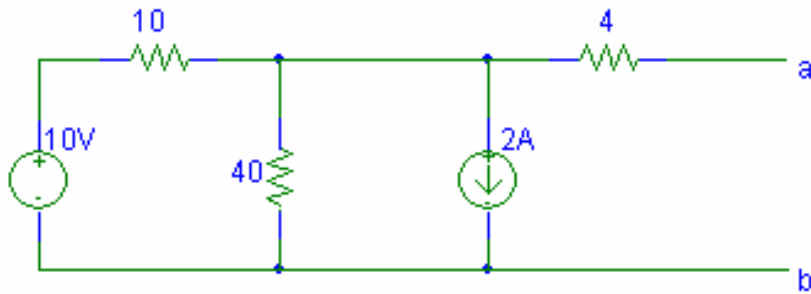

Find the Thevenin equivalent circuit at terminal pair a and b for the circuit shown.

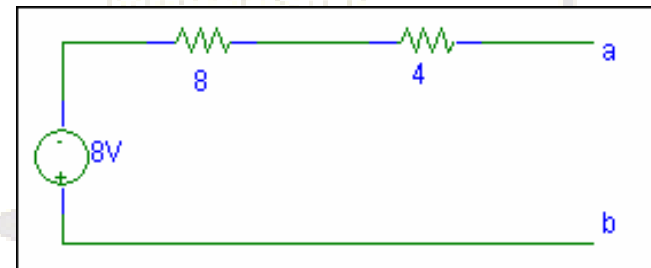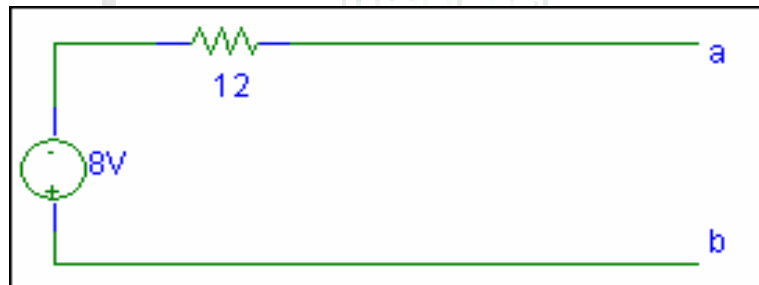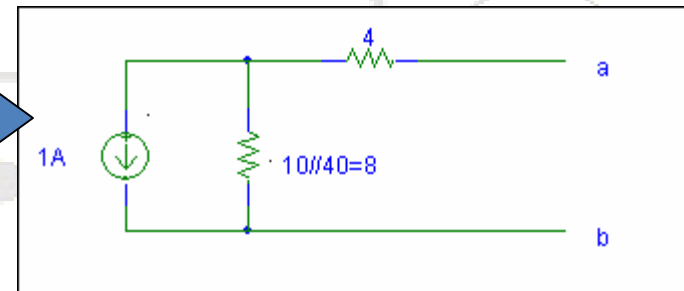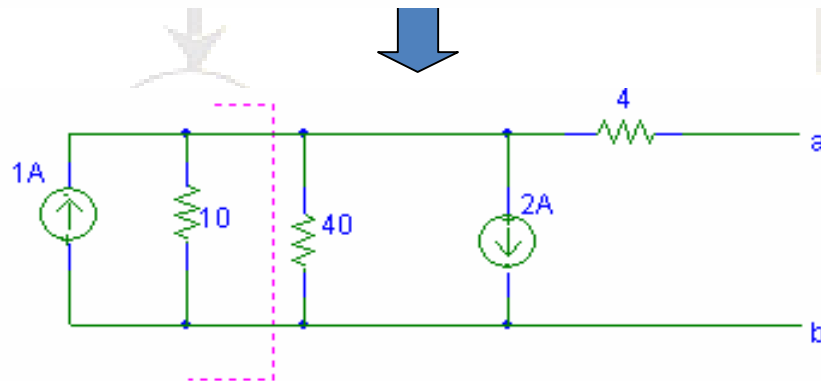
This specific problem can be solved by using different approaches. We solve the problem by using source transformation technique.



Thus we have

$$R_{TH} = 12\Omega \quad \text{and} \quad v_{TH} = -8V$$


Thevenin Theorem

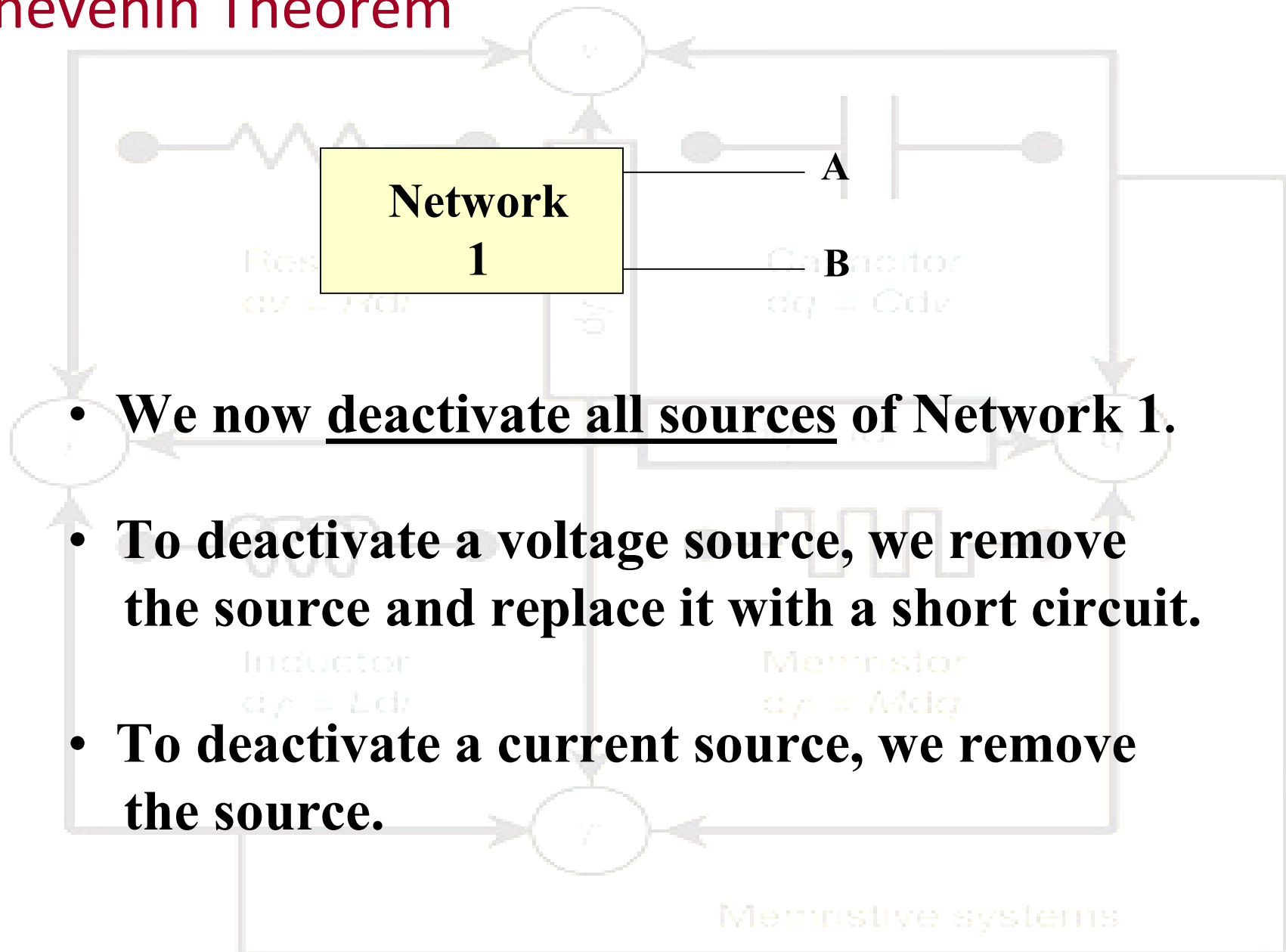

- We now deactivate all sources of Network 1.
- To deactivate a voltage source, we remove the source and replace it with a short circuit.
- To deactivate a current source, we remove the source.


Thevenin Theorem

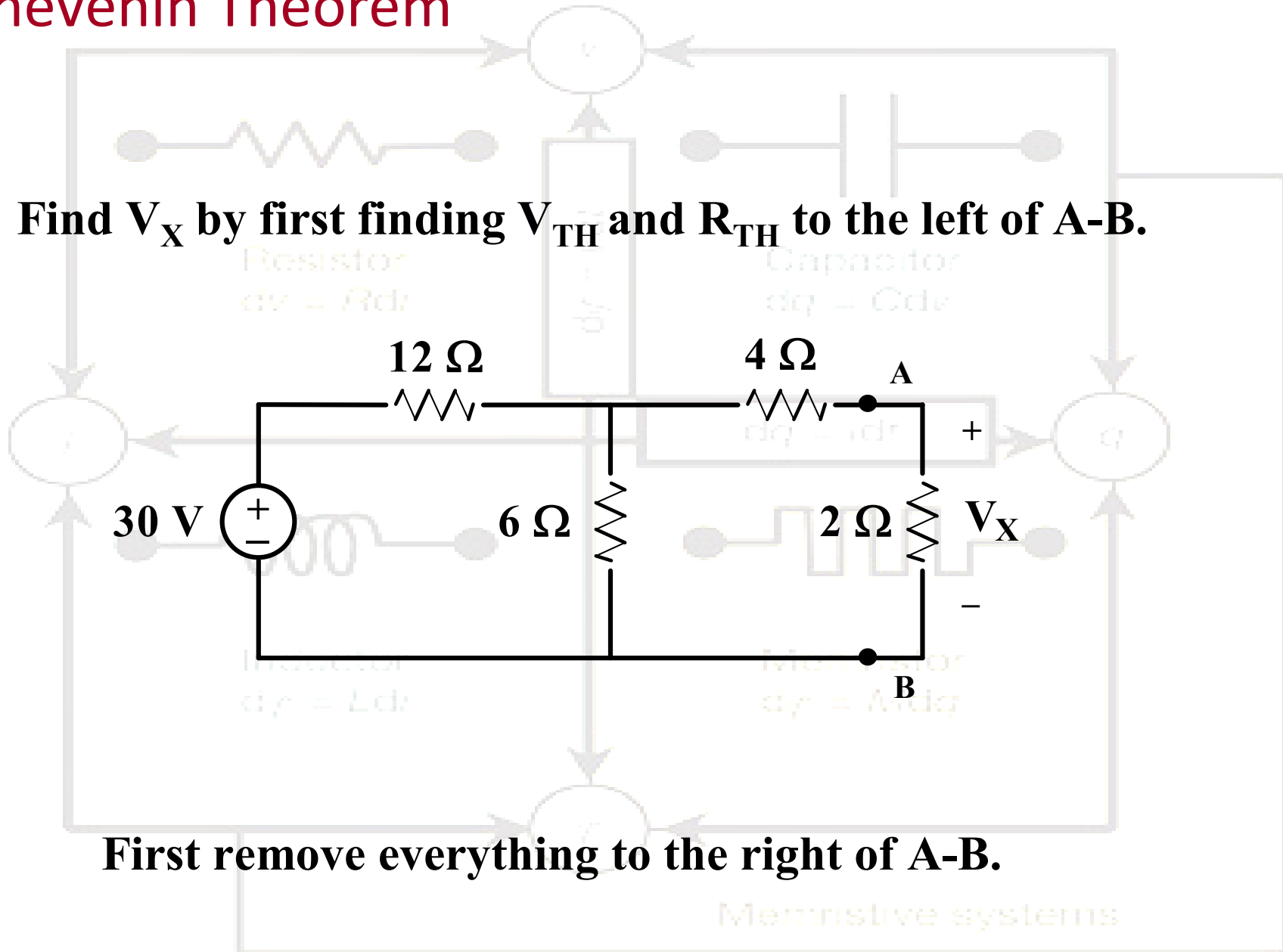Find V_X by first finding V_{TH} and R_{TH} to the left of A-B.



First remove everything to the right of A-B.

Thevenin Theorem

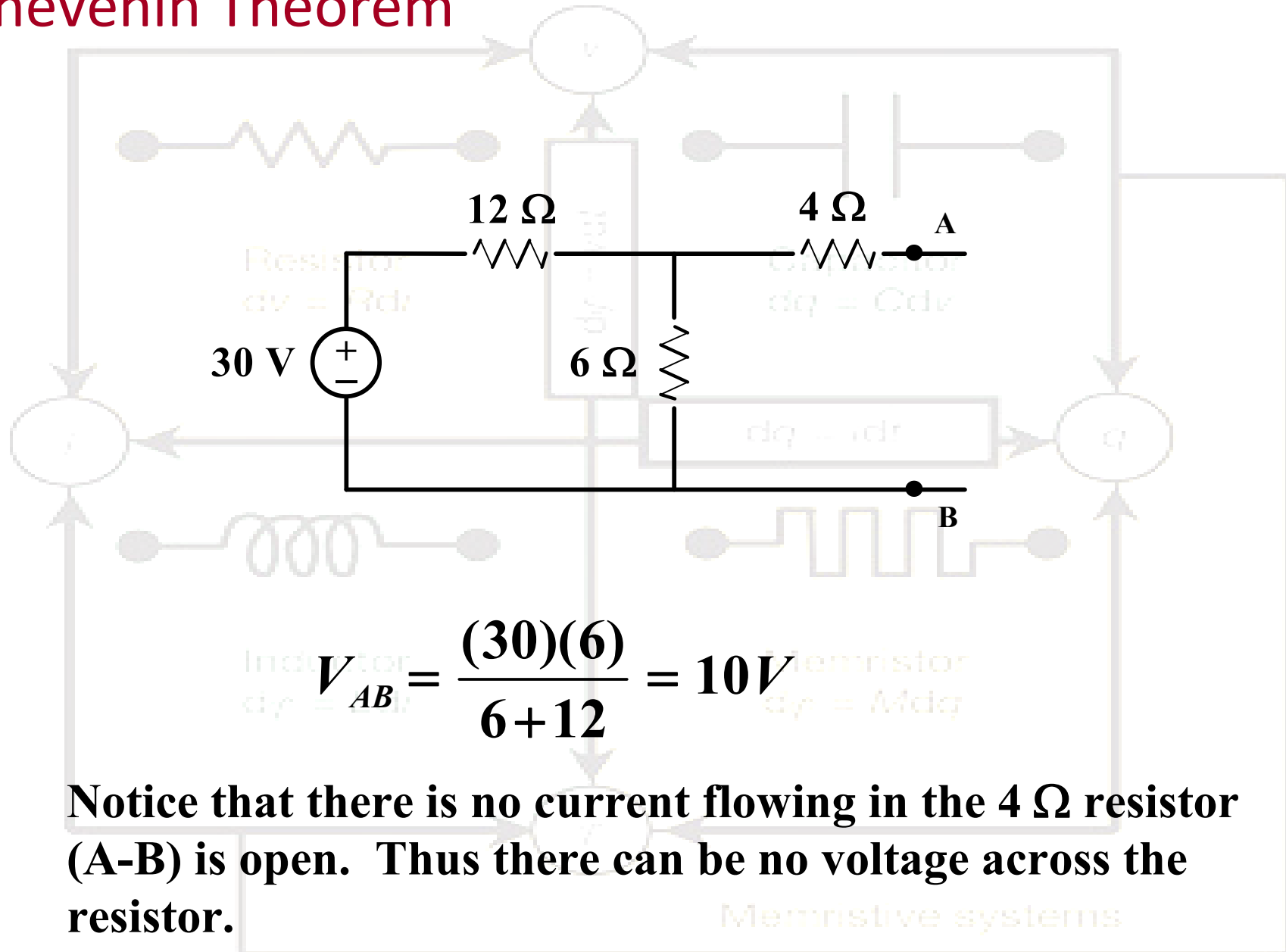


$$V_{AB} = \frac{(30)(6)}{6+12} = 10V$$

Notice that there is no current flowing in the 4 Ω resistor (A-B) is open. Thus there can be no voltage across the resistor.


Thevenin Theorem

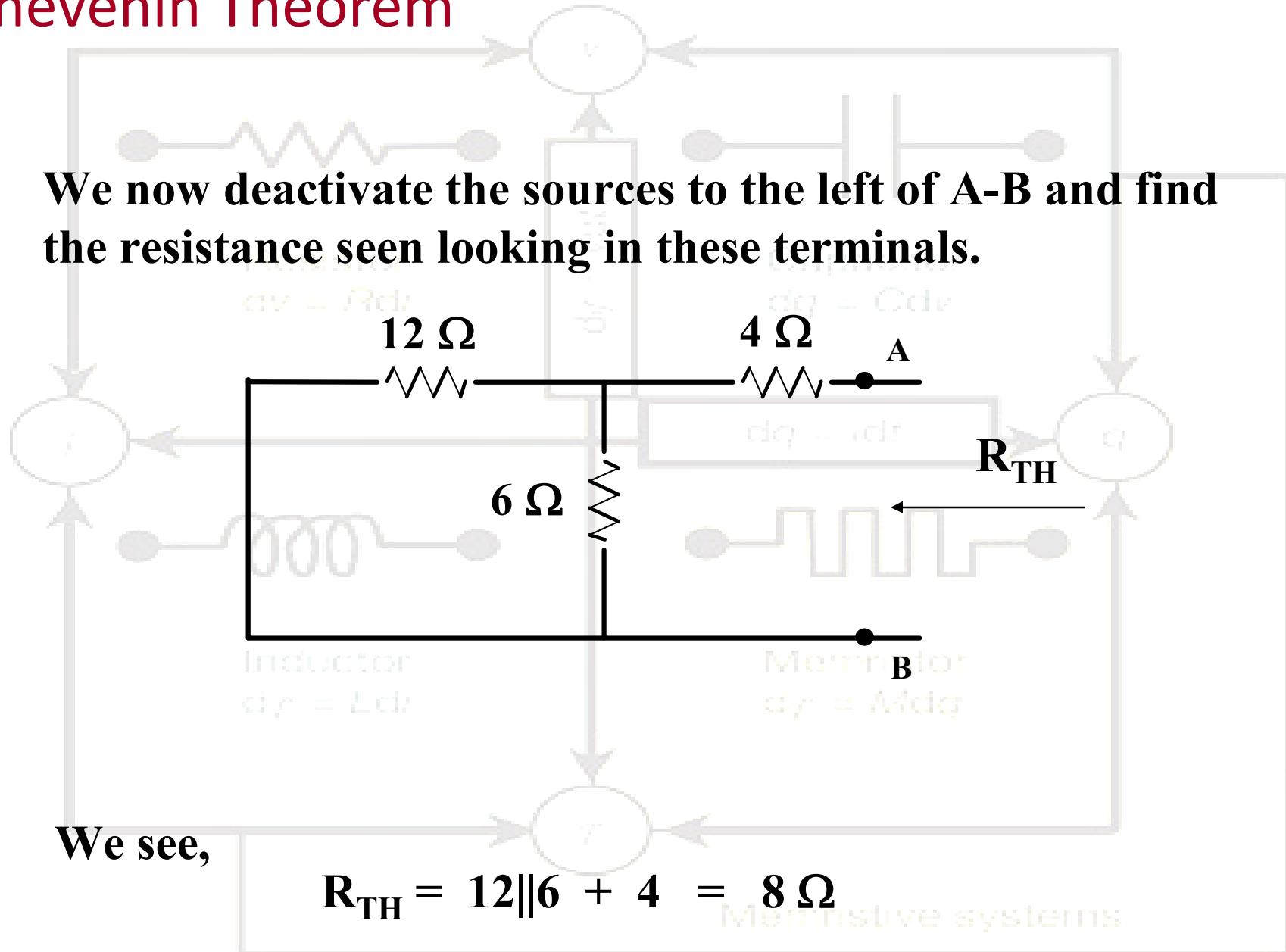We now deactivate the sources to the left of A-B and find the resistance seen looking in these terminals.




Thevenin Theorem

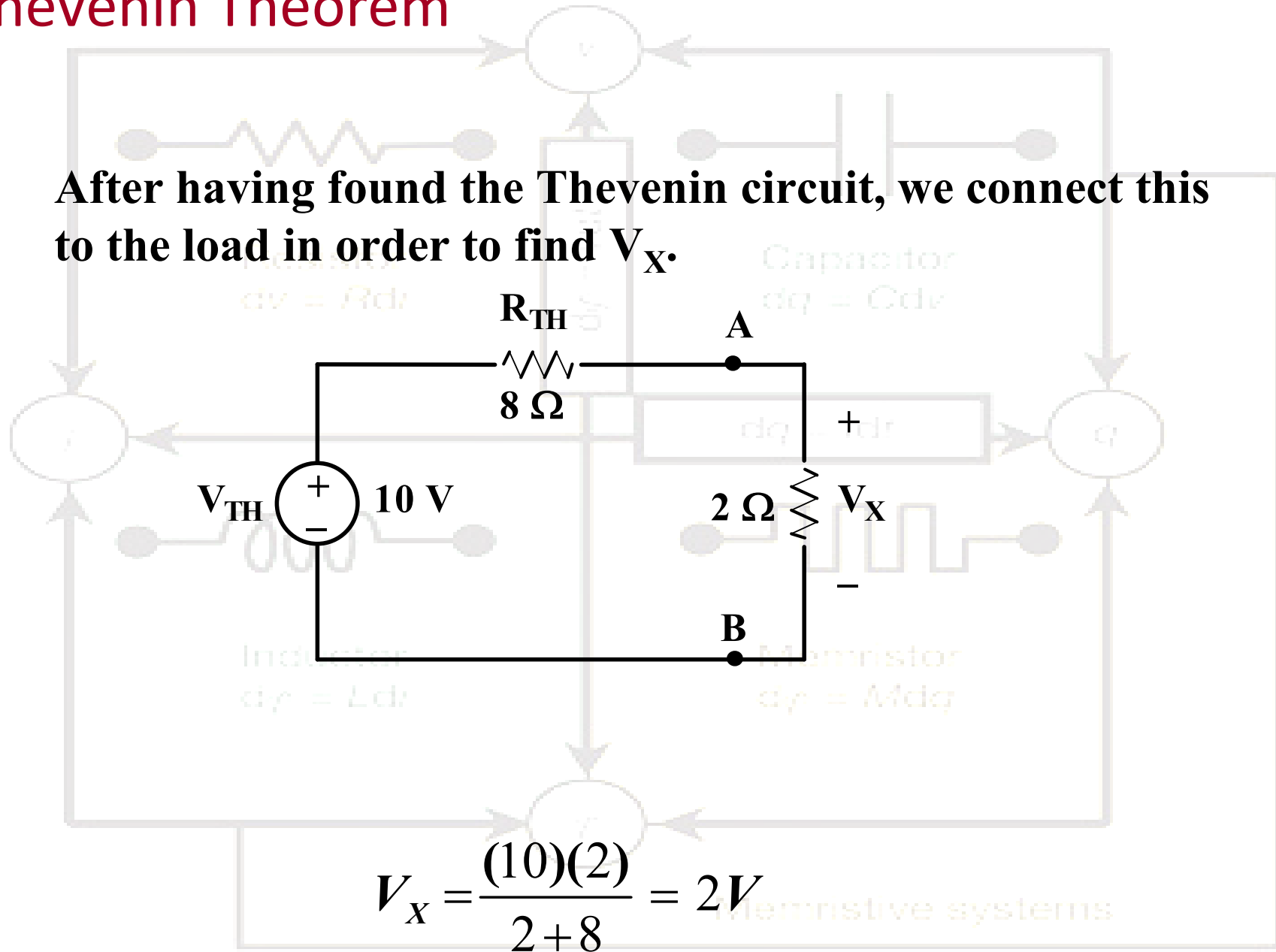After having found the Thevenin circuit, we connect this to the load in order to find V_X .




Thevenin Theorem

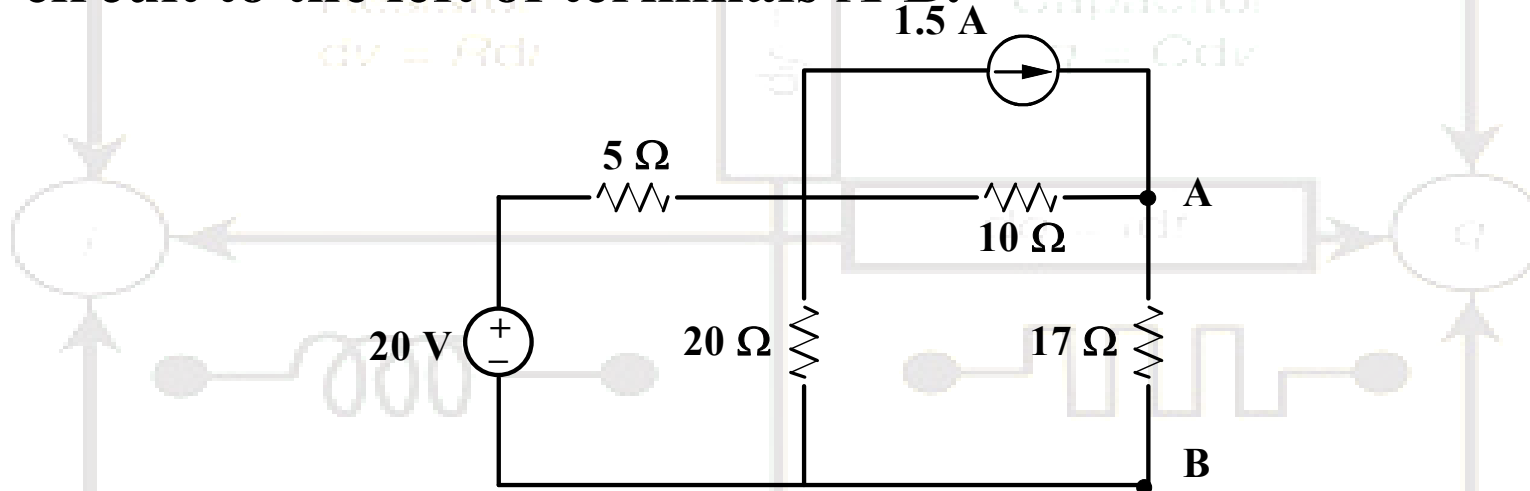For the circuit below, find V_{AB} by first finding the Thevenin circuit to the left of terminals A-B.




We first find V_{TH} with the $17\ \Omega$ resistor removed. Next we find R_{TH} by looking into terminals A-B with the sources deactivated.


Thevenin Theorem

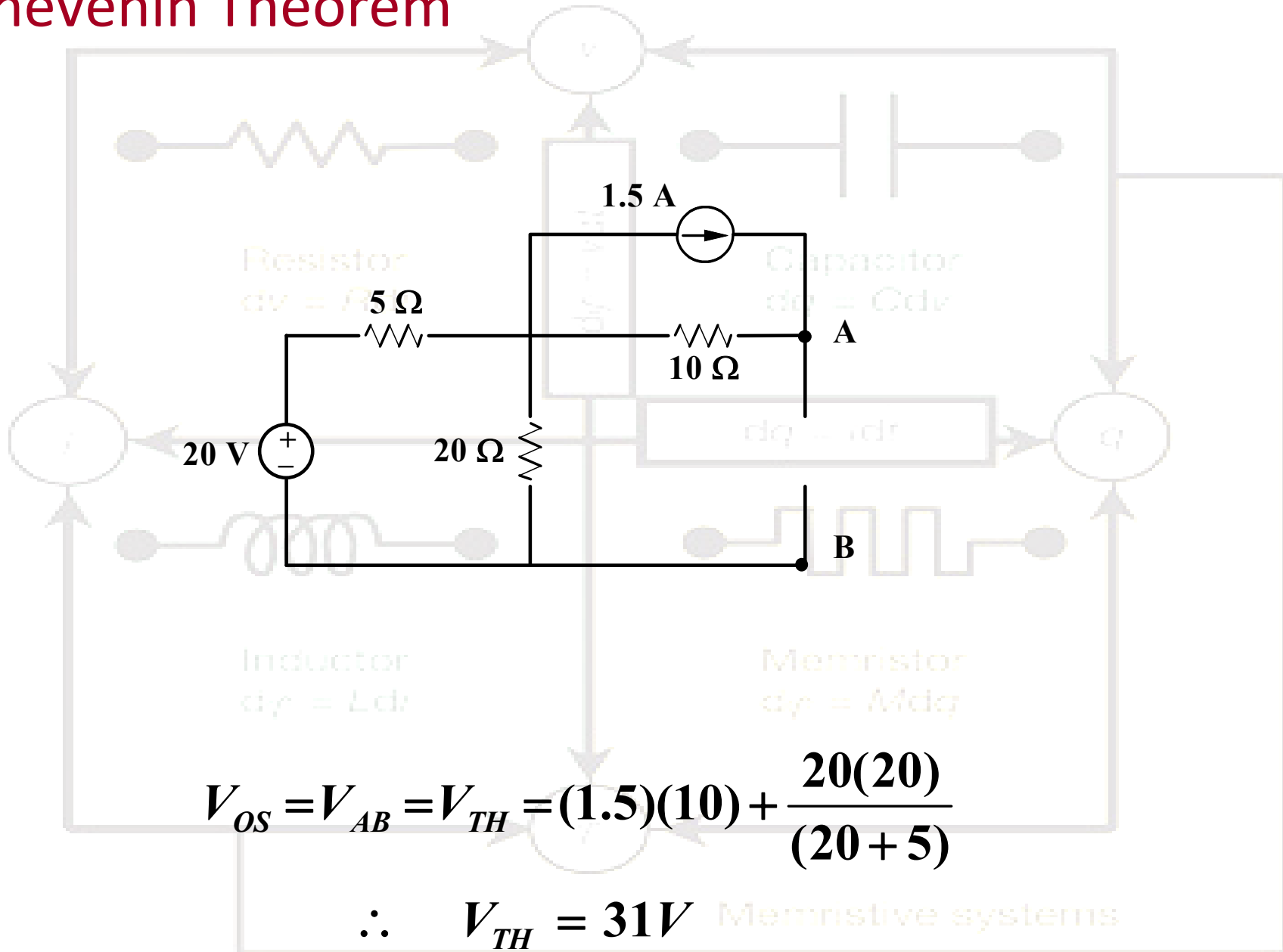

Thevenin Theorem

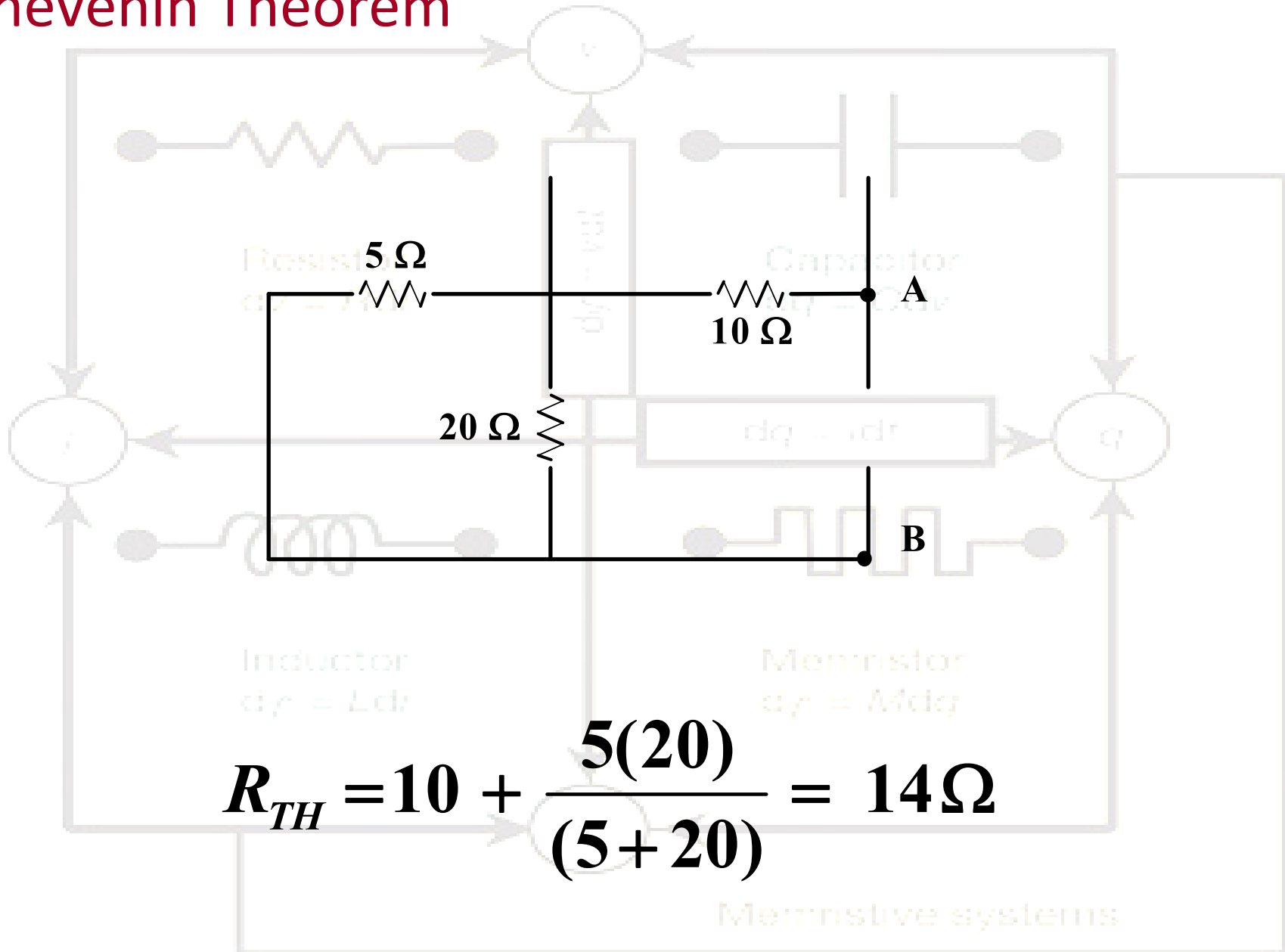


Thevenin Theorem

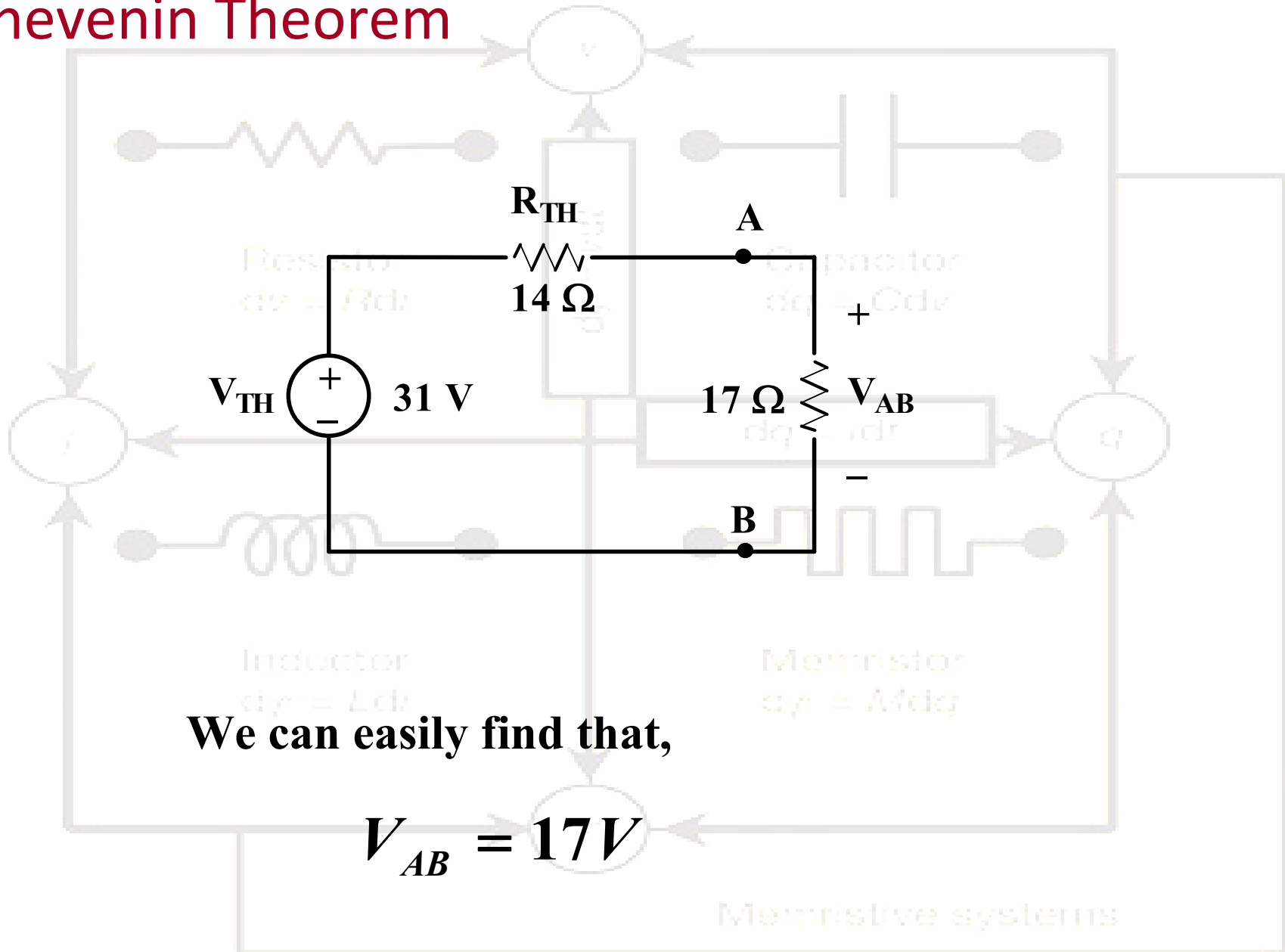

Norton theorem

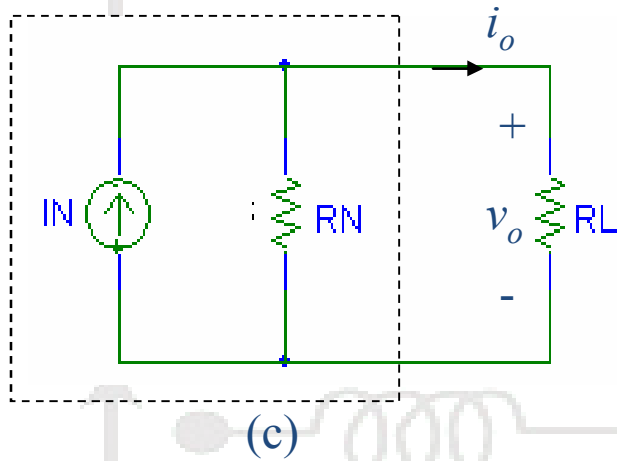•Based on source transformation we have learned, we can determine $i_N(t)$ and R_N



$$R_N = R_{TH} = \frac{v_{oc}(t)}{i_{sc}(t)}$$

$$i_N(t) = \frac{v_{TH}}{R_{TH}} = i_{shortcircuit}(t) \equiv i_{sc}(t)$$


Inductor
 $dy = Ldi$

Memristor
 $dy = Mdiq$


Memristive systems

Norton theorem

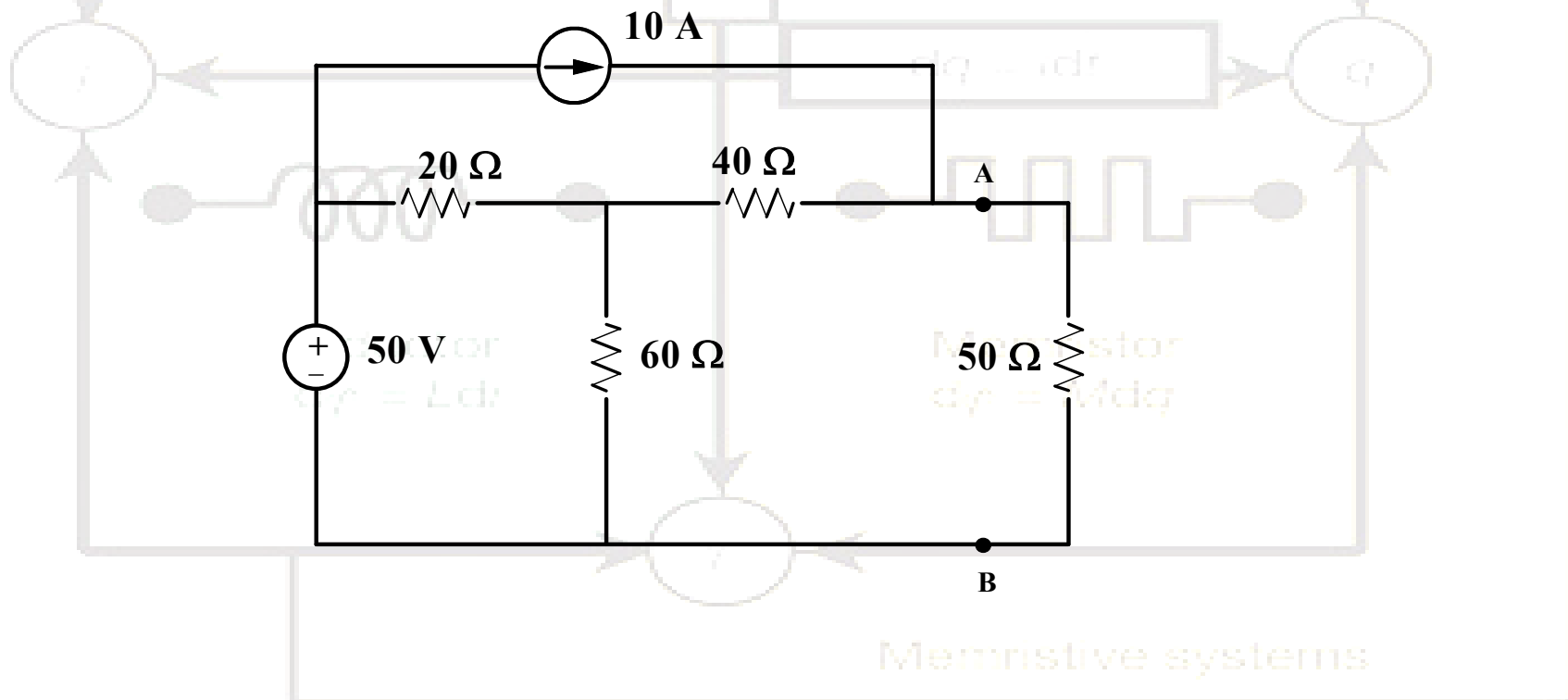Find the Norton equivalent circuit to the left of terminals A-B for the network shown below. Connect the Norton equivalent circuit to the load and find the current in the $50\ \Omega$ resistor.



Norton theorem

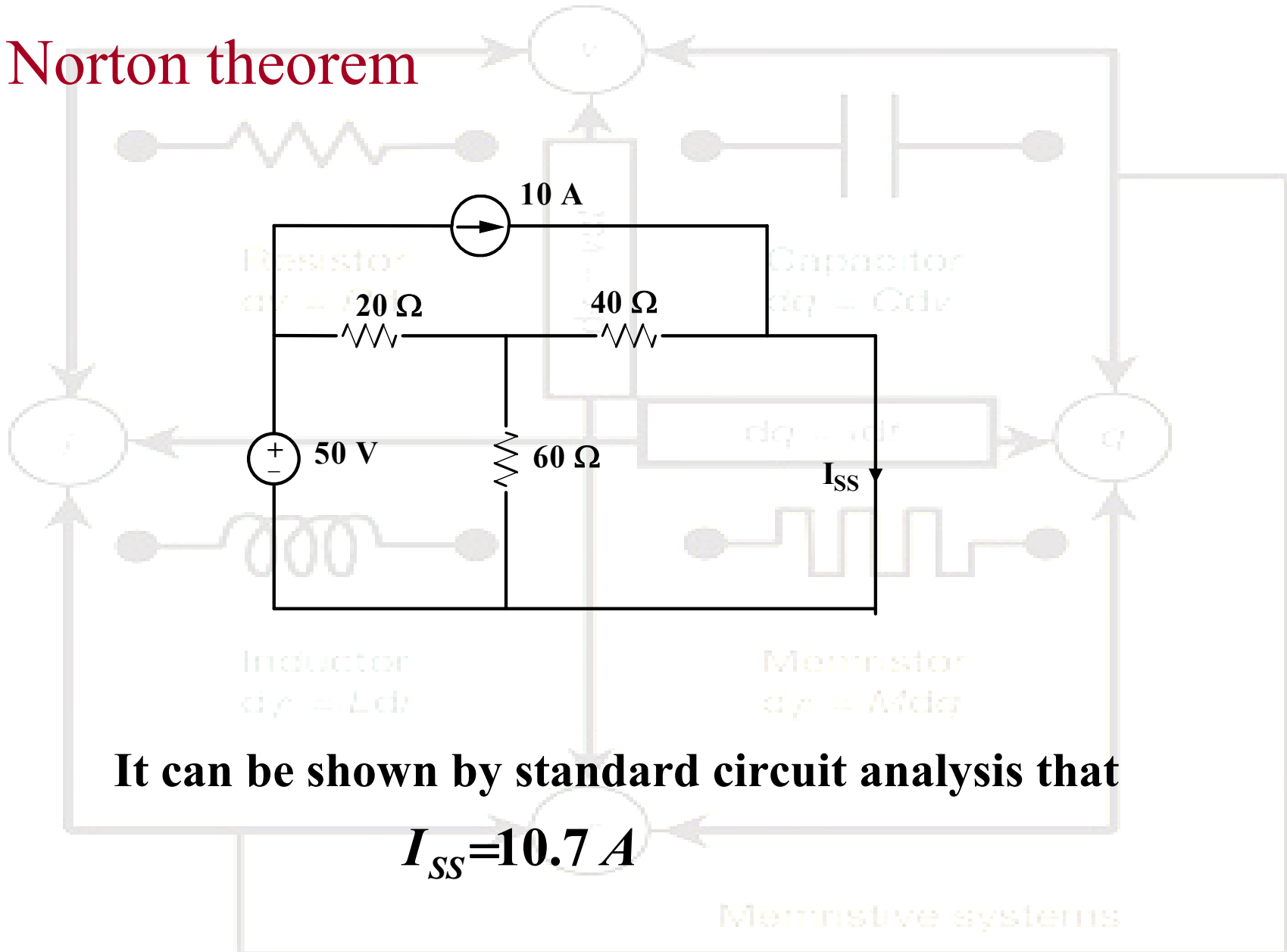

It can be shown by standard circuit analysis that

$$I_{SS} = 10.7 \text{ A}$$


Memristive systems

Norton theorem


It can also be shown that by deactivating the sources,
We find the resistance looking into terminals A-B is

$$R_N = 55 \Omega$$

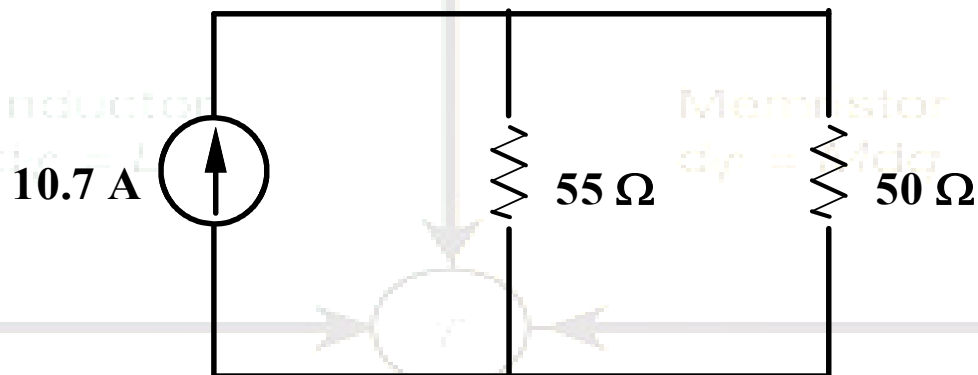R_N and R_{TH} will always be the same value for a given circuit.
The Norton equivalent circuit tied to the load is shown below.



Norton theorem

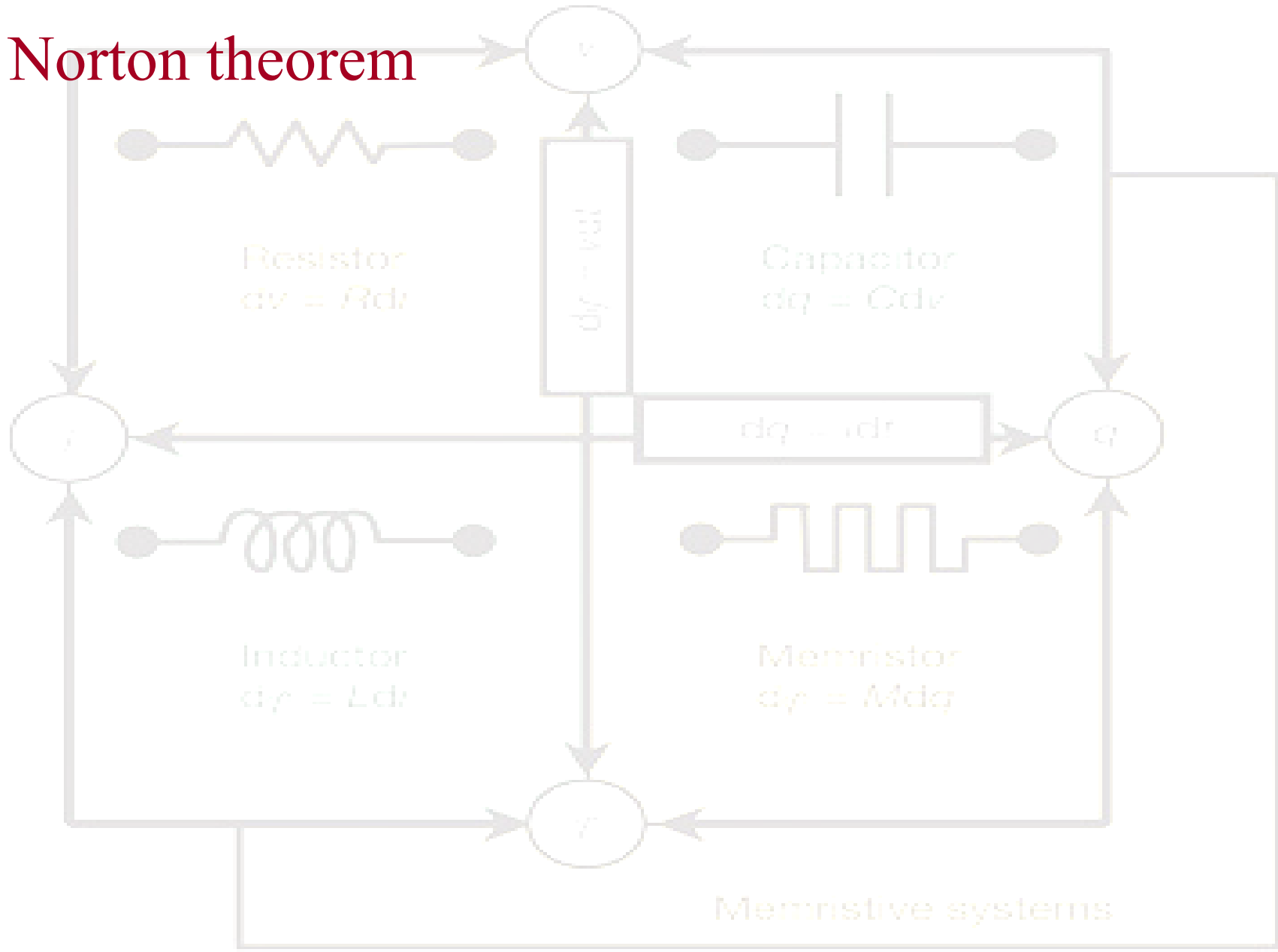

Norton theorem

