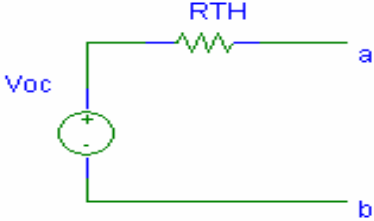
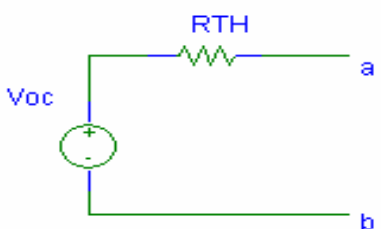



# Method of finding Thevenin equivalent Circuit

Number of method	If the circuit contains:	Thevenin equivalent circuit
1	Resistors and independent sources only (case 1)	 <p>a) Connect an open circuit between terminals a and b. Find <math>v_{oc} = v_{ab}</math> the voltage across the open circuit</p> <p>b) Deactivate the independent sources (replace independent voltage sources with short circuits and independent current sources with open circuits). Find <math>R_{TH}</math> by methods introduced in Chapter 2.</p>
2	Resistors and independent and dependent sources (case 2) or case 1	<p>a) Connect an open circuit between terminals a and b. Find <math>v_{oc} = v_{ab}</math> the voltage across the open terminals.</p> <p>b) Connect a short circuit between terminals a and b. Find <math>i_{sc}</math> the current directed from a to b in the short circuit.</p> <p>c) Calculate <math>R_{TH} = v_{oc}/i_{sc}</math>.</p>
3	Resistors and dependent sources only.	<p>a) Note that <math>v_{oc} = 0</math></p> <p>b) Connect a 1-A current source from terminal b to terminal a. Determine <math>v_{ab}</math></p> <p>c) Then <math>R_{TH} = v_{ab}/1</math>.</p>

# Method of finding Thevenin equivalent Circuit


Number of method	If the circuit contains:	Thevenin equivalent circuit
1	Resistors and independent sources only (case 1)	 <p>a) Connect an open circuit between terminals a and b. Find <math>v_{oc} = v_{ab}</math> the voltage across the open circuit</p> <p>b) Deactivate the independent sources (replace independent voltage sources with short circuits and independent current sources with open circuits). Find <math>R_{TH}</math> by methods introduced in Chapter 2.</p>
2	Resistors and independent and dependent sources (case 2) or case 1	<p>a) Connect an open circuit between terminals a and b. Find <math>v_{oc} = v_{ab}</math> the voltage across the open terminals.</p> <p>b) Connect a short circuit between terminals a and b. Find <math>i_{sc}</math>, the current directed from a to b in the short circuit.</p> <p>c) Calculate <math>R_{TH} = v_{oc}/i_{sc}</math>.</p>
3	Resistors and dependent sources only.	<p>a) Note that <math>v_{oc} = 0</math></p> <p>b) Connect a 1-A current source from terminal b to terminal a. Determine <math>v_{ab}</math></p> <p>c) Then <math>R_{TH} = v_{ab}/1</math>.</p>

# Method of finding Thevenin equivalent Circuit

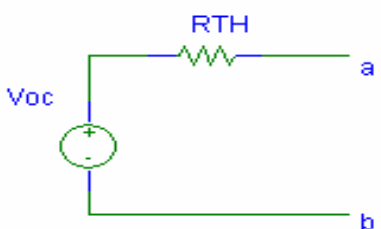Number of method	If the circuit contains:	Thevenin equivalent circuit
1	Resistors and independent sources only (case 1)	 <p>a) Connect an open circuit between terminals a and b. Find <math>v_{oc} = v_{ab}</math> the voltage across the open circuit</p> <p>b) Deactivate the independent sources (replace independent voltage sources with short circuits and independent current sources with open circuits). Find <math>R_{TH}</math> by methods introduced in Chapter 2.</p>
2	Resistors and independent and dependent sources (case 2) or case 1	<p>a) Connect an open circuit between terminals a and b. Find <math>v_{oc} = v_{ab}</math> the voltage across the open terminals.</p> <p>b) Connect a short circuit between terminals a and b. Find <math>i_{sc}</math> the current directed from a to b in the short circuit.</p> <p>c) Calculate <math>R_{TH} = v_{oc}/i_{sc}</math>.</p>
3	Resistors and dependent sources only.	<p>a) Note that <math>v_{oc} = 0</math></p> <p>b) Connect a 1-A current source from terminal b to terminal a. Determine <math>v_{ab}</math></p> <p>c) Then <math>R_{TH} = v_{ab}/1</math>.</p>
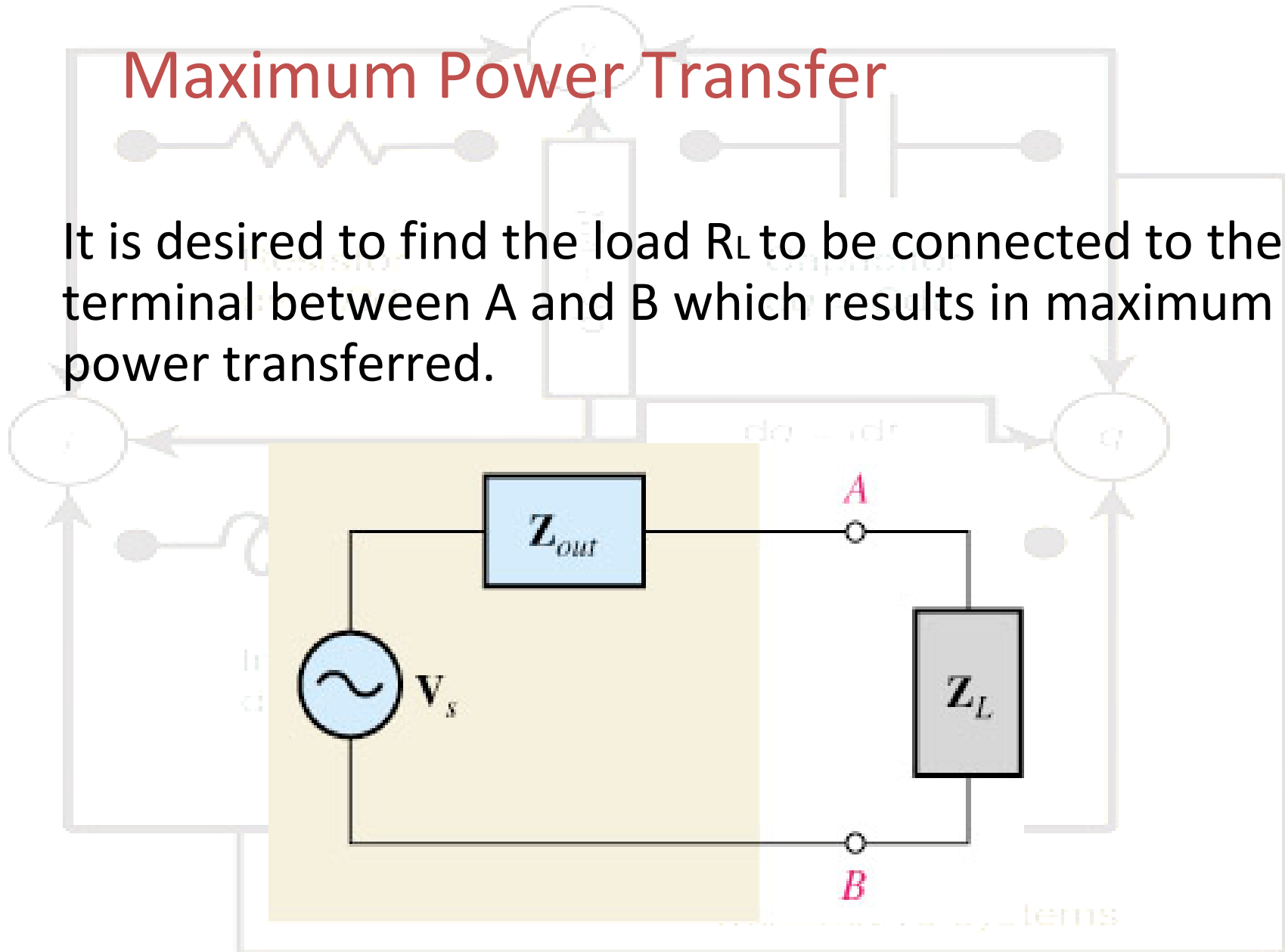
## Maximum Power Transfer

It is desired to find the load  $R_L$  to be connected to the terminal between A and B which results in maximum power transferred.



## Maximum Power Transfer

- To find the value of  $R_L$ , the network is replaced by its Thevenin equivalent.
- Then :

$$p = i^2 R_L = \left( \frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

- The  $R_L$  that maximizes the above equation can be found by taking the first derivative of  $p$  with respect to  $R_L$  and equate it to zero.

## Maximum Power Transfer

$$\frac{dp}{dR_L} = V_{Th}^2 \frac{(R_{Th} + R_L)^2 - R_L * 2(R_{Th} + R_L)}{(R_{Th} + R_L)^4}$$

By equating the above equation to zero:


$$(R_{Th} + R_L)^2 = 2R_L(R_{Th} + R_L)$$

$$\Rightarrow R_L = R_{Th}$$

Then the maximum power transferred:


$$P_{\max} = \frac{V_{Th}^2 R_L}{(2R_L)^2} = \frac{V_{Th}^2}{4R_L}$$

# Example

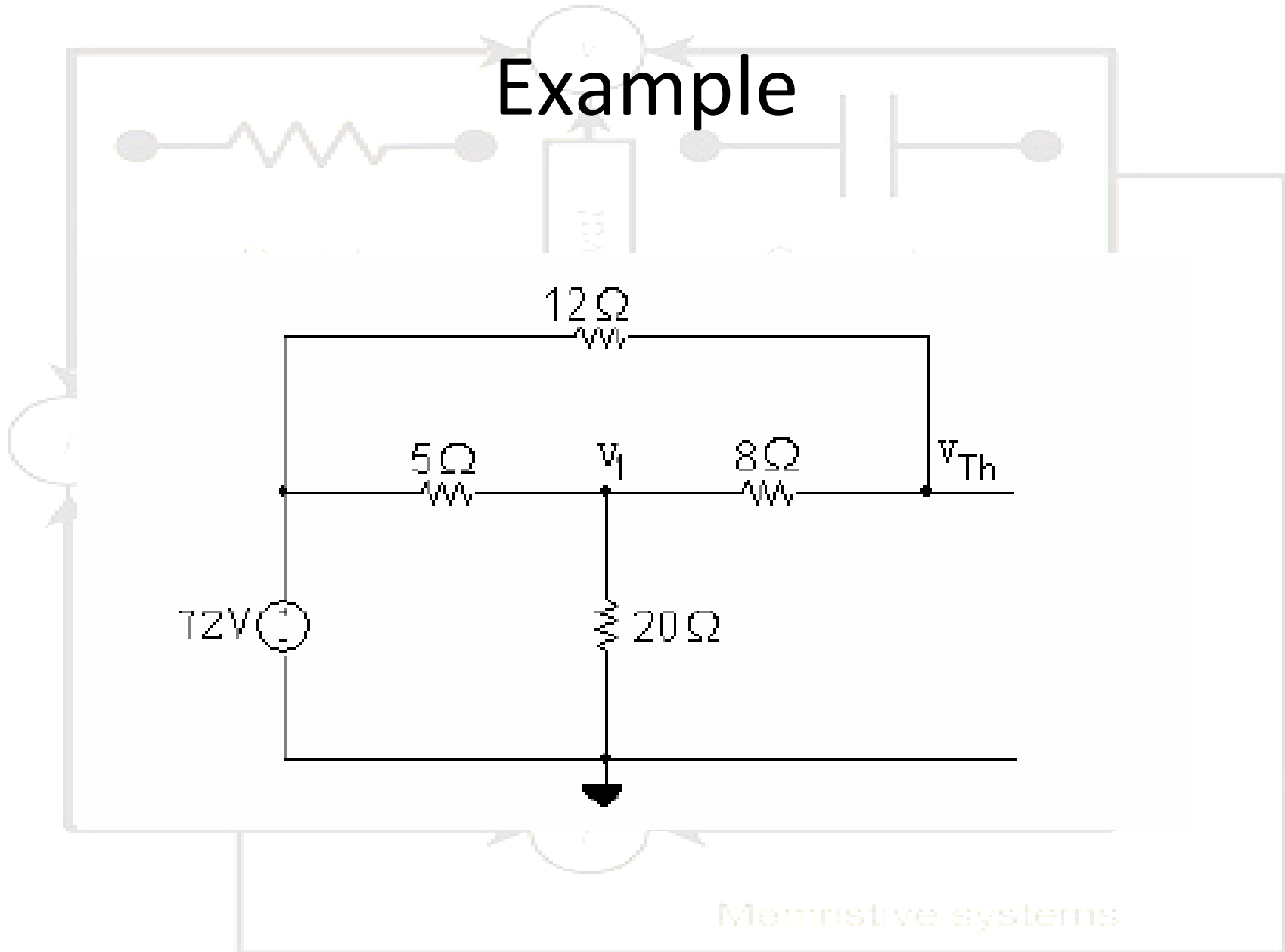




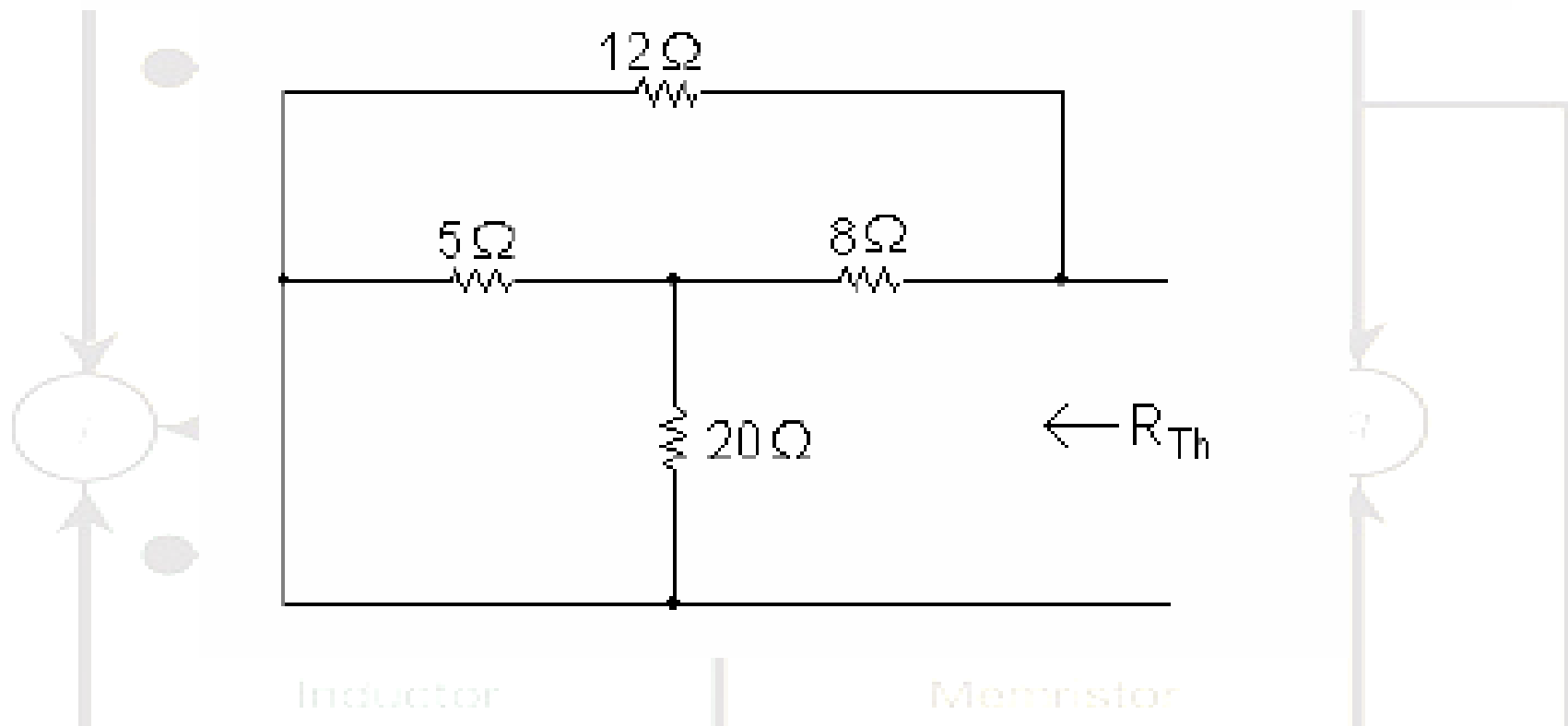To find  $R_{Th}$ , replace the 72 V source with a short circuit:



Note that the  $5\ \Omega$  and  $20\ \Omega$  resistors are in parallel, with an equivalent resistance of  $5\ ||\ 20 = 4\ \Omega$ . The equivalent  $4\ \Omega$  resistance is in series with the  $8\ \Omega$  resistor for an equivalent resistance of  $4 + 8 = 12\ \Omega$ . Finally, the  $12\ \Omega$  equivalent resistance is in parallel with the  $12\ \Omega$  resistor, so  $R_{Th} = 12\ ||\ 12 = 6\ \Omega$ .

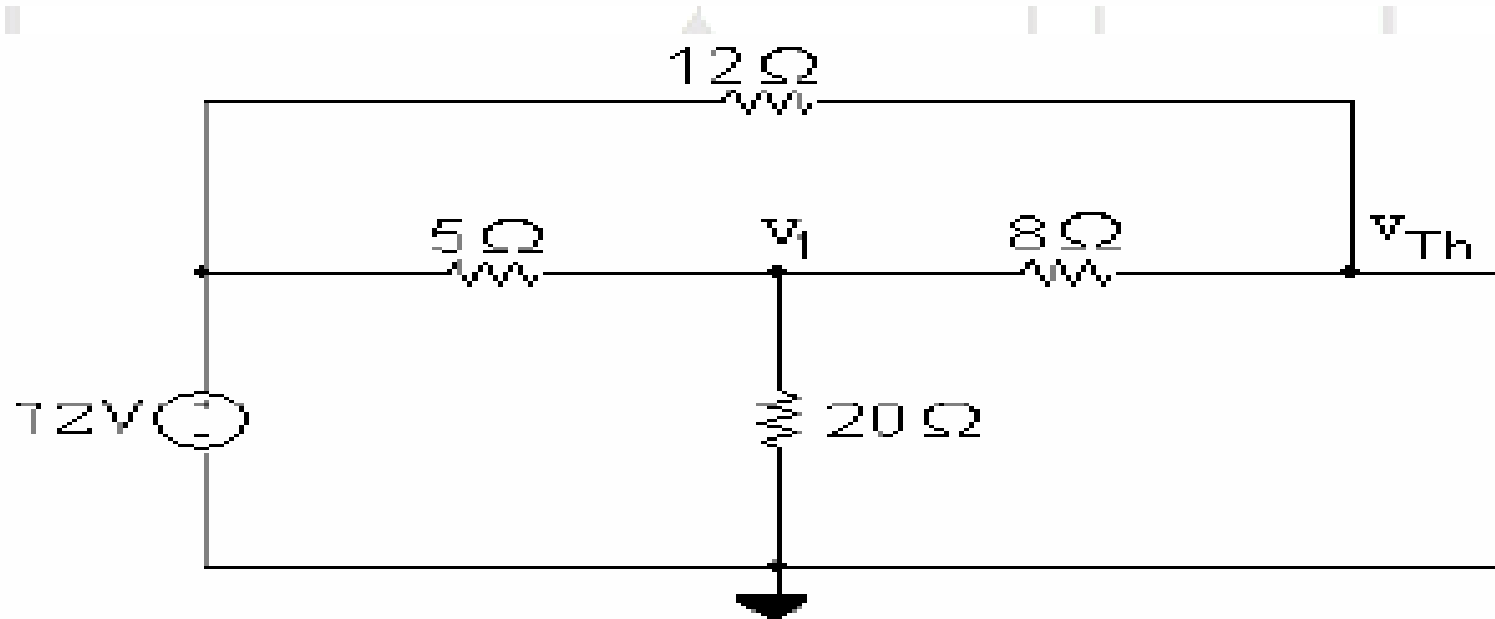Use node voltage analysis to find  $v_{Th}$ . Begin by redrawing the circuit and labeling the node voltages:



The node voltage equations are

$$\frac{v_1 - 72}{5} + \frac{v_1}{20} + \frac{v_1 - v_{Th}}{8} = 0$$

$$\frac{v_{Th} - v_1}{8} + \frac{v_{Th} - 72}{12} = 0$$

Place these equations in standard form:

$$v_1 \left( \frac{1}{5} + \frac{1}{20} + \frac{1}{8} \right) + v_{Th} \left( -\frac{1}{8} \right) = \frac{72}{5}$$

$$v_1 \left( -\frac{1}{8} \right) + v_{Th} \left( \frac{1}{8} + \frac{1}{12} \right) = 6$$

Solving,  $v_1 = 60$  V and  $v_{Th} = 64.8$  V. Therefore, the Thévenin equivalent circuit is a 64.8 V source in series with a 6 Ω resistor.

- RL must equal to  $R_{Th} = 6$  ohms
- The maximum power transferred=

Memristive systems