



**Arab Academy for Science and Technology and Maritime Transport**

**College of Engineering and Technology**

**Computer Engineering Department**

# **CC216 Digital Logic Design**

## **Lecture 3**








# Binary Logic and Gates

- Binary **logic** deals with binary variables (i.e. can have two values, “0” and “1”)
- Binary variables can undergo three basic logical operators **AND, OR and NOT**:
  - AND is denoted by a dot ( $\cdot$ )
  - OR is denoted by a plus ( $+$ ).
  - NOT is denoted by an overbar ( $\bar{\quad}$ ), a single quote mark (') after the variable.



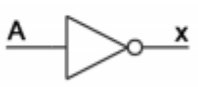
# Operator Definitions and Truth Tables

- ***Truth table*** - a tabular listing of the values of a function for ***all possible combinations of values on its arguments***
  - **Example: Truth tables for the basic logic operations:**
-


# Operator Definitions and Truth Tables

Name	NOT	AND	NAND	OR	NOR	XOR	XNOR																																																																																																
Alg. Expr.	$\bar{A}$	$AB$	$\overline{AB}$	$A+B$	$\overline{A+B}$	$A \oplus B$	$\overline{A \oplus B}$																																																																																																
Symbol																																																																																																							
Truth Table	<table border="1"> <thead> <tr> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	X	0	1	1	0	<table border="1"> <thead> <tr> <th>B</th> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	B	A	X	0	0	0	0	1	0	1	0	0	1	1	1	<table border="1"> <thead> <tr> <th>B</th> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	B	A	X	0	0	1	0	1	1	1	0	1	1	1	0	<table border="1"> <thead> <tr> <th>B</th> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	B	A	X	0	0	0	0	1	1	1	0	1	1	1	1	<table border="1"> <thead> <tr> <th>B</th> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	B	A	X	0	0	1	0	1	0	1	0	0	1	1	0	<table border="1"> <thead> <tr> <th>B</th> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	B	A	X	0	0	0	0	1	1	1	0	1	1	1	0	<table border="1"> <thead> <tr> <th>B</th> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	B	A	X	0	0	1	0	1	0	1	0	0	1	1	1
A	X																																																																																																						
0	1																																																																																																						
1	0																																																																																																						
B	A	X																																																																																																					
0	0	0																																																																																																					
0	1	0																																																																																																					
1	0	0																																																																																																					
1	1	1																																																																																																					
B	A	X																																																																																																					
0	0	1																																																																																																					
0	1	1																																																																																																					
1	0	1																																																																																																					
1	1	0																																																																																																					
B	A	X																																																																																																					
0	0	0																																																																																																					
0	1	1																																																																																																					
1	0	1																																																																																																					
1	1	1																																																																																																					
B	A	X																																																																																																					
0	0	1																																																																																																					
0	1	0																																																																																																					
1	0	0																																																																																																					
1	1	0																																																																																																					
B	A	X																																																																																																					
0	0	0																																																																																																					
0	1	1																																																																																																					
1	0	1																																																																																																					
1	1	0																																																																																																					
B	A	X																																																																																																					
0	0	1																																																																																																					
0	1	0																																																																																																					
1	0	0																																																																																																					
1	1	1																																																																																																					

# Logic Gate Symbols and Behavior

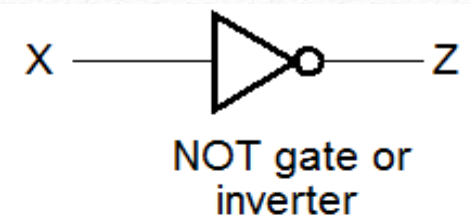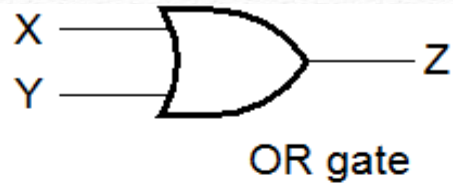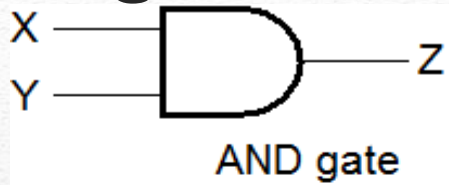

(a) Graphic symbols

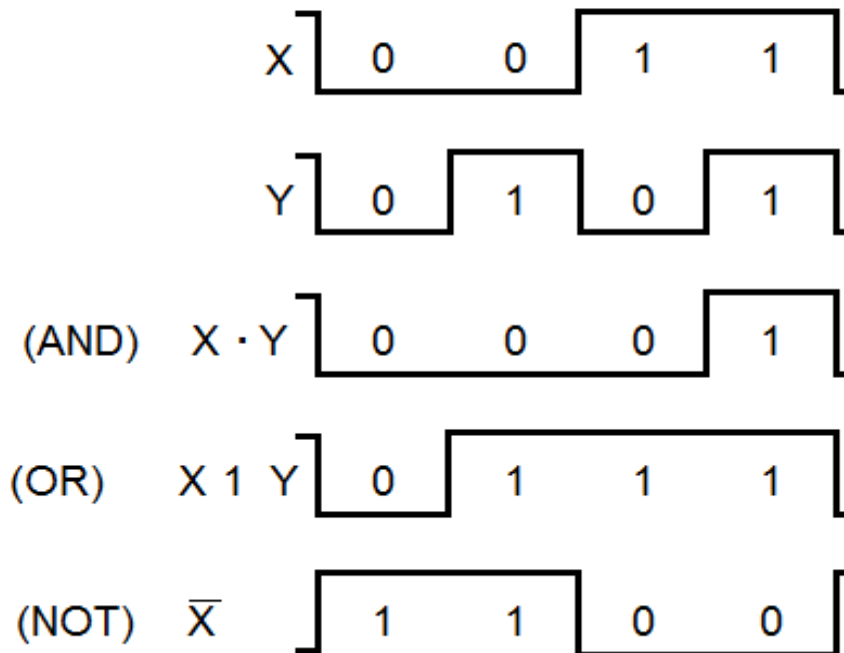


(b) Timing diagram

# Logic Diagrams and Expressions

$$F = A + A\bar{B}$$

Logic Diagram

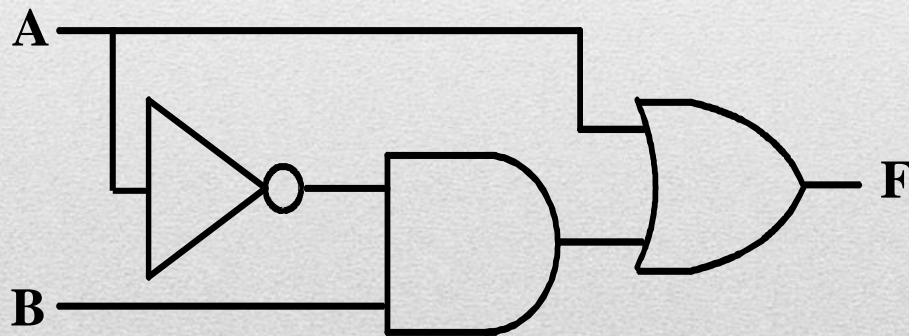

Truth Table

A	B	F
0	0	
0	1	
1	0	
1	1	

# Boolean Algebra

- Boolean algebra deals with binary variables and a set of three basic logic operations: AND ( $\cdot$ ), OR ( $+$ ) and NOT ( $\bar{\phantom{x}}$ ) that satisfy basic identities

## Basic identities

---

1.  $X + 0 = X$

3.  $X + 1 = 1$

5.  $X + X = X$

7.  $X + \bar{X} = 1$

9.  $\bar{\bar{X}} = X$

2.  $X \cdot 1 = X$

4.  $X \cdot 0 = 0$

6.  $X \cdot X = X$

8.  $X \cdot \bar{X} = 0$

# Boolean Algebra

## Boolean Theorems of multiple variables

---

10.  $X + Y = Y + X$

Commutative

11.  $XY = YX$

12.  $(X + Y) + Z = X + (Y + Z)$

Associative

13.  $(XY)Z = X(YZ)$

14.  $X(Y + Z) = XY + XZ$

Distributive

15.  $X + YZ = (X + Y)(X + Z)$

16.  $\overline{X + Y} = \overline{X} \cdot \overline{Y}$

DeMorgan's

17.  $\overline{X \cdot Y} = \overline{X} + \overline{Y}$

---



# Example: Boolean Algebraic Proof

- $A + A \cdot B = A$       (**Absorption Theorem**)

Proof Steps

Justification

$$A + A \cdot B$$

$$= A \cdot 1 + A \cdot B$$

(Operation with 1)

$$= A \cdot (1 + B)$$

(Distributive Law)

$$= A \cdot 1$$

(Operation with 1)

$$= A$$

# Example: Boolean Algebraic Proof

$$A + A'B = A + B$$

$$A + AB + A'B$$

$$A + B(A + A')$$

$$A + B(1)$$

$$A + B$$

# DeMorgan


Use **DeMorgan's** Theorem to complement a function:

- Interchange AND and OR operators
- Complement each constant value and literal

# Example: DeMorgan's theorem

$$F = AB + C(E+D)$$

Find  $\overline{F}$

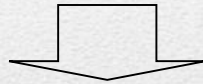

Exercise: find  $\overline{G}$   
 $G = UX(Y+VZ)$

