



Arab Academy for Science and Technology and Maritime Transport

College of Engineering and Technology

Computer Engineering Department

CC216 Digital Logic Design

Lecture 3








Binary Logic and Gates

- Binary **logic** deals with binary variables (i.e. can have two values, “0” and “1”)
- Binary variables can undergo three basic logical operators **AND, OR and NOT**:
 - AND is denoted by a dot (\cdot)
 - OR is denoted by a plus ($+$).
 - NOT is denoted by an overbar ($\bar{\quad}$), a single quote mark (') after the variable.



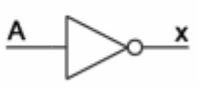
Operator Definitions and Truth Tables

- ***Truth table*** - a tabular listing of the values of a function for ***all possible combinations of values on its arguments***
 - **Example: Truth tables for the basic logic operations:**
-


Operator Definitions and Truth Tables

Name	NOT	AND	NAND	OR	NOR	XOR	XNOR																																																																																																
Alg. Expr.	\bar{A}	AB	\overline{AB}	$A+B$	$\overline{A+B}$	$A \oplus B$	$\overline{A \oplus B}$																																																																																																
Symbol																																																																																																							
Truth Table	<table border="1"> <thead> <tr> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> </tr> </tbody> </table>	A	X	0	1	1	0	<table border="1"> <thead> <tr> <th>B</th> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	B	A	X	0	0	0	0	1	0	1	0	0	1	1	1	<table border="1"> <thead> <tr> <th>B</th> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	B	A	X	0	0	1	0	1	1	1	0	1	1	1	0	<table border="1"> <thead> <tr> <th>B</th> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	B	A	X	0	0	0	0	1	1	1	0	1	1	1	1	<table border="1"> <thead> <tr> <th>B</th> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	B	A	X	0	0	1	0	1	0	1	0	0	1	1	0	<table border="1"> <thead> <tr> <th>B</th> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	B	A	X	0	0	0	0	1	1	1	0	1	1	1	0	<table border="1"> <thead> <tr> <th>B</th> <th>A</th> <th>X</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	B	A	X	0	0	1	0	1	0	1	0	0	1	1	1
A	X																																																																																																						
0	1																																																																																																						
1	0																																																																																																						
B	A	X																																																																																																					
0	0	0																																																																																																					
0	1	0																																																																																																					
1	0	0																																																																																																					
1	1	1																																																																																																					
B	A	X																																																																																																					
0	0	1																																																																																																					
0	1	1																																																																																																					
1	0	1																																																																																																					
1	1	0																																																																																																					
B	A	X																																																																																																					
0	0	0																																																																																																					
0	1	1																																																																																																					
1	0	1																																																																																																					
1	1	1																																																																																																					
B	A	X																																																																																																					
0	0	1																																																																																																					
0	1	0																																																																																																					
1	0	0																																																																																																					
1	1	0																																																																																																					
B	A	X																																																																																																					
0	0	0																																																																																																					
0	1	1																																																																																																					
1	0	1																																																																																																					
1	1	0																																																																																																					
B	A	X																																																																																																					
0	0	1																																																																																																					
0	1	0																																																																																																					
1	0	0																																																																																																					
1	1	1																																																																																																					

Logic Gate Symbols and Behavior

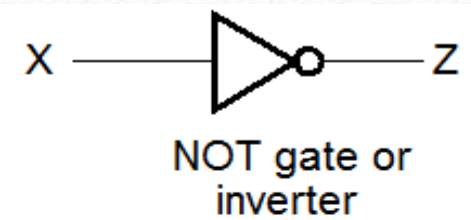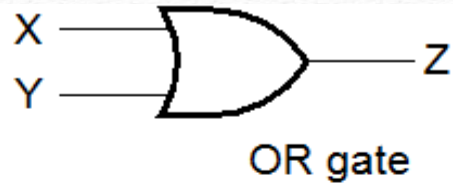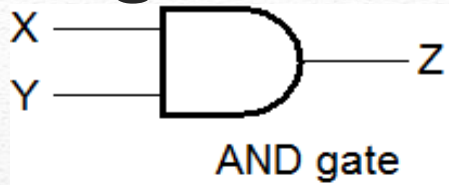

(a) Graphic symbols

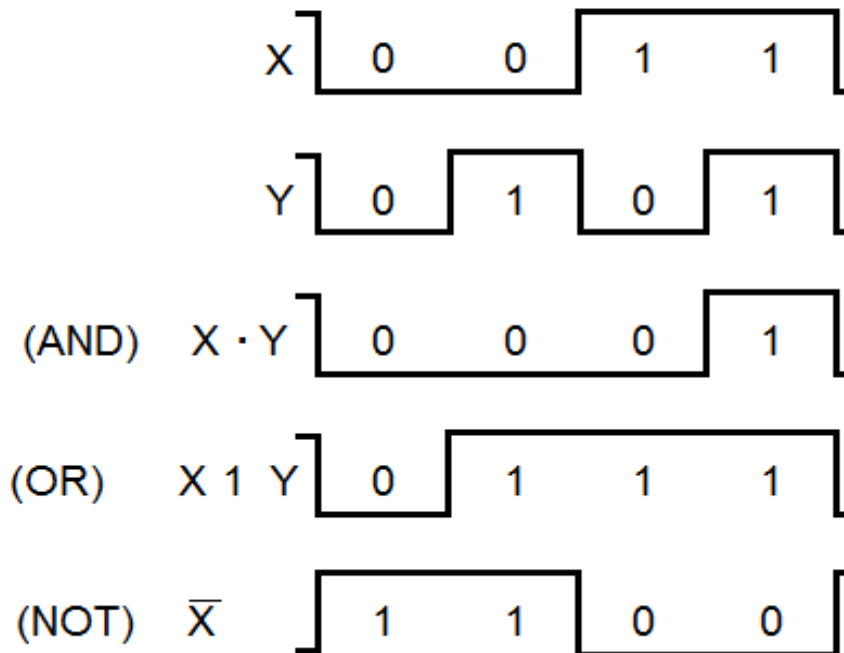


(b) Timing diagram

Logic Diagrams and Expressions

$$F = A + A\bar{B}$$

Logic Diagram

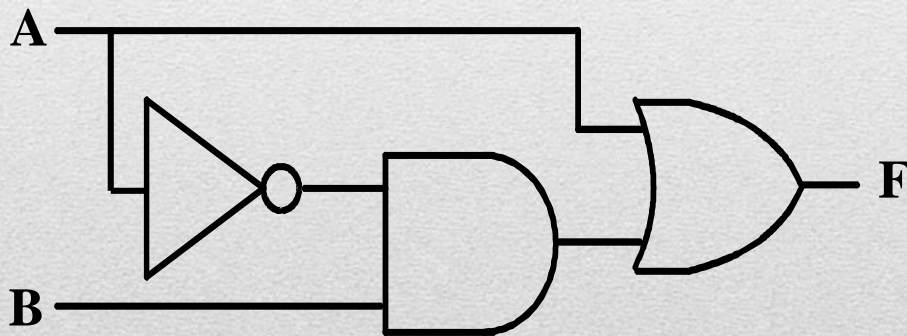

Truth Table

A	B	F
0	0	
0	1	
1	0	
1	1	

Boolean Algebra

- Boolean algebra deals with binary variables and a set of three basic logic operations: AND (\cdot), OR ($+$) and NOT ($\bar{}$) that satisfy basic identities

Basic identities

1. $X + 0 = X$

3. $X + 1 = 1$

5. $X + X = X$

7. $X + \bar{X} = 1$

9. $\bar{\bar{X}} = X$

2. $X \cdot 1 = X$

4. $X \cdot 0 = 0$

6. $X \cdot X = X$

8. $X \cdot \bar{X} = 0$

Boolean Algebra

Boolean Theorems of multiple variables

10. $X + Y = Y + X$

Commutative

11. $XY = YX$

12. $(X + Y) + Z = X + (Y + Z)$

Associative

13. $(XY)Z = X(YZ)$

14. $X(Y + Z) = XY + XZ$

Distributive

15. $X + YZ = (X + Y)(X + Z)$

16. $\overline{X + Y} = \overline{X} \cdot \overline{Y}$

DeMorgan's

17. $\overline{X \cdot Y} = \overline{X} + \overline{Y}$

Example: Boolean Algebraic Proof

- $A + A \cdot B = A$ (**Absorption Theorem**)

Proof Steps

Justification

$$A + A \cdot B$$

$$= A \cdot 1 + A \cdot B$$

(Operation with 1)

$$= A \cdot (1 + B)$$

(Distributive Law)

$$= A \cdot 1$$

(Operation with 1)

$$= A$$

Example: Boolean Algebraic Proof

$$A + A'B = A + B$$

$$A + AB + A'B$$

$$A + B(A + A')$$

$$A + B(1)$$

$$A + B$$

DeMorgan


Use **DeMorgan's** Theorem to complement a function:

- Interchange AND and OR operators
- Complement each constant value and literal

Example: DeMorgan's theorem

$$F = AB + C(E+D)$$

Find \overline{F}

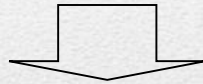

Exercise: find \overline{G}
 $G = UX(Y+VZ)$

